


elektor

electronics worldwide



e-CAD Software FREE DOWNLOAD

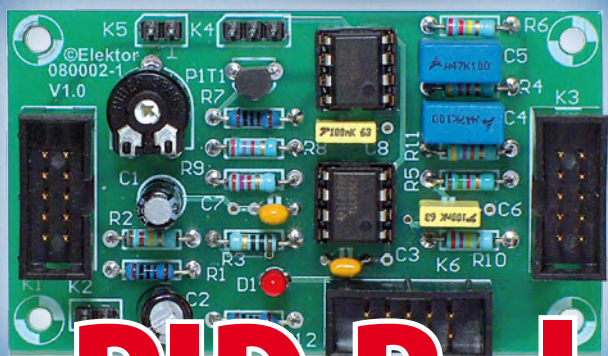...LED BICYCLE LIGHT...BASCOM AVR COURSE...DCC CONTROLLER...ULTRASONIC DETECTOR



PID Balancing Act

...a real challenge...

Think that Cursor!

brain-driven user interface




IDEAL KITS FOR ELECTRONIC ENTHUSIASTS



ULTRA LOW DISTORTION AMPLIFIER MODULE

KC-5470 £26.25 plus postage & packing

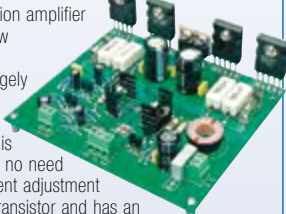This ultra low distortion amplifier module uses the new ThermalTrak power transistors and is largely based on the high-performance Class-A amplifier. This improved circuit has no need for a quiescent current adjustment or a Vbe multiplier transistor and has an exceptionally low distortion figure. Kit supplied with PCB and all electronic components. Heatsink and power supply not included.



- Output Power: 135WRMS into 8 ohms and 200WRMS into 4 ohms
- Freq Resp. at 1W: 4Hz to 50kHz
- Harmonic Distortion: <.008% from 20Hz to 20kHz

NEW FOR 08

BRIDGE MODE ADAPTOR

KC-5469 £7.75 plus postage & packing

IDEAL FOR STEREO AMPLIFIERS. Lets you run a stereo amplifier in 'Bridged Mode' to effectively double the power available to drive a single speaker. There are no mods required on the amplifier and the signal processing is done by the kit before the signals are fed to the stereo amp. Ideal for say, using a stereo amp as an occasional PA amp for social functions or using an old amplifier to drive a sub-woofer in a home theatre.



- Kit supplied with silk screened PCB and all specified components.
- Requires balanced (+/-) power supply.

LOW COST DIGITAL MULTIMETER

QM-1500 £2.25 plus postage & packing

This full featured Digital Multimeter is perfect for the home handyman or young experimenter and will give years of reliable service. It features a huge 10A DC current range as well as diode and transistor testing functions. Also measures AC & DC volts and resistance. At this price you should buy two!



LED WATER LEVEL INDICATOR MKII KIT

KC-5449 £10.25 plus postage & packing

This simple circuit illuminates a string of LEDs to quickly indicate the water level in a rainwater tank. The more LEDs that illuminate, the higher the water level is inside the tank. The input signal is provided by ten sensors located in the water tank and connected to the indicator unit via light duty figure-8 cable. Kit supplied with PCB with overlay, machined case with screen printed lid and all electronic components.



- Requires 12-18V AC or DC 500mA plugpack.

PIC LOGIC PROBE KIT

KC-5457 £4.50 plus postage & packing

Most logic probes are designed to operate on 5V rails. This design operates on a wide voltage range down to 2.8V so it's suitable for use on the most modern circuits. It's also extremely compact with SMT devices on a PCB only 5mm wide, so it will fit inside a very slim case. It's capable of picking up a pulse only 50mS long and will also detect and hold infrequent pulses when in latch mode. Kit includes PCB and all specified electronic components including pre-programmed PIC. You'll need to add your own case and probe - a clear ballpoint pen case and needle, works well.



STAINLESS STEEL TOOLS

5" Stainless Steel Long Nose Pliers TH-1888 £4.95 plus postage & pkg



Made from polished stainless steel, have a leaf spring and have serrated jaws.

Stainless Steel Side Cutters - 115mm TH-1890 £3.50 + postage & pkg


High quality small side cutters that have thick (2mm) blades and soft comfort plastic spring loaded handles.



THEREMIN SYNTHESIZER KIT

KC-5295 £17.50 plus postage & packing

The Therman is a strange musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Therman. By moving your hand between the antenna and the metal plate, you can create unusual sound effects. Kit includes a machined, silkscreened, and pre drilled case, circuit board, all electronic components with clear English instructions.

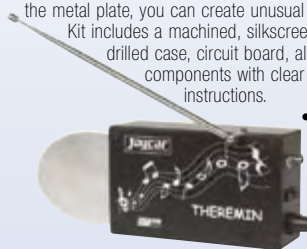

- Required 9VDC wall adapter (Maplin #GS74R £7.99)

IR REMOTE EXTENDER MKII KIT

KC-5432 £7.25 plus postage & packing

Operate your DVD player or digital decoder using its remote control from another room. It picks up the signal from the remote control and sends it via a 2-wire cable to an infrared LED located close to the device. This improved model features fast data transfer, capable of transmitting pay TV digital remote control signals using the Pace 400 series decoder. Kit supplied with case, screen printed front panel, PCB with overlay and all electronic components.



- Requires 9 VDC power (Maplin #GS74R £7.99) and 2-wire cable

RESISTANCE WHEEL

RR-0700 £5.75 plus postage & packing

Great for experiments or selecting the best resistance for a circuit. Choose from 36 x 0.25W 5% resistors ranging from 5 ohms to 1M ohms. Comes complete with leads and insulated crocodile clips.



FREE CATALOGUE

Checkout Jaycar's extensive range

We have kits & electronic projects for use in:

- Audio & Video
- Car & Automotive
- Computer
- Power
- Lighting
- Test & Meters
- Learning & Educational
- General Electronics Projects
- Gifts, Gadgets & Just for fun!

For your FREE catalogue logon to www.jaycarelectronics.co.uk/elektor or check out the range at www.jaycarelectronics.co.uk



POST & PACKING CHARGES

Order Value	Cost
£10 - £49.99	£5
£50 - £99.99	£10
£100 - £199.99	£20
£200 - £499.99	£30
£500+	£40

Max weight 12lb (5kg).
Heavier parcels POA.
Minimum order £10.

Note: Products are despatched from Australia, so local customs duty & taxes may apply. Prices valid till 30/09/08

HOW TO ORDER

- **ORDER ON-LINE:** www.jaycarelectronics.co.uk
- **PHONE:** 0800 032 7241*
- **FAX:** +61 2 8832 3118*
- **EMAIL:** techstore@jaycarelectronics.co.uk
- **POST:** P.O. Box 107, Rydalmere NSW 2116 Australia
- **ALL PRICING IN POUNDS STERLING**
- **MINIMUM ORDER ONLY £10**

*Australian Eastern Standard Time (Monday - Friday 09.00 to 17.30 GMT + 10 hours only)
Expect 10-14 days for air parcel delivery

0800 032 7241

www.jaycarelectronics.co.uk

Jaycar
Electronics

BitScope USB Mixed Signal Oscilloscope

Analog + Digital

Digital Storage Oscilloscope

- ✓ Dual Channel Digital Scope with industry standard probes or POD connected analog inputs. Fully opto-isolated.

Mixed Signal Oscilloscope

- ✓ Capture and display analog and logic signals together with sophisticated cross-triggers for precise analog/logic timing.

Multi-Band Spectrum Analyzer

- ✓ Display analog waveforms and their spectra simultaneously. Base-band or RF displays with variable bandwidth control.

Multi-Channel Logic Analyzer

- ✓ Eight logic/trigger channels with event capture to 25nS.

DSP Waveform Generator

- ✓ Optional flash programmable DSP based function generator. Operates concurrently with waveform and logic capture.

Mixed Signal Data Recorder

- ✓ Record to disk anything BitScope can capture. Supports on-screen waveform replay and export.

User Programmable Tools and Drivers

- ✓ Use supplied drivers and interfaces to build custom test and measurement and data acquisition solutions.

Inventing the future requires a lot of test gear...

...or a BitScope



BS100U Mixed Signal Storage Scope & Analyzer

Innovations in modern electronics engineering are leading the new wave of inventions that promise clean and energy efficient technologies that will change the way we live.

It's a sophisticated world mixing digital logic, complex analog signals and high speed events. To make sense of it all you need to see exactly what's going on in real-time.

BS100U combines analog and digital capture and analysis in one cost effective test and measurement package to give you the tools you need to navigate this exciting new frontier.



Standard 1M/20pF BNC inputs

Smart POD Connector



Opto-isolated USB 2.0

12VDC with low power modes


BitScope DSO Software for Windows and Linux

BS100U includes BitScope DSO the fast and intuitive multichannel test and measurement software for your PC or notebook.

Capture deep buffer one-shots, display waveforms and spectra real-time or capture mixed signal data to disk. Comprehensive integration means you can view analog and logic signals in many different ways all at the click of a button.

The software may also be used stand-alone to share data with colleagues, students or customers.

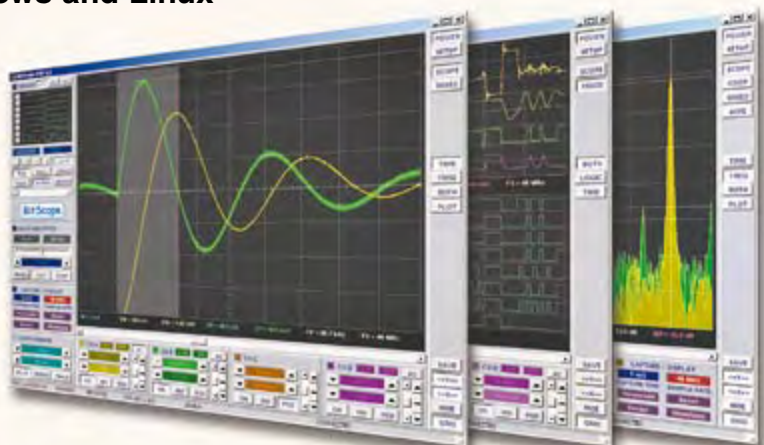Waveforms may be exported as portable image files or live captures replayed on another PC as if a BS100U was locally connected.



www.bitscope.com

Crossing the Pyrenees, Alps, Atlantic & the Great Wall

Electronics is now a largely borderless activity as far as publishing and exchange of information are concerned. The only barrier that seems to exist (mostly in people's heads) is language, but hey no problem as English is the *lingua franca* of electronics, everyone knows their *printers* and *datasheets* and Elektor is available in several translated editions to those preferring their mother tongue. That is not to say the *couleur locale* can be dispensed with and consequently all our international editors and advertisers do their best to localise the magazine to their markets.

The Spanish edition of Elektor, admirably edited by Eduardo Corral, was launched one year ago to reach readers not just in Spain, but also in the US and a number of south-American countries. The same basically for the Portuguese licenced edition, of which a special version is produced for Brazil. By the time you read this, Elektor's Italian licence partner Inware Edizioni srl should have their website and subscriptions intake up and running and we can look forward to seeing an authorised Italian Elektor again after a dozen or so years.


Elektor is also crossing the Atlantic, now trialling the US market with a slightly adapted, locally printed and distributed version of this, the international English version of the magazine. Although our entry into the 'States is still in the 'block diagram' phase, I'm convinced that adding North American subscribers and advertisers holds a promise of significantly widening the circle of enthusiasts, professionals and companies serviced by our magazine, website, products and events. Speaking of e-events, we're now taking reservations (via the Elektor website) for our second business trip to China in November of this year. The second round will comprise a business conference with local industrialists and a visit to the only government-authorised market for electronics trade and manufacturing. A visit to the Great Wall is also scheduled in — if only to see for yourself that it failed both ways as a barrier to modern electronics.

Jan Buiting
Editor

The idea behind this College project is to try to balance a ball on a beam using a PID control loop. If the ball is pushed, the system moves the beam to return the ball to its initial position.

So get out your USB DAQ card and a PC, and show off!


BALL & BEAM for Elektor USB DAQ Card

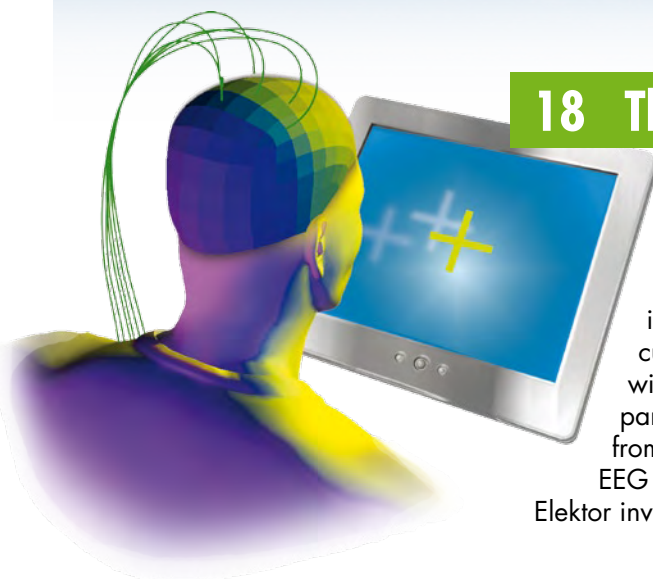

18 The Thought Cursor

Controlling a computer using the power of thought alone is less far-fetched than you might believe. The easy part is to measure precisely the tiny currents in the brain associated with thought processes; the hard part is to extract the thoughts from the morass of multi-channel EEG (electroencephalogram) data. Elektor investigates.

34 DCC Command Station

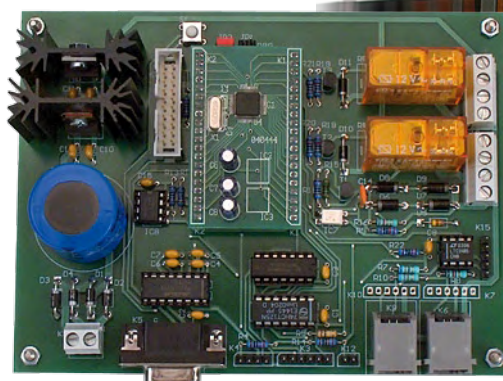

In this article we present a design for the device that forms the heart of a digitally controlled model railway: the DCC Command Station. The computing power in this advanced design is provided by a high-performance ARM7 processor.

CONTENTS

Volume 34
September 2008
no. 381

projects

- 26** Ball & Beam for Elektor USB DAQ Card
- 34** DCC Command Station
- 44** Luxury LED Bicycle Light
- 50** Light as Air (ATM18 series)
- 56** BASCOM AVR Course (1)
- 60** Projection over Hundreds of Metres
- 68** E-blocks: Accelerated Design
- 72** Ultrasonic Sound Detector

technology


- 18** The Thought Cursor

info & market

- 6** Colophon
- 8** Mailbox
- 10** News & New Products
- 20** Panorama: e-CAD Anthology
- 80** Elektor SHOP
- 84** Sneak Preview

infotainment

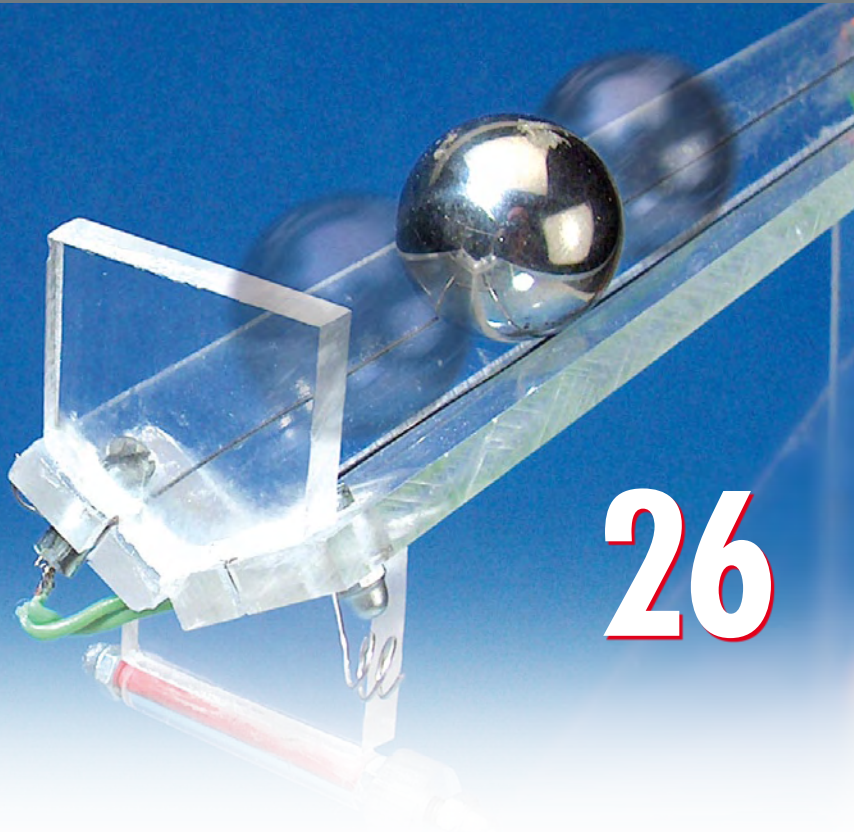- 76** Hexadoku
- 77** Retronics: EIT decade scaler tube (ca. 1954)



26

20 Panorama: e-CAD Anthology



The November 2005 'Kaleidoscope' DVD with 30-odd programs relating to electronics CAD (Computer-Aided Design) was a huge success. Three years on, we decided to repeat the exercise. This time round, instead of physical DVD with the magazine, the programs come as free downloads!

60 Projection over Hundreds of Metres

With a few servos, a laser module from eBay, a microcontroller and a little dexterity we can make a laser projector which, depending on the laser, can be seen from several hundreds of metres.



elektor international media

Elektor International Media provides a multimedia and interactive platform for everyone interested in electronics.

From professionals passionate about their work to enthusiasts with professional ambitions.

From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment.

Analogue and digital; practical and theoretical; software and hardware.

English
German
Dutch
French
Chinese



Italian
Spanish
Swedish
Finnish

Volume 34, Number 381, September 2008

ISSN 1757-0875

Elektor aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Publishers: Elektor International Media, Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447 www.elektor.com

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription.

Elektor is published 11 times a year with a double issue for July & August.

Elektor is also published in French, Spanish, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor:
Wisse Hettinga (w.hettinga@elektor.nl)

Editor: Jan Buiting (editor@elektor.com)

International editorial staff: Harry Baggen, Thijs Beckers, Ernst Krempelsauer, Jens Nickel, Guy Raedersdorf.

Design staff: Antoine Authier (Head), Ton Giesberts, Luc Lemmens, Daniel Rodrigues, Jan Visser, Christian Vossen

Editorial secretariat: Hedwig Hennekens (secretariaat@elektor.nl)

Graphic design / DTP: Giel Dols, Mart Schroijen

Managing Director / Publisher: Paul Snakkers

Marketing: Carlo van Nistelrooy

Customer Services: Anouska van Ginkel

Subscriptions: Elektor International Media, Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447
Internet: www.elektor.com

Masterclass High-End Valve Amplifiers



➔ Specifically for audio designers,
audiophiles, DIY enthusiasts etc.

In this Masterclass Menno van der Veen will examine the predictability and perceptibility of the specifications of valve amplifiers. Covered are models that allow the characteristics of valve amplifiers to be explored up to the limits of the audible domain from 20 Hz to 20 kHz. This then leads to the minimum stability requirements that the amplifier has to satisfy. The coupling between output valves and output transformer are also modelled. This gives new insight into a unique type of distortion: Dynamic Damping Factor Distortion (DDFD). Negative feedback is often used in amplifiers. What is the optimum and what are the audible consequences? The correct amplification of micro details is explained, based on new research, and new models about this are presented.



events

Menno van der Veen, Msc

Leading designer of valve amplifiers and output transformers

Programme:

Reception and registration (9.30)

Preamplifiers: equivalent schematics, limits in the frequency domain

Power amplifiers: modelling of class A to B, interaction of the specifications for OPTs and frequency range and damping factor

Lunch (12.15-12.45)

Negative feedback: how negative feedback can be done right, remarkable experiments in "the project"

Output transformer: limits and possibilities for the output transformer

Discussion and end (3.30)

The course fees are £ 160.00 (Including handout, certificate and lunch)

Subscribers to Elektor are entitled to 5% discount!

Date: Saturday 4 October 2008

Location: Birmingham City University

Time: From 10am to 3.30pm

REGISTER NOW!
Places are strictly limited.

More info and registration at www.elektor.com/events

Email: subscriptions@elektor.com

Rates and terms are given on the Subscription Order Form

Head Office: Elektor International Media b.v.

P.O. Box 11 NL-6114-ZG Susteren The Netherlands
Telephone: (+31) 46 4389444, Fax: (+31) 46 4370161

Distribution: Seymour, 2 East Poultry Street, London EC1A, England
Telephone: +44 207 429 4073

UK Advertising: Huson International Media, Cambridge House,
Gogmore Lane, Chertsey, Surrey KT16 9AP, England.
Telephone: +44 1932 564999, Fax: +44 1932 564998

Email: p.brady@husonmedia.com

Internet: www.husonmedia.com

Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Elektor International Media b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning or recording, in whole or in part without prior written permission from the Publisher. Such written permission must also be obtained before any part of this

publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publisher to alter the text and design, and to use the contents in other Elektor International Media publications and activities. The Publisher cannot guarantee to return any material submitted to them.

Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions excluded.

© Elektor International Media b.v. 2008

Printed in the Netherlands

Age, technology and education

Dear Editor — in response to the quite extensive article ‘UK University Courses for Electronics & Electrical Engineering’ in the February 2008 issue of *Elektron*, and recognising that the problem is not exclusive to the UK, I’d like to present the subject with a slightly different perspective: what kind of education shall the University bestow on the ‘new students’? Although a learning curve is always related to the complexity of the subject matter, fields like electronics, communications or computers have an added difficulty; the technology advances do not agree very well with unstructured or occasional study. In fact, age is a difficulty which will influence more the newcomers or new candidates to a job. As an example of applied mobile communications, let’s look at a third generation mobile phone (3G). From project design right up to manufacturing, just how many disciplines are involved?

Of course nobody can be an expert covering everything from the functional architecture right up to the case design and ergonomic matters, although the team leader should have clear ideas about such vastly different subjects as VLSI or camera lenses. He or she will be supported by an extensive group of experts for each main part, whether a power supply controller, a multilayer PCB or the battery to be used. We can move the problem to another layer, allowing the project leader to get support from the product supplier, as is often the case, but then he or she forfeits freedom of choice and time. Consequently it is often decided to mix in-house expertise, supplier support and external sources to carry out well defined tasks.

It’s often heard that “there is nothing new today”; the latest mobile phone being no more than the previous one enriched with better features or implementing new technologies, more frequently some ‘feature’ to keep up with the competition. Hence brand new products need know-how, which basically is the cumulative experience of successful projects, innovation



and creativity. Innovation and creativity often goes on account of newcomers, graduated or not. Not being stuck in past, they just have ideas — maybe old concepts, but new for them!

The screening has to be done by experienced experts, but a question arises, are they prepared to understand a brilliant idea? The notion of ‘education and then a job’ is not motivating for creative people, they want to be part of the action. Today, technologies advance much faster than any practical application, so insisting on education followed by more education without presenting an opportunity to experiment in practice, causes many students to either drop out or go for a

short time graduation path. New students must have deep knowledge of the fundamentals related to any technology or field of application. A graduate in history or languages doing an MA on Computer Science will know a lot of ‘names’ but most probably still not understand why the work of Jack Kilby was so important for today’s degree of integration in ICs.

The panorama is not exclusive to electronics, communications or computers. If we think about biotech, nanotech or any other emergent technologies the situation is worse. For years, scientists, universities and private labs worked hard on nanotube growth — today we can buy such tools off the shelf; that’s the reality. After 20 years of R&D and lump sums invested, nanotechnology today is a well established industry, and the return will be high.


With real-life needs and applications often neglected as opposed to pure technology research, I wonder if the industry will be able to cope with its need to find sufficient skilled professionals in the near future. It’s time for the industry, the universities and private labs to get together and start reflecting. The European countries are too hierarchically minded for some matters, and too tolerant for others. But we are not alone in the competition.

Rui Figueiredo (Portugal)

The OC171 Mystery (solved) (1)

Dear Jan — referring to your article in the Summer Circuits 2008 edition I would question the ‘solved’ part of the title as the cause of the growth of the fibres is still subject to speculation in the article.

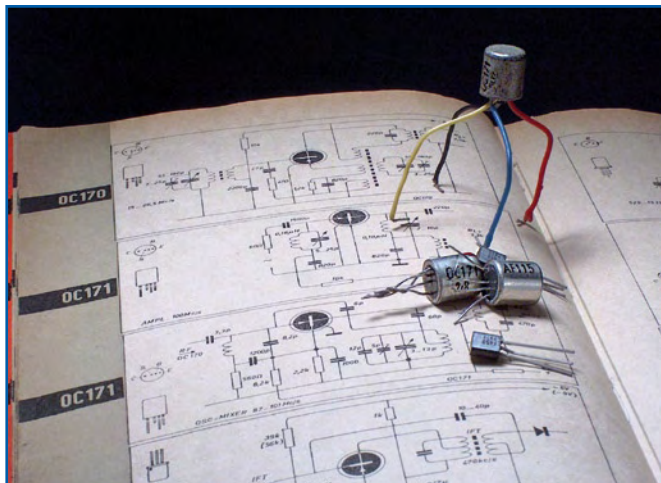I was involved in the investigation of similar sounding metallic fibre growth inside a metal can, in my case it was a VCO module, eventually causing failure by shorting to the circuit inside the can. The fibres were shown to be crystalline tin and



grew usually straight (though some were curly) from the can out into the air space at various angles. The cause was traced to the can being made of tin plated brass and the growth of such fibres is apparently a well known phenomenon. These fibres grow more quickly in a cold environment which matched our experience with this VCO.

The article does not state the composition of the OC171 metal can, but there are pictures and a video here

www.vintage-radio.info/whiskers/ for a similar effect in an AF117 which states that the can is tin plated and that the whiskers are tin.

It would seem that tin plating is not such a good idea when applied to enclosures for electronic circuits!

Jim Thurgood (UK)

Thanks for the response to my article Jim — it seems to have generated an unexpected amount of feedback. Also thanks for the interesting link. I am also grateful to Andy Emmerston for his advice that the history of electronics contains a few mistakes and it is useful to write about them!

For more scientifically based theories, you might want to have a look at www.springerlink.com/content/v77jl33102116274/ which indicates that the cause of this dendritic growth problem may be undercooling, but I am not sufficiently well informed to know how relevant this article is. This may be related also:

www.nature.com/nature/journal/v216/n5115/abs/216574b0.html I agree that the exact nature of the microscopic hair growth inside these transistors is still a matter of debate or research but in the title I was referring to the mystery of circuits suddenly failing after 25-40 years, and that has been solved as far as I am concerned.

The OC171 Mystery (solved) (2)

Hi Elektor — thanks for an interesting Summer Circuits edition; lots of nice, small projects off the beaten track.

By the way, those funny short-circuits in the old OC trannies may be 'tin whiskers' i.e. e growth of tin hairs from tinned surfaces. A nasty problem with PCB tracks, too! Lots of information out there on the web if you Google for tin + whisker.

Jan Philipp Wuesten (AskJanFirst) (Germany)

That's right Jan Philipp, 'whisker' is a correct term to use in this case.

The OC171 Mystery (solved) (3)

Dear Editor — I just received my July/August 2008 edition and read the above article with interest. It mentions 'hairs' growing. IMHO these are whiskers, i.e., needle-shaped monocrystals growing out of layers separated by galvanic or pyrolytic effects.

The hairs are just a few micrometers thick and may be removed by a current surge (alas, this may end transistor's life).

I was curious to read that several theories had been created around this effect, realizing that 'whiskers' formation is a well known problem.

H. Kobow (Germany)

Thank you for your response to my article, which also appeared in translation in the German Elektor. Whisker growth is indeed a correct term to describe the effects. Although the theories behind pyrolytic growth and dendrite formation from tin and metal junctions and compounds have been covered by advanced metallurgy for many years, I can only assume that the makers of the OC170/171 transistors had no way of knowing in the early 1960s. After all, it takes about 25-40 years for the hairs to become long enough to cause short-circuits, the period well exceeding the useful lifetime of a transistor radio. As I wrote, 'zapping' the whiskers is not a permanent solution.

A stable audio signal (2)

Dear Sir — this refers to the request of Mr. Monteban for a stable a.f. signal source for audio measurements (Mailbox, June 2008). A construction project called 'Spot Sinewave Generator' was published in the May and June 1985 issues of *Elektor*, which hopefully will cover Mr. Monteban's requirements.

Darius Toorkey (India)

Thanks for helping Mr. Monteban, Darius.



Marconi rebranding of FUP1D

Hi Jan — Retronics is always a very interesting section. I have a good few pieces of test equipment of that age and older myself. I may start writing about them when I retire next year! Referring to the June 2008 instalment I have the FUP1D, with the additional UHF band. It is branded 'MI', which stands for Marconi Instruments and would originate in the UK. It is identical to your photo but is labelled TF2950, which was the Marconi series of numbers for test equipment.

Ed Dinning (UK)

Many thanks Ed an looking forward to seeing some articles from you. Thanks also to Ludo ON4AIO from Belgium who mailed me a copy of the TF2950 product information sheet.

Good old 8051

Dear Editor — I still see a lot of projects based on some 8051 derivative. And almost everybody uses some C compiler or assembler.

For those who like programming in Pascal here is Turbo51 — a free Pascal compiler for the 8051 family of microcontrollers. It's found at <http://turbo51.com> and features a fast single pass optimizing compiler, Borland Turbo Pascal 7 syntax, full floating point support, mixed Pascal and assembler programming, full use of register banks, advanced multi-pass optimizer, smart linker, generates com-

pact high quality code, output formats include binary, Intel HEX and assembler source. I wrote Turbo51 because I like Pascal programming language, still work a lot with 8051 and couldn't find any good Pascal compiler for 8051. I believe that sooner or later there will be some project published in your magazine that will use Turbo51.

Igor Funa

Corrections & Updates

Portable Thermometer

July & August 2008, p. 19, ref. 080418-1

The type number shown in the circuit diagram for IC5 should be: PIC16F684.

MailBox Terms

- Publication of reader's correspondence is at the discretion of the Editor.
 - Viewpoints expressed by correspondents are not necessarily those of the Editor or Publisher.
 - Correspondence may be translated or edited for length, clarity and style.
- When replying to Mailbox correspondence, please quote Issue number.
- Please send your MailBox correspondence to:

editor@elektor.com or
Elektor, The Editor,
1000 Great West Road,
Brenford TW8 9HH, England.

New 2 MB & 8 MB nvSRAMs from Cypress

Cypress Semiconductor Corp. recently introduced 2-Mbit and 8-Mbit non-volatile static random access memories (nvSRAMs), extending their nvSRAM portfolio from 16 kbit to 8 Mbit. The new devices feature access times as low as 20 ns, infinite read, write and recall cycles, and 20-year data retention. They offer the best solution for applications requiring continuous high-speed writing of data and absolute non-volatile data security. Systems requiring nvSRAM functionality include servers, RAID applications, harsh-environment industrial controls, automotive, medical and data communications.

The 2-Mbit nvSRAM and CY14B108 8-Mbit nvSRAM are ROHS-compli-



ant and directly replace SRAM, battery-backed SRAM, EPROM and EEPROM devices, offering reliable non-volatile data storage with-

out batteries. Data transfers from the SRAM to the device's non-volatile elements take place automatically at power down. On power

up, data is restored to the SRAM from the non-volatile memory. Both operations are also available under software control. The new nvSRAMs are manufactured on Cypress's S8(tm) 0.13-micron SONOS (Silicon Oxide Nitride Oxide Silicon) embedded non-volatile memory technology, enabling greater densities and improved access times and performance.

The new devices have an available Real Time Clock feature that combines the industry's lowest standby oscillator current with the highest performance integrated memory, enabling event time-stamping supported by non-volatile memory.

www.cypress.com/NVM

(080624-1)

Elektor E-vent: Study Trip to China

Elektor's second Study Trip to China is planned for 9-18 November 2008.

We will visit the China Electronics Fair in Shanghai with an exhibition area of 60,000 m² representing the electronics industrial chain set up for one-stop purchasing of high-end components. This authoritative electronics show is the only one with full support from the Chinese Ministry of Information Industry and Ministry of Commerce. It was classed 'A' exhibition in 2003 by the Ministry of Commerce.

Also on the programme is a visit



to the largest electronics-packed street in Beijing and/or Shanghai. The shops, often 4 to 5 floors tall, are choc-a-bloc with components, microcontrollers, experimenter's boards, modules, electric plugs, LEDs in assorted colours, LCDs and much more. Everything an electron-



ics enthusiast can dream up can be found here!

A business conference is also organized as part of the tour, providing an insight into trade opportunities in China.

Of course there is again room for culture like the Forbidden City, Tiananmen Square, the Great Wall, the Maglev train, and more.

The price of this all-inclusive tour is € 3,995 (plus VAT) per person.

If you are interested in joining us in November, please register now on www.elektor.com and you will receive more detailed information.

ZigBee® network module

Radiocrafts AS expand their product line with a compact ZigBee Network Module (ZNM) for use in ZigBee based mesh networks. The ZNM module offers the complete ZigBee network protocol in a small module with an easy to use API interface. By using the new ZNM module, ZigBee applications can be built with minimum effort, reducing time to market.


The RC2300-ZNM module is a compact surface-mounted high performance module measuring only 12.7x25.4x2.5 mm including EMC shielding and integrated

antenna. The module is delivered on tape and reel for volume production.

The module is very easy to use having a UART or SPI interface for serial communication and configuration. The ZigBee application runs in any external controller, communicating with the module by an easy-to-use API. With only 10 API calls, a complete application can be made. The new module supports all features of the ZigBee 2006 standard.

The RC2300-ZNM module is pre-

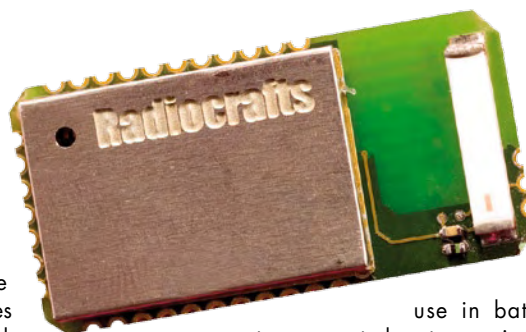certified for operation under the European, FCC and ARIB radio regulations for license-free use. It operates at 16 channels in the 2.45 GHz frequency band. When used with quarter-wave antennas a line-of-sight range of 250 metres can be achieved. Indoor range is typically 10-30 metres. The module is designed for




use in battery operated systems using sleep mode with less than 1 µA. The module, Demo Kits and PC development tools are available now.

www.radiocrafts.com

(080624-III)

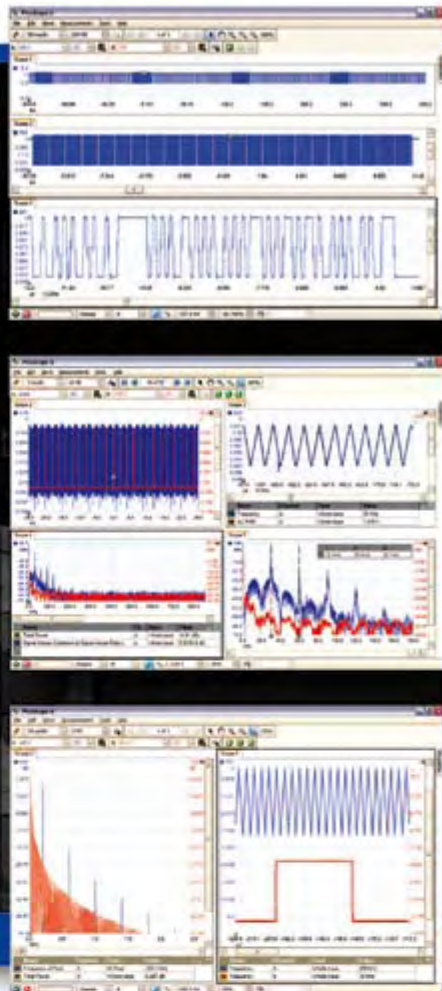USB Connected High Speed PC Oscilloscopes



5000 SERIES PicoScope 5000 Series

The No Compromise PC Oscilloscopes

With class-leading bandwidth, sampling rate, memory depth and an array of advanced high-end features, the PicoScope 5000 PC Oscilloscopes give you the features and performance you need without any compromise.

250 MHz bandwidth
1 GS/s real-time sample rate
128 megasample record length

Advanced Triggers

In addition to the standard triggers the PicoScope 5000 series comes as standard with pulse width, window, dropout, delay, and logic level triggering.

250 MHz Spectrum Analyser High-speed USB 2.0 Connection

Automatic Measurements

Arbitrary Waveform Generator

Define your own waveforms or select from 8 predefined signals with the 12 bit, 125 MS/s arbitrary waveform generator.

Waveform Playback Tool

PicoScope software now allows you to go back, review, and analyse up to 1000 captures within its waveform playback tool.

pico[®]
Technology

3000 SERIES The PicoScope 3000 Series of oscilloscopes from Pico Technology includes general purpose and high resolution models: With 12 bit resolution and 1% accuracy, the 10MHz PicoScope 3424 is able to detect changes as small as 0.024% (244ppm) – making it the ideal 4-channel oscilloscope for analog design and analysis. The higher speed 8 bit models in the PicoScope 3000 series feature sampling rates up to 200MS/s and up to 1 MS/s record lengths for general purpose and portable applications.



2000 SERIES The PicoScope 2000 series oscilloscopes offer single and dual channel units that offer highly portable/low cost solutions to general purpose testing. The award winning 25MHz handheld PicoScope 2105 fits comfortably into the palm of your hand yet still includes the powerful features found in larger oscilloscopes.



VISIT www.picotech.com/scope485

to check out our full line of PC-based instruments or call **01480 396 395** for information and a product catalogue

Multinational Micromouse championship showcases a new generation of robotic talent

Teams from Singapore, India, Iran and the Netherlands joined competitors from across the UK, at this summer's UK Micromouse robotics championship. Organised by Birmingham City University, the event saw over 50 mini robots competing in maze-solving, wall-following, drag racing and mini-sumo challenges.

The senior maze-solving final featured a tense battle between Derek Hall, the 2007 champion, and his regular UK Micromouse adversary, Peter Harrison. The maze-solver challenge sees the autonomous mini-robot 'mice', racing unaided to the centre of a specially constructed maze over a series of timed runs. Derek successfully defended his title, with his 'MouseX' and 'MouseX2' robots claiming the top two places, registering the competition's fastest run-time of 6.98 seconds.

A new generation of robotic talent demonstrated their skills in

the UK Micromouse categories for junior and schools competitors. The robotics club from Singapore's Woodlands Ring Secondary School dominated the top places

course in a time of 2.13 seconds. The honours in the wall-following and line-following categories were shared by the UK's John Hampden Grammar School and Hillcrest

nearly 30 years, with similar events also taking place in the USA and across East Asia. The original aim of stimulating interest in the then fledgling fields of software and electronics is now more relevant than ever. The increasing prevalence of these technologies in industry and society has led to widely-acknowledged skills shortages in these areas.



Competitors gather at the end of the event to compare robots.

UK Micromouse organiser, Birmingham City University's Dr Tony Wilcox says: "It was really encouraging to see this new generation of competitors in action. Mini-robots are a great way to get 'hands-on' and explore software and electronics technologies, which is the most effective way to spark new interest in these areas."

Further details about the event and building mini-robots can also be found at www.tic.ac.uk/micromouse.

in the schools drag racing challenge. Their fastest stepper-motor powered challenger completed the

Community School. Micromouse championships have been held annually in the UK for


RS Components for energy efficient products

RS Components recently launched its Solutions for Energy Efficiency range, allowing electronic design engineers to view and choose from over 1,600 of the best-in-class power-efficiency products, encompassing 40 technologies from 60 leading manufacturers. All products are available direct from rswww.com/electronics, enabling the speedy creation of energy efficient designs.

Product highlights include:

Texas Instruments

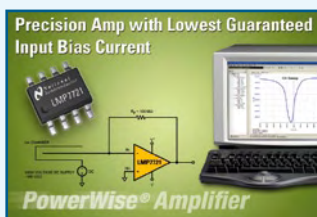- TPS63000 voltage regulator for extremely low power applications such as PDAs, MP3 players and LEDs
- MSP430 ultra low power microcontroller range optimised to deliver extended battery life in portable applications
- CC2520 low power Zigbee transceiver and development kit for RF engineers designing wireless networks in applica-



tions such as automatic meter reading.

National Semiconductor

NI's PowerWise range of energy efficient products includes a wide selection of products from amplifiers that guarantee the lowest input bias current in the industry to data-converters that consume 30% less power than competitive devices.

NXP



GreenChip ICs for power supplies, designed specifically for Laptop computers and LDC TVs, reducing no-load standby power consumption to 0.2-0.3W.

RS Components

Ultra-miniature switch mode power supply units that provide no-load power consumption of <0.5W.

Integral to the range are a number




of energy harvesting products to exploit natural, renewable energy sources. These include wind and solar power products together with their associated regulators and batteries. Also featured are EnOcean wireless control, switching and sensing products that don't need external power or batteries as all the power is generated internally. Passives are also available including ultra compact power inductors from Würth.

A selection of peripheral devices complements the entire offering with various wireless and display options for the engineer to choose from. RS has also selected the Golden Dragon LED range from Osram, one of the market leaders in solid state lighting solutions.

<http://rswww.com/electronics>

(080624-11)

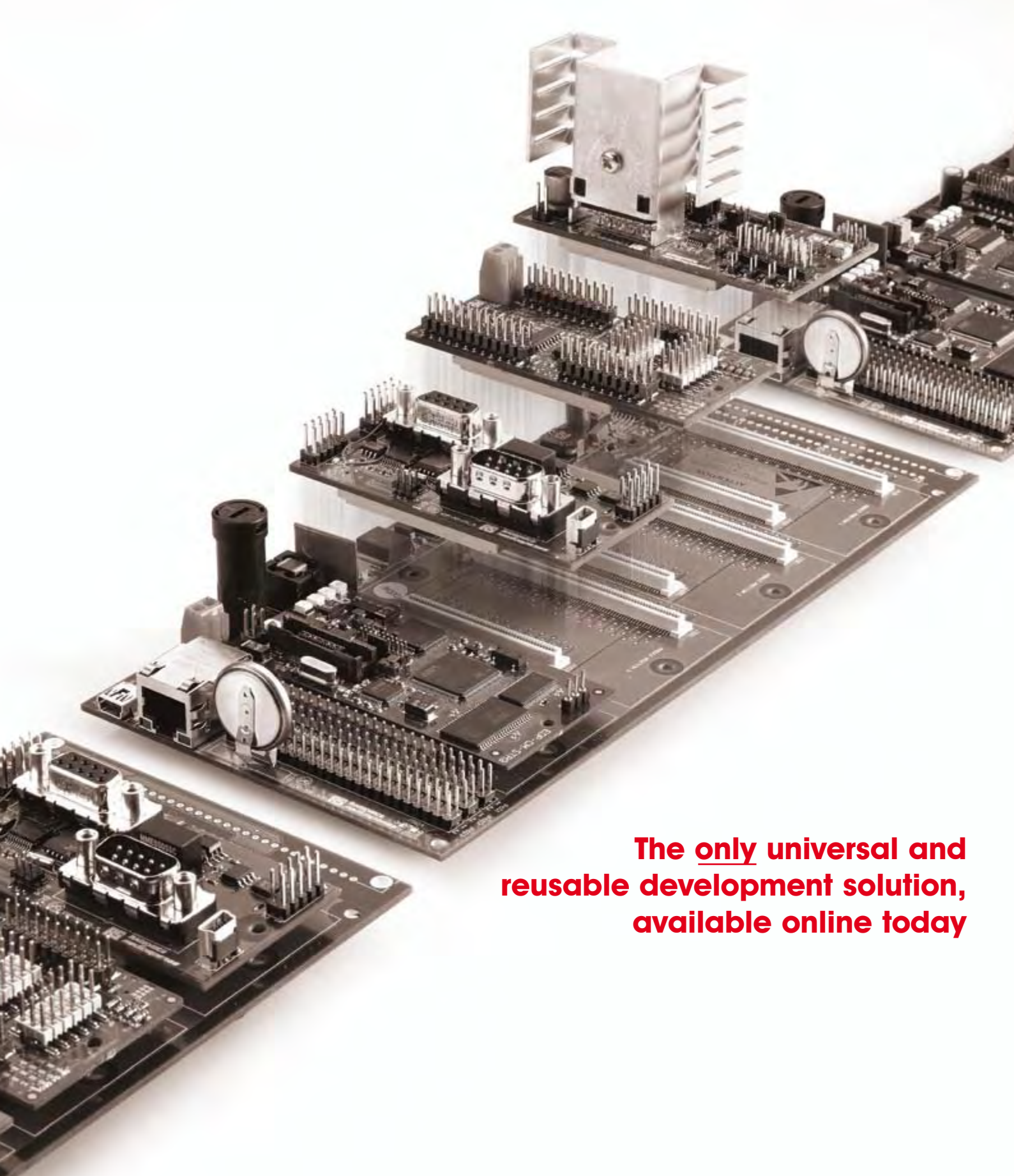

**The only universal and
reusable development solution,
available online today**

**RS EMBEDDED
DEVELOPMENT
PLATFORM**

rswww.com/electronics



Elektor Workshop: Graphical Programming of Microcontrollers using Flowcode

Date: 4 October 2008, from 09.00 – 16.00 hours.

Location: Birmingham City University, Technology Innovation Centre, Millennium Point, Curzon Street, Birmingham B4 7XG.

Lecture and workshop presenters:

Dr. Nick Holden BSc(Hons) PhD CEng MIET, Senior Lecturer in the Centre for Electronics and Software, Technology Innovation Centre, Birmingham City University.

Mr. Parmjit Chima BEng PgDip, Manager, Centre for Electronics and Software, Technology Innovation Centre, Birmingham City University.

The purpose of this one-day course is to program and apply PIC microcontrollers in an accessible and practical way.

The participants will learn how to use Flowcode to exercise some of the functionality



Dr. Nick Holden

of these modern microcontrollers using peripherals such as timers, counters, digital port I/O, A/D and USART, with polling and interrupt techniques.

The course will use the E-blocks hardware with one of the common 40-pin PIC microcontrollers. The graphical programming of the microcontroller is done with



Mr. Parmjit Chima

the revolutionary new software Flowcode version 3. The knowledge gained can also be applied to other 8-bit microcontrollers such as the AVR from Atmel.

The participant will at the end of the day be able to build embedded systems with analogue values and switches as inputs and output

via LCD and LEDs.

This workshop is also a very thorough preparation for programming these microcontrollers in C.

Prerequisites:

- some electronics skills
- digital technologies
- computer proficiency (Windows)

The course fee is £ 160, including lunch and certificate.

Every participant also receives the CD Flowcode software version 3 (value £ 48.30). Elektor subscribers are entitled to a 5% discount.

Note: the number of seats is limited. There is space for only 16 participants! Be quick to register, places are strictly limited.

Programme and registration on www.elektor.com

NI ELVIS II offers USB Plug and Play, full NI Multisim Integration

National Instruments has announced NI ELVIS II, the latest version of the design and prototyping platform that educators worldwide have adopted for hands-on, project-based learning. Based on the powerful LabVIEW graphical system design software, NI ELVIS II gives educators 12 new USB plug-and-play instruments and complete integration with Multisim 10.1 software for SPICE simulation to simplify the teaching of circuit design. In addition, educators can use NI ELVIS II with a suite of third-party boards and curriculum resources to teach control design, telecommunications and microcontroller concepts.

The new NI ELVIS II includes backward compatibility with the previous version, laboratory-friendly features such as USB plug-and-play connectivity and a smaller form factor to simplify setup and lab maintenance. NI ELVIS II also features 12 of the most commonly used instruments in engineering and science laboratories, including an oscilloscope, function genera-

tor, variable power supply and isolated digital multimeter, in one low-cost, easy-to-use platform. Because NI ELVIS II is based on LabVIEW, educators can easily customise the

software, leading SPICE simulation and schematic capture software. Educators and students can use Multisim 10.1 with NI ELVIS II to seamlessly switch between simu-

lating and acquired data, overlay simulated and measured data in the same instrument and use a single platform when simulating or testing to provide a holistic view of the circuit design process – from designing and prototyping to deployment. Multisim also includes other pedagogically relevant features such as custom in-circuit quizzes and a 3-D NI ELVIS II feature that students can use to wire their circuits on a virtual replica of the system, increasing efficiency in the laboratory.



12 instruments or create their own using the provided source code for the instruments.

NI ELVIS II also features complete integration with new Multisim 10.1

lated and acquired data, overlay simulated and measured data in the same instrument and use a single platform when simulating or testing to provide a holistic view of

With an extensive network of plug-in boards from leading vendors in education and industry, educators can use NI ELVIS II to teach a variety of classes, from circuit design, measurement and instrumentation to design, telecommunications and embedded/microcontroller design. Quanser provides three different plants for teaching control design and mechatronics with NI ELVIS II and LabVIEW. Emona Instruments introduced the DATEx telecommunications trainer to teach telecommunications concepts using NI ELVIS II and LabVIEW.

Additionally, Freescale Semiconductor's Microcontroller Student Learning Kits with flexible 8-, 16-

and 32-bit microcontroller modules is fully compatible with NI ELVIS II and leverages the 12 new integrated instruments to teach embedded and microcontroller design. National Instruments is committed to enhancing engineering and sci-

ence education worldwide by providing educators and students with powerful graphical system design software and modular hardware to connect the curriculum with the real world. Professors and students benefit from powerful, professional

tools such as NI LabVIEW graphical development software, which helps students visualise and implement engineering concepts. The integration of LabVIEW in the classroom creates an effective, dynamic learning environment –

from LEGO® MINDSTORMS® NXT in primary schools to research laboratories in universities.

www.ni.com/academic
www.ni.com/nielvis

(080264-1V)

Industry's most secure WiFi embedded networking module

Alpha Micro Components has added the MatchPort b/g Pro to its extensive portfolio of networking products. The MatchPort b/g Pro allows a wide range of machines to be managed and controlled remotely over a network with an added level of security.

MatchPort b/g Pro is claimed to be the industry's most secure embedded WiFi networking module designed for applications that require the safest and most reliable technology for secure data transfer in sensitive applications such as medical records and government data transmissions and financial transactions.

Security features include:

- IEEE 802.11i compliant radio with AES-CCMP (Advanced Encryption Standard-Counter Mode with Cipher Block Chaining Message Authentication Code Protocol) and TKIP (Temporal Key Integrity Protocol)
- Complete suite of 802.1x EAP (Extensible Authentication Protocols) including EAP-TLS (Transport Layer Security), EAP-TTLS (Tunneled Transport Layer Security), PEAP (Open standard from Cisco Systems, Microsoft and RSA Security), LEAP (Lightweight Extensible Authentication Protocol)
- End-to-end TLS/SSL 3.0 (Secure Sockets Layer) and SSH (Secure Shell) tunneling
- End-to-end AES (Advanced Encryption Standard) 128-bit encrypted tunneling



Encryption Standard) 128-bit encrypted tunneling

MatchPort b/g Pro handles the most computationally demand-

ing or data intensive applications effortlessly with a 32-bit, 159 MIPS (Dhrystone 2.1) 166 MHz processor. With 8 MB of SDRAM and 8 MB flash, it provides enough memory capacity for OEM customisation, loading web pages, and data 'store and forward' applications. It features two serial input ports with 230 kbps data rate capability, seven control pins (CP/GPIO), and a wide operational temperature range of -40° to 70°C, with the option to operate up to 85°C with lower MTBF.

www.alphamicro.net

(080624-V)

Elektor Workshop: PIC Programming using 'C' — hands-on for beginners

Date: 4 October 2008, from 09.00 – 16.00 hours.

Location: Birmingham City University, Technology Innovation Centre, Millennium Point, Curzon Street, Birmingham B4 7XG.

Lecture and workshop presenters:

Dr. Anthony Wilcox GRIC PhD CEng MIET, Consultant and Principal Lecturer, Centre for Electronics and Software, Technology Innovation Centre, Birmingham City University.

Mr Andrew Hill BSc MIET, Consultant and Principal Lecturer, Technology Innovation Centre, Birmingham City University.

The main goal of this one-day course is to provide an introduction to the programming of PIC microcontrollers in the C programming language. The course is mainly aimed at par-



Dr. Anthony Wilcox



Mr. Andrew Hill

ticipants who are unfamiliar with the C programming language, but who would like to learn to use it in an embedded environment. The participant will be introduced to those aspects of the C language that are most relevant to the programming of microcontrollers. The

hardware used in the course consists of E-blocks.

Course objectives:

- The participant can make a simple C program
- The participant can program a PIC-microcontroller in C

Prerequisites:

- Some experience in programming is recommended, such as (Visual) Basic, Pascal, Assembly or another language. No prior knowledge of C is expected.
- Some familiarity with electronics, digital technology and computer proficiency (Windows)

The course fee is £ 160, including lunch and certificate.

Every participant also receives the CD C for PIC Microcontrollers (value £ 48.30). Elektor subscribers are entitled to a 5% discount.

Note: the number of seats is limited. There is space for only 16 participants! Be quick to register, places are strictly limited.

Programme and registration on www.elektor.com

Altium joins European fight against piracy

Altium Limited, the electronics design industry's leading developer of unified electronic product development solutions, has extended its Business Software Alliance (BSA) membership to include the Europe, Middle East and Africa (EMEA) region. The move will strengthen Altium's IP protection and complement its anti-piracy movements in China and the rest of Asia. The move will see Altium join

BSA's efforts to crack down on the \$US48 billion black hole caused by piracy – with over 40% of these losses stemming from the EMEA region alone. Many European countries have shown an overall decline in piracy rates since 2003, however characteristics vary with each country and market. For example, Greece which has a piracy rate of 58% experienced industry losses of \$198

million last year, while the United Kingdom which has a piracy rate of 26% — one of the lowest in the EMEA region — experienced losses of more than \$1.8 billion. But software piracy not only has a detrimental effect on the software industry, it also poses a threat to the IT industry, ultimately affecting local job opportunities and investments into research and development.

The EMEA region is a very large market for Altium, making up more than 33% of total sales in the financial year ending June 30, 2007. Altium's increased support for the BSA is a positive step forward, helping Altium to protect its IP and secure future innovations in electronics design.

www.altium.com

(080624-VI)


Motor Mount & Wheel kit

It's time to give your robot the mobility and style it deserves with the new Motor Mount and Wheel Kit with position controller from Parallax. Powerful 12 VDC, 150 rpm motors are combined with precision machined 6061 aluminium hardware to provide enough power, strength, and beauty to make other robots jealous.

Conveniently positioned screw holes in the bearing block make mounting this kit a breeze, and the included 6-inch (15 cm) pneumatic rubber tires perform

well on a variety of smooth or rugged terrains.

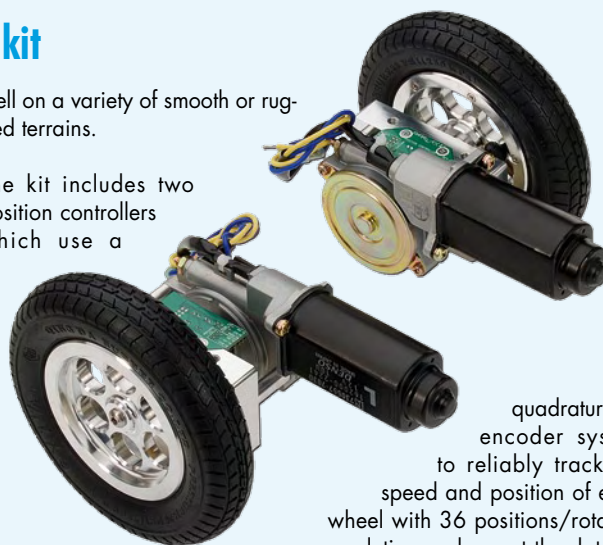The kit includes two position controllers which use a



quadrature encoder system to reliably track the speed and position of each wheel with 36 positions/rotation resolution and report the data on

command via a 19.2 kbps serial bus. The position controllers can also be interfaced with HB-25 motor controllers (sold separately) to automatically provide user-definable smooth speed ramping and accurate position control, which frees up the main processor to handle more important tasks.

www.Parallax.com

(080624-VIII)

Turner, Constable and a Lascar data logger

As well as exhibiting works by great British artists such as J.M.W. Turner and John Constable, the Bury Art Gallery, Museum and Archive also contains a number of Lascar's EL-USB-2 temperature and humidity data loggers. And whilst a data logger won't pull the crowds in like a Turner masterpiece, it will do its bit to ensure these works are kept in the best condition for generations to come.

Alison Green, Museum Assistant explains, "It's taken over a hundred years to build up this collection and its value, historically and socially, is enormous. It's very important we monitor the environment in which the collections are housed. Exposure to extremes of heat, cold, aridity or humidity can cause textiles, canvas, wood and other materials to quickly deteriorate."



A search on the internet turned up a product by Lascar Electronics — a data logger — designed to measure and record both temperature and humidity over a specified period of time. "This is

a great product", says Alison. "I can simply plug it into my computer's USB port, give it a name, set some alarms and choose a sampling rate. When it's programmed, it's small enough that I can pop it

back into a case without it taking over the display and away it goes measuring temperature and humidity levels. When the logger is full of data or I see an alarm level has been reached because its red alarm light is flashing, I take it back to the computer and download all the recordings to see what environment our exhibits have been exposed to. It's not just in the best interest of the exhibits — we're a publicly funded organization and we have to actually prove we're looking after everything in the museum."

The EL-USB-2 is available immediately directly from Lascar Electronics at a price of £ 49.95. Discounts for quantity are available upon request.

www.lascarelectronics.com

(080624-VII)

EasyPIC5 C Starter Pack—everything needed to start developing PIC projects in C for just £189




The EasyPIC5 C Starter Pack contains everything needed to start learning about and developing with PIC microcontrollers using the C programming language. The package contains the popular EasyPIC5 development board, a full version of MikroElektronika's powerful mikroC compiler, USB and serial cables, blue backlit 16x2 character and 128x64 graphic LCDs, touch-screen overlay for graphic LCD, DS1820 temperature sensor and a 40-pin enhanced Flash PIC16F887 microcontroller—all for just £189.

The EasyPIC5 C Starter Pack is well-suited to beginners and experienced developers alike and comes with high-quality printed documentation and a large number of easy-to-understand example programs for a number of PIC microcontrollers.

The **EasyPIC5** supplied in the starter pack is a full-featured development board for PIC10F, 12F, 16F and 18F microcontrollers in 8, 14, 18, 20, 28 and 40-pin packages. The EasyPIC5 incorporates an on-board USB-based PIC programmer and in-circuit debugger as well as a useful selection of built-in I/O devices such as LEDs, switches, 7-segment displays, potentiometers, RS-232 interface, PS/2 and USB connectors and provision for fitting of the included LCD displays, touch-screen and DS1820 temperature sensor. What's more, all of the PIC's input/output lines are available for connection to your own circuits or to any of our huge range of low-cost optional add-on boards such as Ethernet, RS-485, CAN, LIN, IrDA and RFID communications, EEPROM, SD/MMC and Compact Flash storage, 12-bit A/D and D/A, and many useful interfacing and prototyping boards.



Supplied in the EasyPIC5 C Starter Pack is a full version of MikroElektronika's **mikroC**, a powerful integrated development environment and C compiler for PIC12, PIC16 and PIC18 microcontrollers. With its built-in user-friendly features, mikroC makes developing code for PICs easier than ever. When used in conjunction with the EasyPIC5 development board, mikroC provides full in-circuit debugging capabilities. mikroC also provides a library of ready-written routines that provide support for all of the EasyPIC5's on-board I/O devices and optional add-on boards. This enables programs to be quickly constructed even when working with advanced features such as CAN, Ethernet and USB communications, character and graphic LCDs and touch-screen, and EEPROM, MMC/SD and Compact Flash data storage. mikroC also incorporates useful tools such as LCD custom character generator, GLCD bitmap generator, USART, HID and UDP terminals and 7-segment display decoder.

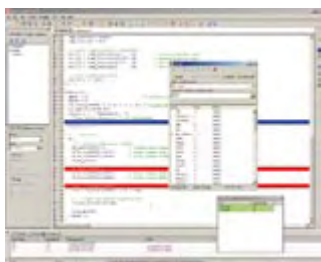

EasyPIC5 BASIC Starter Pack and **EasyPIC5 Pascal Starter Pack** also available at £149 each. Similar starter packs also available for 8051, AVR and dsPIC—please see our website at www.paltronix.com for prices and full details.

Get an oscilloscope, logic analyser and much more with the PoScope USB-based Instrument for only £79



With a PoScope you get:

- Dual-channel oscilloscope
- Spectrum analyser
- Dual-channel chart recorder
- 16-channel logic analyser with UART, SPI, I2C and 1-wire serial bus protocol decoding
- 8-channel pattern generator
- Square-wave/PWM generator


This latest version of the popular PoScope is a must-have tool for those developing microcontroller-based projects or with a general electronics interest and provides the features of six instruments in one compact PC-based unit at an incredibly low price.

The PoScope connects to one of your desktop or laptop PC's USB interfaces (USB 1.1 or USB 2.0), is Windows XP and Vista compatible and comes with easy-to-use software.

The PoScope provides two BNC connectors for oscilloscope, spectrum analyser and chart recorder inputs and a 25-way female D-connector for logic analyser and pattern generator input/outputs. Supplied with USB connecting cable and software and manual on CD-ROM.

A PoScope Bundle is also available for £119, which additionally includes two high-quality oscilloscope probes and a logic analyser test lead and clip set.

The **dual-channel oscilloscope** provides voltage and frequency measurement, absolute, differential and external triggering, adjustable pre-trigger, marker measurements and filtering. Specifications include a 100Hz - 200kHz sampling rate, 1126 samples/channel (1 channel) or 563 samples/channel (2-channel) memory depth with pipe reading of 64k samples per channel, 10-bit resolution A/D and input voltages from -20 ~ +20V.

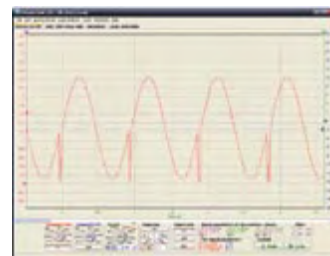

Dual-channel oscilloscope view

The **spectrum analyser** provides Hamming, Hanning, Blackman and Blackman-Harris window functions.

The **chart recorder** provides dual-channel recording at sampling rates from 0.01Hz ~ 200kHz with a maximum record time of 24 hours at Fs < 100Hz. A/D resolution and input voltage range are again 10-bit and -20 ~ +20V respectively.



Sixteen-channel logic analyser view

The **logic analyser** provides 16 channels (eight when pattern generator in use) with a sampling rate of 1kHz ~ 8MHz, internal and external clocking, versatile triggering and an input range of 0 ~ +5V. Memory depth ranges from 1544 bits/channel (Fs <= 1MHz) to 128 bits/channel (Fs <= 8MHz). Built-in **serial bus protocol decoding** facilitates the decoding of UART, SPI, I2C and 1-wire serial buses.

The **pattern generator** allows eight of the logic analyser's channels to be used to provide output waveforms from 1kHz ~ 1MHz with a memory depth of 1544 bits/channel and an output voltage of 0V for logic "0" and 3.3V for logic "1".



UART, SPI, I2C and 1-wire decoding view

The **PWM generator** provides a 7.8125kHz output with a 1 ~ 100% adjustable duty cycle. Square waves can also be output with a 50% duty cycle and an adjustable frequency ranging from 3.91kHz to 1MHz.

Please see our website at www.paltronix.com for further products including components, microcontroller development tools, prototyping aids, educational robot kits, test equipment and wireless communications products.

Pix-Cell GSM Controller

New product—the Pix-Cell is a stand-alone controller offering GSM/GPRS communications, three digital inputs, three 10-bit analogue inputs, SPDT relay output and RS-232 interface priced at £129.



ZeroPlus Logic Analysers

A range of powerful 16 and 32-channel logic analysers with advanced serial bus protocol decoding including CAN, LIN, USB, UART, SPI, I2C, 1-wire and more. With prices from only £125, there's a logic analyser in this range to suit all needs and budgets.



Universal Development System

The UNI-DS3 is a versatile microcontroller development system supporting PIC, dsPIC, 8051, AVR, ARM and PSoC devices with an extensive range of built-in I/O features and on-board USB programmer priced from £109.



The Thought Cursor

Brain-computer interfaces and how they work

Jens Nickel

Controlling a computer using the power of thought alone is less far-fetched than you might believe. The easy part is to measure precisely the tiny currents in the brain associated with thought processes; the hard part is to extract the thoughts from the morass of multi-channel EEG (electroencephalogram) data.

Research groups all over the world [1, 2, 3] are working on how to tease out useful control information from an intricately interdependent array of measured brain currents. One ultimate aim is to allow a patient to control a motor in a prosthetic limb using just a thought, allowing tetraplegic people to stand independently and go about their daily business more easily. It will be a few years before such systems are ready for widespread use, but they are already functioning in the laboratory.

Measuring, amplifying and digitising the tiny currents involved does not require special equipment. The job the researchers are tackling is to distil the multitude of sampled data channels down to a simple command, which requires plenty of processing power and some clever software algorithms.

The Berlin Brain-Computer Interface (BBCI) [1] is a cooperative project between the intelligent data analysis group at FIRST, part of the Fraunhofer Institute, the neurology clinic neurophysics group at Charité University Hospital, Berlin, and the Technical University of Berlin. The prestigious project is funded by the EU, by the DFG research foundation, and by the German government.


How it works

The BBCI uses the 'pre-movement' principle, whereby the patient must imagine themselves wanting to move a finger, hand or foot, in order to execute a command. The brain currents are measured using electrodes attached to the skin of the subject's head. Using this principle and connection method limits the system to just a couple of movement commands ('left' and 'right', for example) as otherwise the error rate becomes too high. Nevertheless, this is enough to control a simple computer game using the power of thought alone. Robot control has also been demonstrated [4]. Using a simple cursor-based system, writing has been shown to be possible at speeds of up to about seven characters per minute [5]. For this example the user must be able to see the cursor on the screen to allow feedback from the computer.

Many brain-computer interfaces demand that the subject undergo training (possibly lasting as long as one week!) to learn the thought patterns that give rise to brain currents that the machine can discriminate reliably. The BBCI, however, shifts the burden of learning to the computer, which can shorten the adaptation process to just half an hour, with the subject imagining themselves moving either their left or their right index finger (for example) for periods of a second or so at a time. About one third of subjects tested manage to defeat the ability of the system to learn their thought patterns, for reasons that are not yet understood.

2 Amplifiers and A/D converter

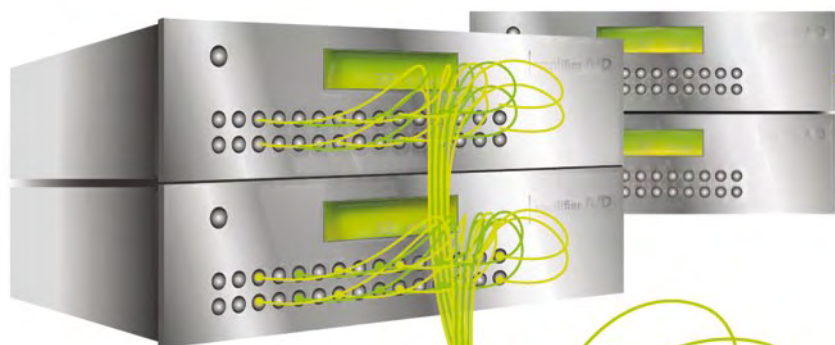The signals are taken via a flat cable to four amplifier units, each comprising 32 channels. The signals are digitised at 5 kHz to a resolution of 16 bits and then sent to a PC over a fibre optic link. These units are readily available on the market, with a price in the tens of thousands of pounds.



1 Electrodes

In the BBCI brain currents are measured using 128 Ag/AgCl (silver/silver chloride) electrodes, mounted together in a cap to fit over the head [6]. Caps of this kind are also used in medical research and cost a couple of thousand pounds. The electrodes are distributed over the whole of the upper part of the head, each making contact with the skin over a patch approximately 5 mm across. Within the project a cap has been developed that does not need gel to improve the electrical contact between electrode and skin but which can still measure and continuously record potential difference fluctuations of around 50 μV .



The brain currents fluctuate with typical frequencies between 0.5 Hz and 50 Hz, with the distribution being dependent on the nature of the brain's activity. 'Alpha waves', between 8 Hz and 13 Hz, are well known and are seen in the EEG when the brain is relaxed. When preparing to make a movement, lower frequencies (below 4 Hz) also come into the picture.

3 Preprocessing

The recorder PC takes the signals from the A/D converters and carries out some preprocessing operations which help to reduce the computational demands of the subsequent stages. The signals are band-pass filtered (between 0.05 Hz and 200 Hz) and then downsampled to 1000 Hz. Raw data packets are then sent to the next computer over the network, and simultaneously are stored in a database.

4 Signal analysis

The analysis stage starts with further preprocessing, whereby the signal is downsampled again to 100 Hz. From thinking about making a movement to executing it takes around a second: this means that it is best to collect one second's worth of data to analyse the corresponding fluctuations in brain currents. Data from periods of 128 samples (corresponding to about 1.2 s) are collected and multiplied by a window function chosen to give greater weight to the later samples. A Fourier transform is then applied, and from this the frequency components below 7 Hz are extracted. An inverse transformation reconstructs the signal, which is now resampled at 20 Hz. This forms the result of the signal analysis stage.

5 Classification

The classification module is implemented in C++ and in MATLAB, and embodies the majority of the technology that has been developed. Two threads running in parallel on the signal analysis computer examine the signals, each looking for evidence of one of the two possible control commands. The results from the two threads are combined, and any detected control command is transmitted over the network every 40 ms.

6 Feedback

The control commands are used to drive a multimedia program that runs on a further computer (the 'feedback client'). This then enables the subject to see the effect of their thoughts directly on the screen.

Computer network

Because of the large amount of computing power required, the BBCI employs several off-the-shelf PCs connected together over a 100 Mbit Ethernet network [6].

Internet Links

[1] http://ida.first.fraunhofer.de/bbci/index_en.html

[2] <http://bci.tugraz.at>


[3] www.bci-info.tugraz.at

[4] www.first.fraunhofer.de/owx_1_3836_2_2_0_e19487f27e917f.html

[5] <http://ida.first.fhg.de/publications/BlaDorKraSchWilMurMue06.pdf>

[6] <http://ida.first.fhg.de/publications/KreBlaCurMue07.pdf>

(080332)

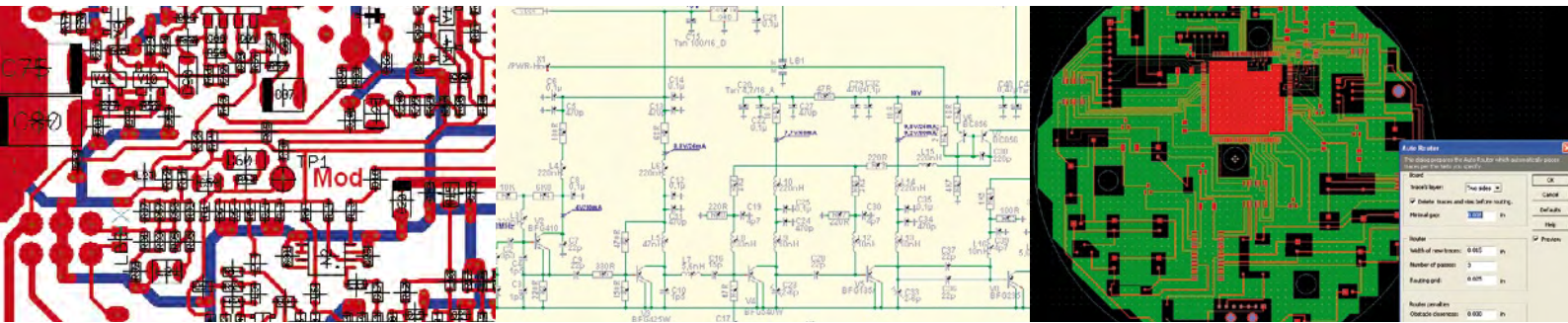

Panorama

An anthology of CAD programs

Guy Raedersdorf (Elektor France)

In November 2005 we published an article ‘Kaleidoscope’, accompanied by a DVD-ROM that included almost thirty programs relating to CAD (Computer-Aided Design). Given its success, we decided to repeat the exercise. Only this time round, for several different reasons, there’s no DVD with the magazine.

In our hunt for CAD software, we tried to collect as many evaluation versions as possible – demos with greater or lesser restrictions, but also 100% functional versions of programs – within this family of software. We’re well aware it’s impossible to be exhaustive and there are still some that have ‘slipped through our net’. But don’t worry, that’s doubtless just till next time round...

Ed.: don’t hesitate to tell us about your finds, favourites, etc., we’ll share them with all our readers.

Unfortunately, it’s just not possible for us to go into all the details of the dozens of CAD programs available on the market. So we’ll have to content ourselves with just mentioning certain features that struck us while we were installing and getting to know them.

Finally, let’s just add that ibfriedrich (Target3001!) and Seetrax (Ranger2 XL) have offered us ‘Elektor special’ versions with possibilities that go beyond their usual evaluation versions. We’re sure our readers will be able to make the most of these.

Why no physical DVD?

At the current price of blank writable DVDs, we didn’t feel it was justified (either from an economic point of view, or indeed an environmental one) to issue a physical DVD with each of the 150,000 copies of this September 2008 issue

(a Spanish edition was added to the European group three years ago). So we’re suggesting a dual approach:


1. the various programs can be downloaded individually (particularly suitable for those readers who don’t have a fast internet connection); all you have to do is go into the ‘virtual DVD’ and download the .zip file from the relevant directory.
2. or there’s a ‘virtual DVD’ that appears ‘physically’ as an .iso file to download from our website (warning: it’s almost 1.7 GB, which means a broadband connection is virtually obligatory!) and then burn onto a DVD using the burn software of your choice, Nero or Burning Studio. All you then have to do is put the DVD into your drive and it will auto-run (if your operating system is suitably configured), or you can just manually run the **index.htm** file in the root directory of the DVD drive containing your newly-burned DVD.

Now let’s move on to our review – the programs are arranged in alphabetical order.

Abacom

sPlan 6.0, the circuit entry application from Abacom, lets you create a circuit diagram easily and cleanly thanks to an extensive and expandable component library. Worth noting: the possibility of defining the form of the circuit sheets,

FREE DOWNLOAD
www.elektor.com/panorama

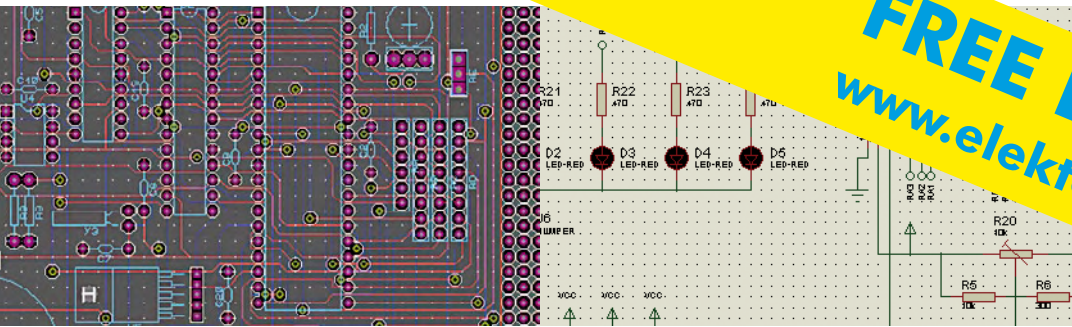

automatic component numbering (standard in most of the software in this category), component search, and the use of variables.

Sprint-Layout 5.0 is an easy-to-learn PCB design program with all the standard functions for this type of activity. It takes only a few minutes to grasp how it works.

Note the co-availability of French and German versions.

Extra on the Panorama 'DVD':

LochMaster 3.0 for your projects on prototype board.

FrontDesigner 3.0 for designing board overlays.

AMS

AMS (Advanced Microcomputer Systems) offers **Circuit-CREATOR**, an application that handles circuit entry, PCB design, and the other usual functions. Like most current programs, it supports SMD components. Options for several fonts per layer and for changing the shape of lands between layers. You can define supply and ground planes with or without thermal dissipation option. Interactive component placement. The rat's nest suggests optimum component layout, but also makes manual routing easy. Has a DRC (Design Rule Checking) function used to check the built-in design rules; it flags up an error and shows where it is. Their program also includes a simulation application **SpiceCreator**, also available as an **extra** on the DVD.

Baas

Many of our readers are familiar with the name **Layo1PCB**; it was in fact one of the first PCB design programs with more than one language to choose from. This is still the case with this latest version, Layo1PCB version 10.19 on offer from Baas Electronics. The version on offer here is the simplest version. As it is not linked to a netlist, this program lets you place your components wherever you want and draw tracks the way you want. To be able to read a netlist generated by a circuit entry program such as those created by Mentor, multiSim, Calay, Protel, or Tango, you need to move up to the professional version, Layo1 PCB Design.

Capilano


As part of the Panorama download we're offering you two products from the Capilano stable, the **DesignWorks Express for Windows** program and the evaluation version of **DesignWorks Professional 5**. DesignWorks Express for Windows (free) is a handy application for circuit entry (single-sided) as long as the number of pins remains under 500. All options are open to you: editing, saving, print-out, and even producing netlists for loading into a PCB design program, for example **Pad2Pad** (also free) described below.

Like its little brother, DesignWorks Professional 5 is a circuit entry application. 100% hierarchical design, standard and custom netlist formats, extensive component library, are just a few of its features.

Let's just note that there is also a version of DesignWorks Professional 5 with a simulation function.

Cadence

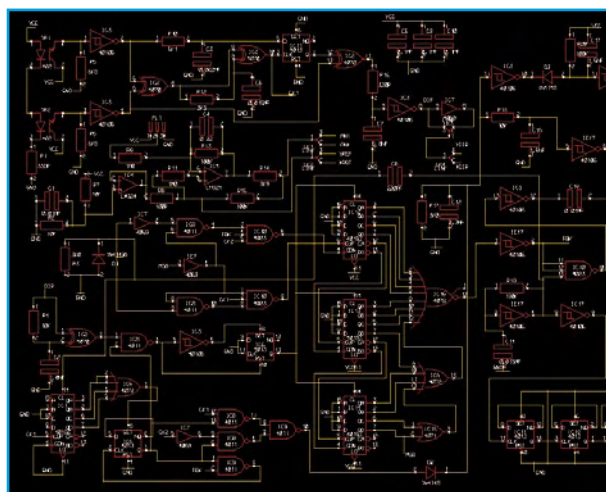The **OrCAD® PCB Designer** suite from Cadence, the 'proto-genitor' of circuit entry software, is now at version 16.0. Integration has reached its highest point, meaning a remarkable consistency in the commands common to the



various modules that make up OrCAD PCB Designer, in this way making it possible to design a project from start to finish, from entering the circuit, via component drawing, to designing the PCB. It includes an interactive autorouter SPECCTRA (re-named Allegro PCB Router), a piece of software that seems to be becoming the must-have solution in the field of autorouting.


Once installed, the software appears in the form of two programs, **OrCAD Capture CIS** for circuit entry (with a DRC function that lets you eliminate the majority of errors right from the outset) and **OrCAD PCB Editor** for PCB design and routing. A new ActiveParts function lets you search for information about an OrCAD component using various criteria.

Cadsoft

Eagle 5.0 from Cadsoft is one of the most popular circuit entry and PCB design programs amongst hobbyists in Europe. It owes its popularity to the ease of use and perform-

ance of the non-commercial version (see table). It exists in several versions, including a Freeware version limited to a board area of 100 × 80 mm, 2 signal layers, and 1 circuit sheet. Apart from these limitations, you can do everything that can be done with the Professional version. If you want to have a manual (in English or German), a CD-ROM, and unconditional technical support, then it's worth purchasing a license (€ 49).

It's worth noting that Eagle is one of the few CAD applications, if not the only one as far as we are aware, to exist in Windows, Linux, and Mac versions.

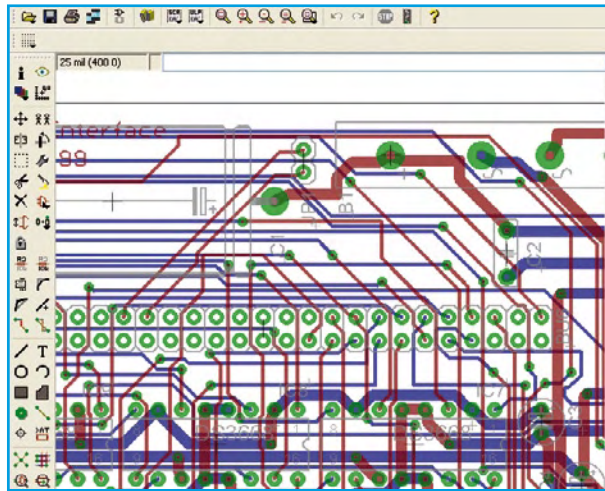

FreePCB 1.20

Allan Wright's **FreePCB** is a free PCB design program. The Manual available on the author's website is an excellent resource for finding out what's involved when you want to design a printed circuit. There's no circuit entry function, so you'll either need to use a circuit entry program, or else create your own netlist, making sure it can be imported into FreePCB. The existence of a rat's nest helps a great deal in positioning the components properly, thus making it possible to avoid unnecessary track lengths. The presence of a shape editor is quite surprising in such an environment, but FreePCB's specific function is to make printed circuits, and it does this well.

ibFriedrich

TARGET 3001! V13 is the worthy successor to its predecessor V12, covered in November 2005. A few points of interest:

- 3D view of the project (lets you see if a project is viable)
- Reverse-engineering (you really have to discover this amazing tool, now included in more and more programs)
- Multi-lingual (board markings and documentation!)
- Assistant for aligning components geometrically (placing 7 LEDs along an arc from 20° to 120° becomes child's play).
- Fuller library of 'standard' components
- Automatic library updating, etc.

Note: The version on offer here is an 'Elektor special' version that lets you do a lot more than the standard demo version.

KiCad

The only fully OpenSource program in this 'Panorama', **KiCad** is actually a suite of four programs under an overall project manager, Kicad. It is fully functional, comprising all the modules needed, from circuit entry, **Eeschema**, to PCB design, **Pcbnew** (which also lets you visualize it in 3D), via the Gerber file viewer **Gerbview** and **Cvpcb**, the form selection program for the components used in the project. Even though it's OpenSource, KiCad is far from being a second-rate piece of software; it's very comprehensive and even includes autorouting.

The documentation includes a very instructive and well-presented tutorial.

LabCenter


The latest offering from LabCenter is **Proteus Design Suite 7.2**. Proteus is in fact a combination of two programs in one: **ISIS** for circuit entry and **ARES** for PCB design with autorouting and 3D visualisation. Together, these form a powerful, highly-integrated environment. There are several versions, from the Starter Kit, with a netlist limited to 500 pins, to the Level 3 version which handles unlimited pins and layers.

ISIS supports hierarchical design and can be used to create busses; ARES is based on netlists, and is able to use physical DRC.

Like many current applications, the libraries include over 10,000 different components.

McCAD

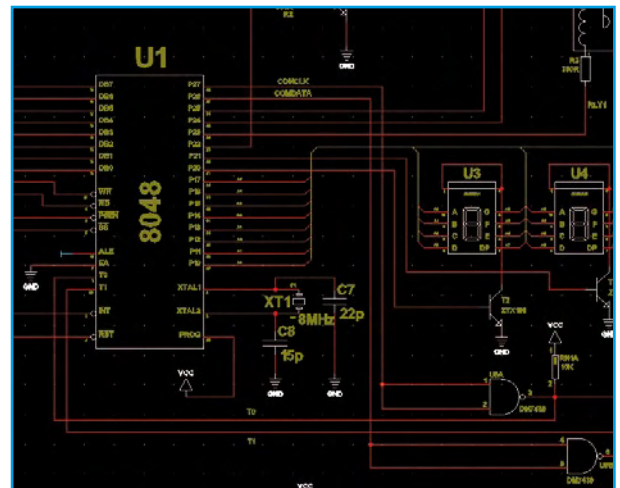McCad has made a reputation for itself in the Mac world as the first manufacturer of CAD software to run on Mac




– at a time when our PCs were still only running on DOS! McCAD offers 2 programs for Windows, **EDS-1** and a higher-performance version of this software, **EDS-plus**. The evaluation version is for EDS-1. McCAD has opted for a modular approach, customers buying just those modules they need: basic or advanced circuit entry, digital/analogue simulation, PCB design, autorouting, Gerber conversion, etc. There is also a free version, EDS Lite.

Worth noting: the possibility of downloading a very instructive e-book 'Quickstart to Simulation' devoted to simulation.

National Instruments

Multisim from National Instruments is an old acquaintance to the Elektor designers. For years, they've been working with Ultiboard, the forerunner of this program. Multisim, the latest offering from the Electronic Workbench Group – which has now become part of NI – has evolved into a multi-faceted tool combining circuit entry, interactive circuit simulation, PCB design, and compliance testing. Multisim is available in different versions: Base, Full, and Power Pro. We are offering you a trial of the Base version.

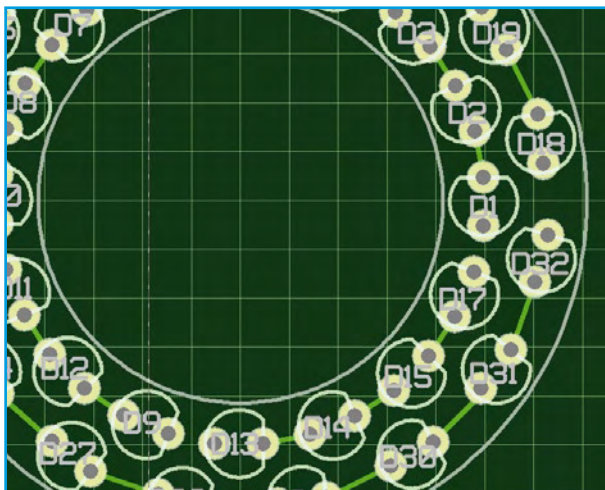Multisim in fact comprises two modules, Multisim for cir-



cuit entry and SPICE simulation, and **Ultiboard**, in its new livery, for PCB design with built-in routing. The possibility of using LabVIEW measuring instruments adds an extra dimension to this software.

Number One Systems

Easy-PC from Number One Systems has been well-known for years, and is now at version 11.0. What struck us with this new version is the existence of Design Calculators that let you perform various operations like defining track size according to current, and calculating their impedance, as well as the temperature rise in operation. Naturally, DRC is available here too.

One of the interesting options – found in other software too, albeit under a different name – is the Intelligent Gerber Import, which lets you re-create, from a Gerber file from any source, an Easy-PC PCB from which it is then even possible to derive a full circuit diagram.

In addition, you'll also find a demo version of **Easy-Spice**, a simulation program.

Seetrax

Seetrax has added two of its programs to our list: **Ranger2 XL** and **Seetrax XL Designer** (SXLD to its friends). To install Ranger2 XL, all you have to do is run the *setup.exe* file; once installation is over, you'll have the demo version of Ranger2 XL with its original restrictions.

To now change your demo version into the 500-pin version (a present from Seetrax), all you need do is copy the *licence.dat* licence file (from the 'Licence' subdirectory; make sure the name is right, without any other additional suffix) into the ... \seetrax\ranger2xl\data directory.

Seetrax XL Designer is the second program from Seetrax. To install the demo version, all you need do is run the *XLDesignerDemo_1.49.exe* file. Licence installation

takes place during this operation, so the program works right away. This version is limited to projects comprising a maximum of 30 components and 50 nets (it is otherwise identical to the full version). When the program is run, it offers a button to search for updates.

Note: After transfer of the licence file, the version of Ranger2 XL offered here is the '500' version that normally sells for £90.


Those Engineers

Spicycle is a full program that lets you design a PCB directly from a netlist or in more conventional fashion from a circuit diagram. As all the operations are carried out under Active X control, it is possible to perform back annotation between the circuit diagram, the netlist, and the simulation parameters. One interesting aspect of Spicycle is that it includes a very comprehensive symbol library, making it possible to design not only an electronic circuit, but even to create a sort of schematic diagram of any kind of system (for a wind tunnel, for example).

Spicycle offers a simulation in 'mixed' mode (integrates seamlessly with the **SpiceAge** simulator). Data transfer to the circuit diagrams is bidirectional, meaning you can import a SPICE netlist which is then presented in the form of interconnected circuit symbols. Back annotation becomes a real pleasure.

Tsien

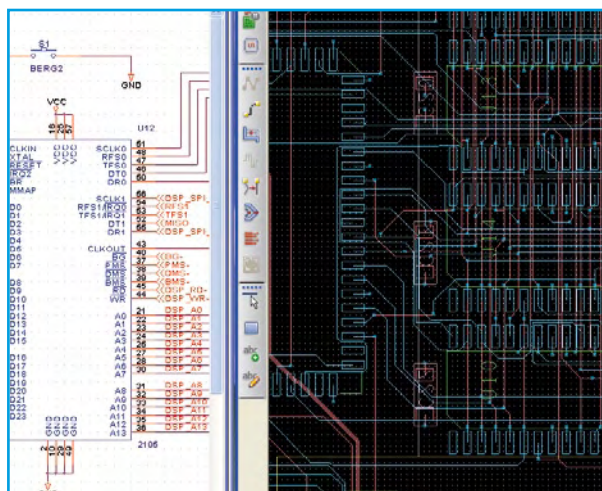BoardMaker3 has come a long way since it came out in 2000, and has been regularly updated. The V1.33.0022 version on offer here dates from 24 June 2008. BoardMaker3 is an integrated environment for PCB design; it has high-performance tools for circuit entry, Spice simulation, 3D visualisation, and autorouting.



Worth noting: on the www.tsien.info/guide.php site there is a series of pages that explain extremely well what's involved when you start to tackle a circuit entry and PCB design application.

Visionics

EDwinXP includes all the tools you could wish for required to produce a printed circuit: the circuit editor, PCB editor (with autoplacement and autorouting), simulators in EDSpice mixed mode, the library manager, and all the rest.

Worth noting: the presence of a thermal analyser (with sig-

nal integrity and field analysis), and a test for the effects of electromagnetic radiation on the circuit. The installation of this program alone is already a real feat for the eyes.

Note: It's important for the directory where the EDwinXP161 files are going to be decompressed to have a name of 8 characters or less (e.g. EDwinXP) if you want to be able to install the program (see the readme.txt file that comes with the program).

So where are the missing ones?

Despite all our efforts, we didn't manage to 'nail' all the CAD software manufacturers we'd have liked for our round-

up. Some of them weren't in a position to make an evaluation version of their programs available to us (for example, **Altium**, which does however boast a most attractive virtual demonstration centre at www.altium.com/evaluate/demo-center/# and choose your language), others simply chose not to.

Conclusion

Reviewing almost 20 programs, whether comprehensive or specializing in just PCB design, really brought home to us the increasing complexity of this type of software. Using such programs demands a relatively up-to-date PC, if you

Manufacturer	Program name	Circuits	PCB	Autorouting	Simulation
Abacom	sPlan 6.0 *	yes	-	-	-
	Sprint-Layout *	-	yes	yes	-
	Frontdesigner 3.0 *	-	-	-	-
	Lochmaster 3.0 *	-	-	-	-
Advanced Microcomputer Systems	Circuit Creator *	yes	yes	yes	yes
	Spice Creator *	-	-	-	yes
Baas Electronics	Layo1PCB 10.0 *	-	yes	-	-
Cadence	OrCAD 16.0 *	yes	yes	yes	option
CADSoft	Eagle 5.0 ¹⁾				
	Light *	yes	yes	yes	-
	Standard	yes	yes	yes	-
	Professional	yes	yes	yes	-
Capilano	DesignWorks Express * ²⁾	yes	via Pad2Pad	-	-
	DesignWorks 5.0 *	yes	via Pad2Pad	with add. module	with add. module
FreePCB	Free PCB 12.0 *	-	yes	with add. module	
IBFriedrich	TARGET3001! ³⁾				
	Light *	yes	yes	yes	yes
	Smart	yes	yes	yes	yes
	Economy	yes	yes	yes	yes
	Professional	yes	yes	yes	yes
	Design Station	yes	yes	yes	yes
KiCAD	KICAD *	yes	yes	yes	-
LabCenter	Proteus 7.2 *	yes	yes	yes	yes
McCAD	EDS-1 *	yes	yes	with add. module	with add. module
	McCAD 3SPICE Lite *	-	-	-	yes
	SimPlus *	-	-	-	yes
National Instruments	NI Circuit Design Suite 10.1 *	yes	yes	yes	yes
Number One Systems	Easy PC *	yes	yes	with Router +	Easy-Spice
Others	Easy-Spice *	-	-	-	yes
Pad2Pad	Pad2Pad *	-	yes	-	-
Seetrax	Ranger2 XL ⁴⁾	yes	yes	with add. module	-
	XL Designer *	yes	yes	with add. module	-
Those Engineers	Spicycle *	yes	yes	-	SpiceAge
	SpiceAge *	-	-	-	yes
Tsien	BoardMaker 3 *	yes	yes	gateway	yes
Visionics	EDWinXP 11.6 *	yes	yes	yes	yes

* = included on Panorama virtual DVD, N.I. = No info, - = No or Not Applicable

¹⁾ Versions also available for Mac and Linux (see under 'Extra')

²⁾ Free version

³⁾ This is an upgraded Elektor special version

⁴⁾ The version on the virtual DVD is the Ranger2 XL/500 version (normally worth £90)

want to avoid its turning into a real trial of patience. In any case, you'll need quite a lot of that to get to grips with any of these programs. Most of the top-end programs (price-wise too!) are hardly very different in terms of what they offer, except in terms of certain details.


And what for one user may seem to be an unforgivable omission may be an option that another user has no need of. It's a question of taste and requirements. You are the best judge of that. So why not take a look at our website and download the .iso file to create your own DVD, or pick the programme you'd like to try out... Happy exploring!

Ed.: In view of the time that elapsed between writing this article and the 'gathering' of the software appearing on the virtual DVD, it's still a good idea to look and see if there may be a new version of any of the software described in this article you may be interested in (hence the links given in the table).

(080356-1)

The author would like to thank Cadence Design Systems, Inc. for allowing Elektor to distribute OrCAD software from their site and a virtual DVD. By the same token, he would like to thank all the other companies for their unconditional permission.

Price (rrp)	Homepage
€ 39.90	www.abacom-online.de/fr/
€ 39.90	
€ 39.90	
€ 39.90	
\$ 99 to \$ 995	www.advancedmsinc.com/
\$ 99	or www.circuitcreator.com/
€ 99 to € 950	www.baas.nl/
N.C.	www.cadence.com/
	www.cadsoft.de/
€ 49	
€ 750	
€ 1,499	
free	www.capilano.com/
\$ 395 to \$ 790	
free	www.freepcb.com/
	www.ibfriedrich.com/
€ 59	
€ 159	
€ 569	
€ 1,649	
€ 2,999	
free	www.lis.inpg.fr/realise_au_lis/kicad/
£ 150 to £ 1,225	www.labcenter.co.uk/index.cfm/
\$1,095 to \$ 1,395	www.mccad.com/
\$ 395	
\$ 695	
N.I.	www.ni.com/
£ 247 to £ 447	www.numberone.com/
£ 295	
free	www.pad2pad.com/
£ 90 to £ 460	www.seetrax.com/
£ 100 to £1,000	
£ 45 to £ 195	www.spiceage.com/
£ 45	
£ 350/yr or 6x price	www.tsien.info/index.php
\$ 110 to (N.I.)	www.visionics.a.se/

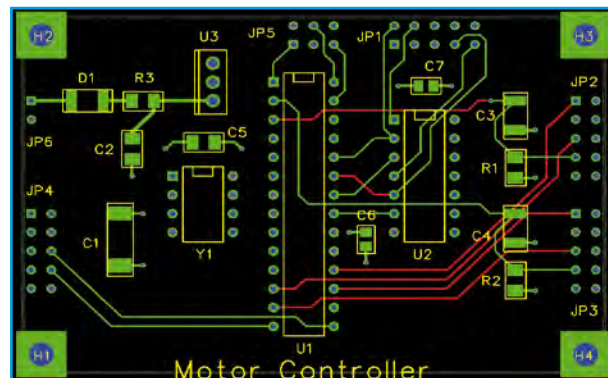

Internet Links


The manufacturers' addresses are given in the table.

CAD software manufacturers

- Altium** www.altium.com
- Ariadne** www.cad-ul.de/ariadne/index.html
- Autotrax** www.kov.com
- CADint** www.cadint.se
- CirCAD** www.holophase.com
- DesignSoft** www.designsoftware.com
- Express PCB** www.expresspcb.com
- Mentor Graphics** www.mentorg.com
- Merco electronics** www.mercoelectronics.info
- PCB Editor** www.waldherr.com
- Pulsonix** www.pulsonix.com/index.asp
- The PCB Designer** www.cad-design.com
- Vutrax** www.vutrax.co.uk/
- Zuken** www.zuken.com

General source links

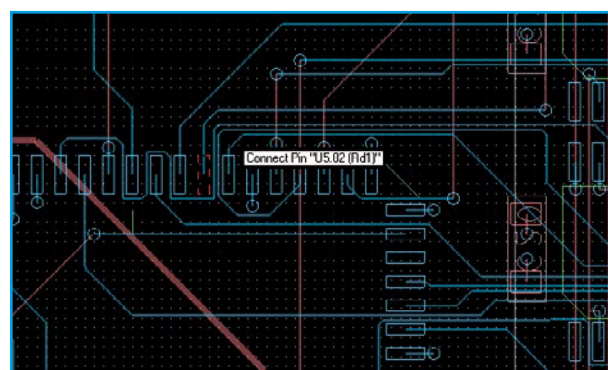- www.terrypin.dial.pipex.com/ECADList.html
- www.abcelectronique.com/annuaire/societes_52.php
- <http://etronics.free.fr/dossiers/softs/soft00.htm>



Ball & Beam for Ele

Grind your teeth on PID design and programming

Jose Luis Rupérez Fombellida & José Manuel Escobosa Bravo

Like it or not, Ball & Beam is a compulsory item on the Electronics Engineering curriculum, specifically for classes on PID (proportional-integral-derivative) control systems. The idea is to try to balance a ball on a beam using a control loop. If the ball is pushed, the system moves the beam to return the ball to its initial position. So let's get out our USB DAQ card and a PC to show off!

Apart from your curiosity and eagerness to learn about PID (one of the great pillars of electronic engineering), the ingredients of this project can be summarised as

- the Elektor USB Data Acquisition (DAQ) Card [1];
- a circuit which acts as interface between the DAQ and the mechanical system;
- mechanics, i.e. construction of the ball & beam system, which is very easy and cheap compared to commercial units;
- A personal computer running a program.

This project can be interesting for anyone keen on electronics and/or computers; even more so if he or she is curious about control and regulation systems or about discrete PID controllers using Windows C++/CLI programming. It may also trigger old hands at electronics to re-live the PID experiments they once did at College in the dim past. The project has a low threshold as

there is no need to do any Laplace or Z transform. There is no need to do any calculation either; apart perhaps from an empirical tweaking of the PID controller by adjusting certain controls in the PC program. Of course, those of you with solid mathematics education can rigorously analyse the system.

On the other hand, seeing how a ball remains stable in a certain position on

Watch the Elektor Ball & Beam scale model on YouTube

the beam not only has didactic or academic interest! Aircraft of the vertical takeoff type such as the Harrier employ similar control loop systems to maintain stability while stationary in the air.

Recipe for the system

The Ball & Beam system consists of electronics, software and mechanical elements and so makes a nice project to run by a group of students from dif-

ferent fields of study. The elements are shown in **Figure 1**.


The electronics comprises two printed circuit boards:

1. Elektor USB Data Acquisition Card (November 2007). This card has 8 digital inputs, 8 digital outputs, 8 analogue inputs and 2 analogue outputs. From all this I/O capacity we employ just one digital output, one analogue output and one analogue input. For a deeper knowledge of this card, the article in ref. [1] should be read.

2. Ball & Beam Interface Card. The card described in this article is used to adapt the Ball & Beam Mechanics to the USB Data Acquisition Card.

For software, we add the **Ball & Beam PC Program**. This application for PC communicates with the Data Acquisition Card to send and receive information from the Ball & Beam mechanical assembly through the Ball & Beam Interface Card. It is developed in C++/

elektor USB DAQ Card

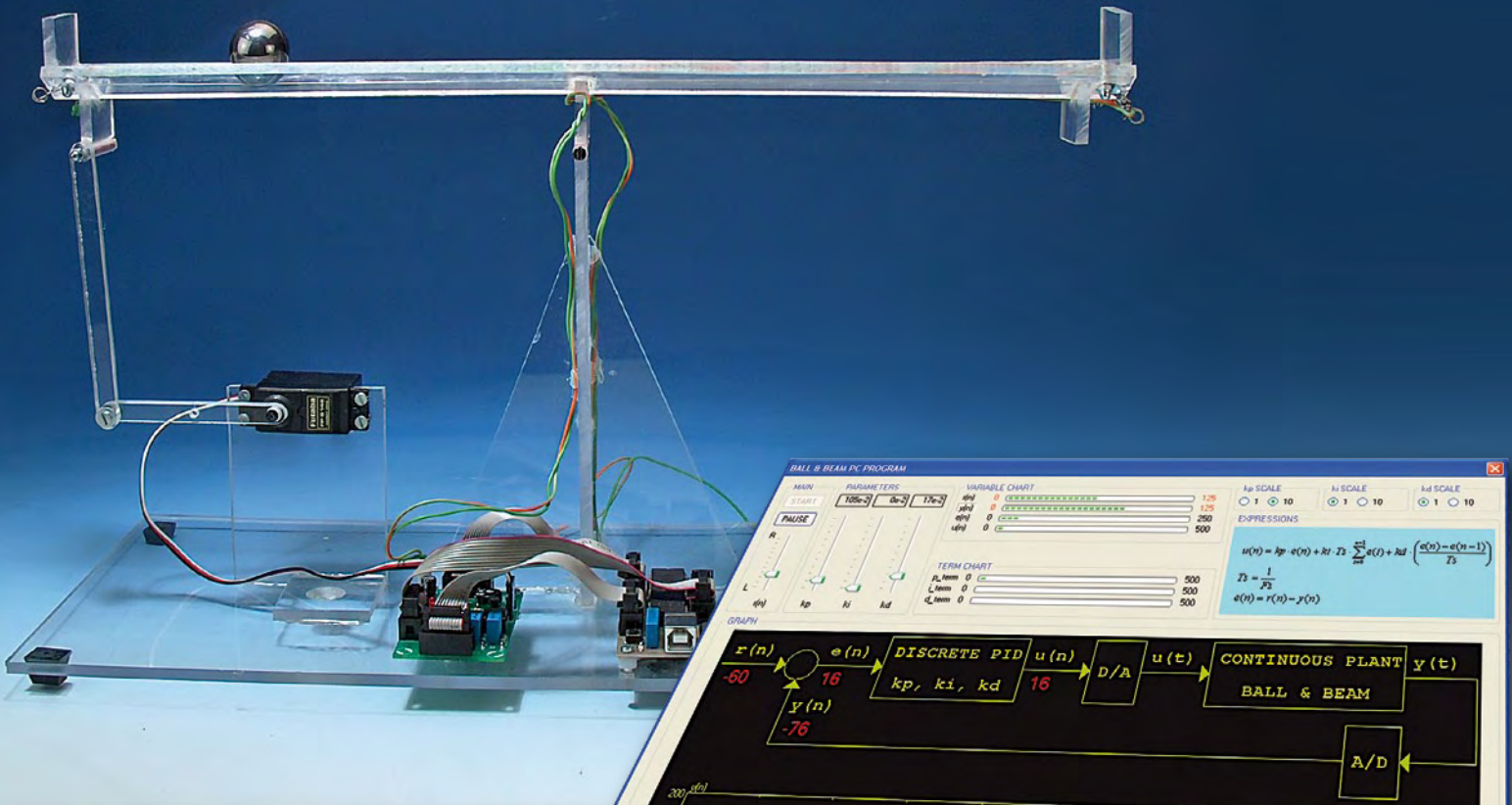

CLI with the free Visual C++ 2008 compiler (Express Edition) available on the Microsoft website). Lastly, the mechanical assembly is a scale model made of methacrylate (methacrylate or Perspex™) which has a V-shaped beam in which a steel ball can roll. It includes a potentiometer (made from resistance wire) to determine the position of the ball on the beam, and a servo to make the beam swing up and down.

USB data acquisition card

From the USB Data Acquisition Card, the following resources are used:

- 1. AN0** — this analogue input is available via pin 1 of connector K5 on the card. This input receives a voltage proportional to the position of the ball on the beam.
- 2. CCP1** — this analogue output is found on the pin 1 of connector K4. It is programmed to control the servo position

and, therefore, the angle of the beam.

- 3. RDO** — this digital output is available on pin 1 of K1. An LED is connected to it, which will blink at the PID sampling frequency F_s when the system is operating.

Ball & Beam interface card

The Ball & Beam Interface Card was purposely kept a simple as possible, using cheap and easy to find components. The price to be paid for this simplicity is some tolerance but that's not a problem since we have an adjustment process available. The circuit diagram of the interface card is shown in Figure 2. It can be

thought of as consisting of three parts.

- 1. LED** — this indicator (with its associated current limiting resistor) is connected to the RDO digital output on the USB Data Acquisition Card. The Ball & Beam PC program will make this LED blink to the sampling frequency F_s .
- 2. Filter** — this is for the ball position 'potentiometer'. As the steel ball touches two lengths of Nickel-Chrome wire, on occasions false contacts will be produced which would give wrong values. To counteract erratic values as much as possible, a low-pass filter consisting of R1 and C1 is included.

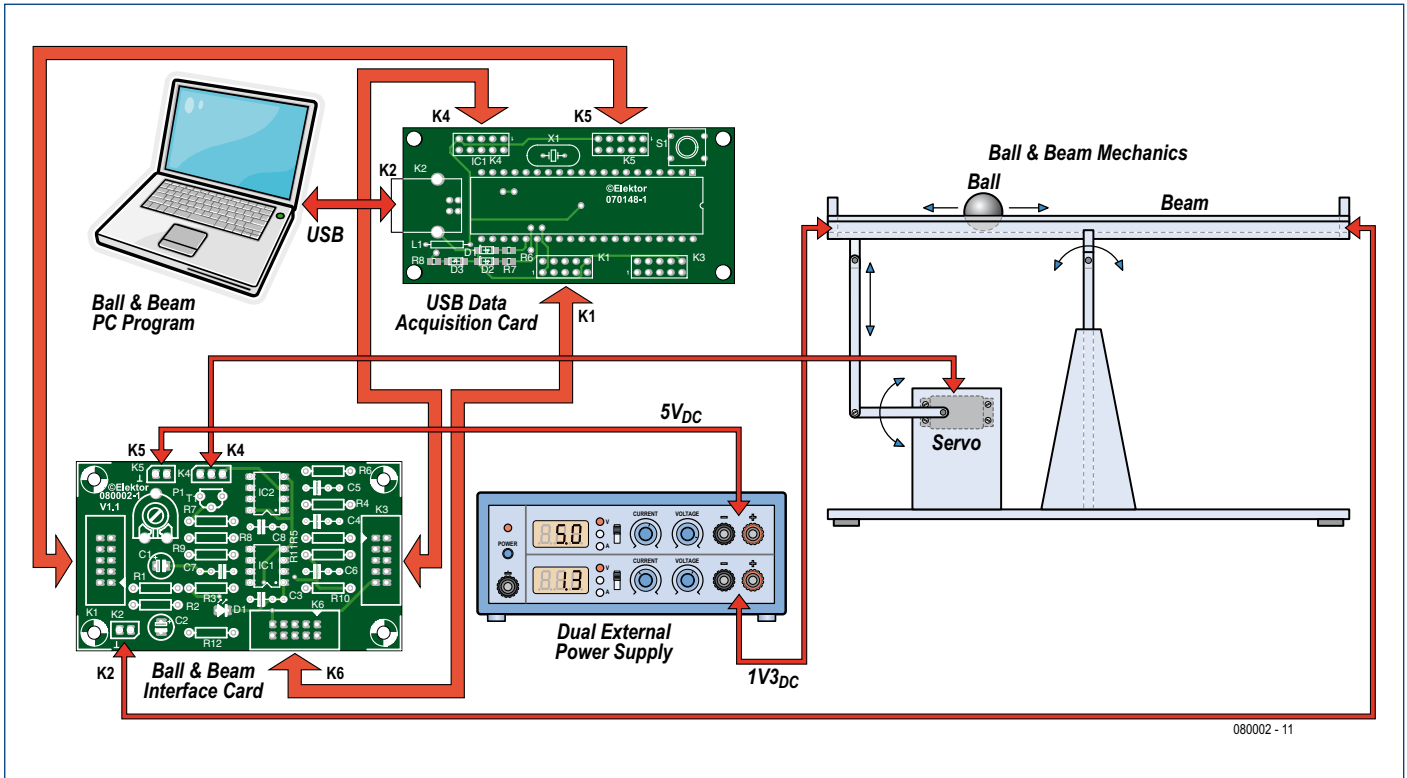


Figure 1. Overview of electronic and mechanical components connected up.

This 6 dB/octave (first order) filter effectively sits between the ball position 'potentiometer' and the AN0 analogue input on the USB Data Acquisition Card. The simulation result of this filter is shown in **Figure 3**. Note that the roll-off frequency is very low at just 7.5 Hz, but enough to perfectly register the ball position due to the movement by the beam.

3. Pulse generator to the servo — the beam slope is determined by the position of a servo. The beam will remain horizontal if the servo is in the centre position. If the servo spindle is at one extreme, the beam slopes some 15°. If it is at the other extreme, the beam slopes 15° opposite.

The signal fed to a servo is composed of pulses with a frequency between 50 Hz and 60 Hz. The pulsewidth determines the servo position and varies between 1 ms and 2 ms. The servo's central position corresponds to 1.5 ms. These times may vary slightly from a servo manufacturer to another. The pulsewidth is controlled by the CCP1 analogue output on the USB DAQ Card.

The relevant electronics is simple: one astable and one monostable implemented using the ICM7555 or TLC555, i.e., the low-power CMOS version of the famous LM/NE555 (which, by the way, should not be used). Both IC1 and IC2 are supplied from the USB port on your computer through the USB DAQ Card. More on the 7555 and relevant calculations in the **inset**.

Around IC2 a monostable has been assembled. Its trigger signal is provided by IC1; that is why the pulses

$$U_{CCP1} = 5D$$

Where D is a constant between 0 and 1. As the CCP1 signal is going to modulate the monostable's pulsewidth, it is necessary to filter it to turn it into a continuous level. This is done by R5, C4, R4 and C5, the components forming a low-pass filter of modest features with a roll-off at about 30 Hz. That's high enough for the sampling frequency F_s and low enough for suppressing harmonics of the 2.9 kHz PWM signal on CCP1. The slope of

the filter is 12 dB/octave (2nd order). Notice that the charging of the monostable's capacitor is not done with the usual

Provide video proof to Elektor if you did the project with a ball heavier than 1 kg.

generated by the monostable have the same frequency as the IC1 astable. The output pulsewidth controls the servo position and must have a frequency between 50 Hz and 60 Hz. The monostable pulsewidth should vary between 1 ms and 2 ms (typically).

The pulsewidth is determined by the CCP1 analogue output. CCP1 supplies a PWM signal with a frequency of about 2.9 kHz whose average in volts can be calculated with the expression:

simple resistor — here, a constant-current source is used. Built around T1, it keeps the capacitor's charge build-up linear, enabling the monostable pulsewidth to vary in linear fashion with the CCP1 signal. The constant current flows in T1's collector line and is adjusted by P1. See the **Monostable IC2 dimensioning inset** for the component value calculations.

The servo, besides the pulse signal, needs a supply voltage. As its current consumption is rather high (hundreds

of milliamps), it is impossible to supply it from the USB DAQ Card (remember where that card gets its power from?). Hence it is essential to power the servo from an external supply rated at 5 V and 1 A, connected up to K5.

Construction

The component mounting plan of the circuit board designed for the interface card is shown in **Figure 4**. As usual the true-scale copper track layout (reflected and non-reflected) is in a free .pdf file found on www.elektor.com/080002 i.e. the web page for the project. Construction of this board should be a breeze as only traditional through-hole components are involved.

The Ball & Beam PC program

The program developed for the project implements a discrete PID controller with an F_s (sampling frequency) of 10 Hz. The PID mathematical derivation is given in the **PID maths inset**. The PC program is also a free download from the project web page. All PID parameters can be controlled and observed in the program, see **Figure 5**. A brief program description is given below.

- **MAIN.** Using **START**, you launch the system and with **PAUSE** you stop it. You can adjust the reference (desired position of the ball on the beam) by adjusting $r(n)$.

- **PARAMETERS.** Here the PID controller's k_p , k_i , and k_d constants can be adjusted. For each of these there are two scales: 1 and 10.

- **VARIABLE CHART.** This shows the evolution of $r(n)$, $y(n)$, $e(n)$, $u(n)$ signals. These are, respectively: reference (desired position of the ball on the beam); real position of the ball on the beam; error and PID controller output to the servo. The starting numbers and end of scale remain in black if the value is positive and they change into red for negative values.

- **TERM CHART.** Here you can view the evolution of proportional, integral, derivative (PID) terms, as parts of the controller maths. As before, black is positive and red is negative.

- **EXPRESSIONS:** In a frame you view the mathematical expression used for the PID controller implementation.

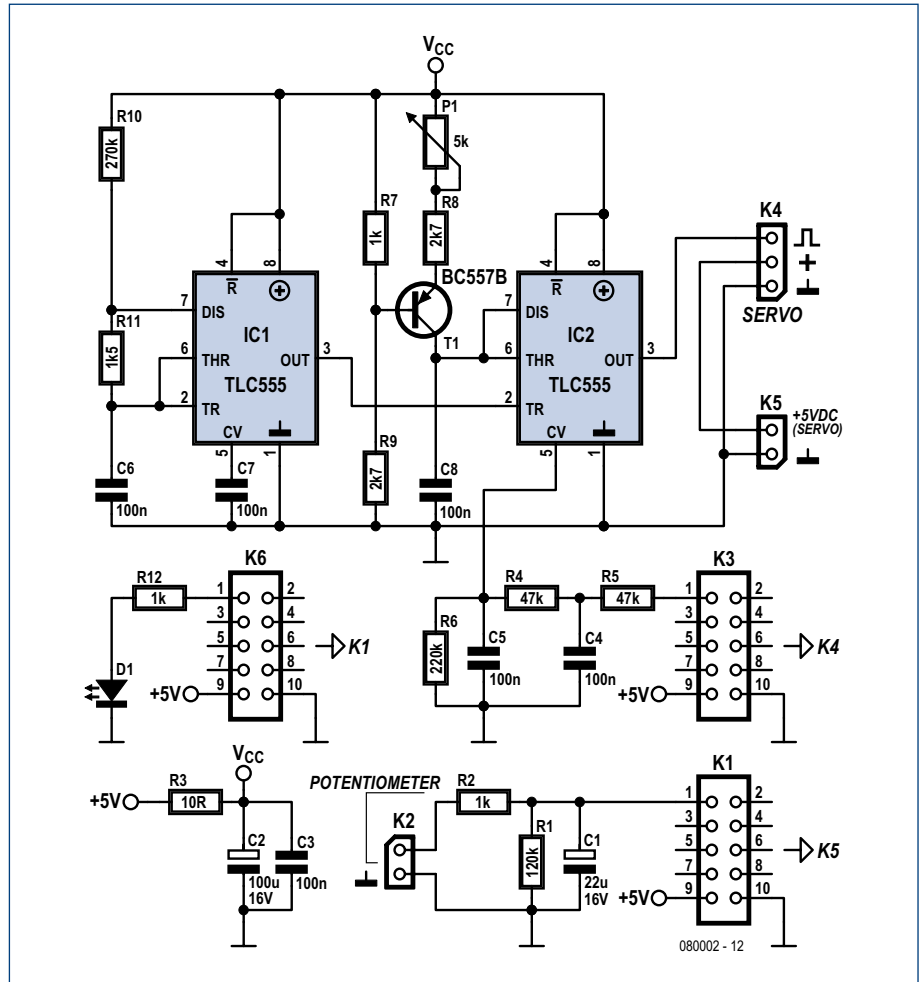


Figure 2. Circuit diagram of the Ball & Beam interface card.

- **GRAPH.** There are two charts: the first one is the whole system's block diagram consisting of the discrete PID controller (implemented by software in the Ball & Beam Program), a D/A converter and an A/D (both on the USB

DAQ) and the 'continuous plant' which is the Ball & Beam mechanical assembly. The Ball & Beam Interface Card only adapts the USB Data Acquisition Card to the Ball and Beam mechanics, that's why it does not appear in the

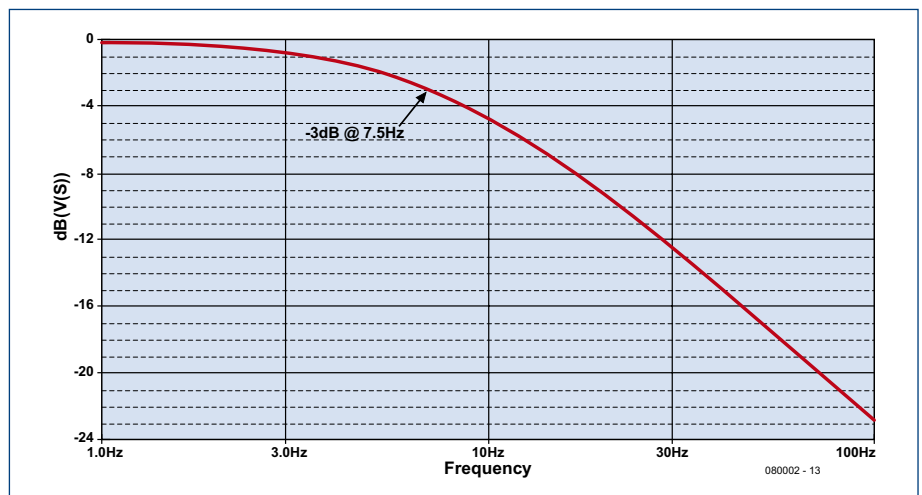


Figure 3. Frequency response of the filter designed for the wire potentiometer.

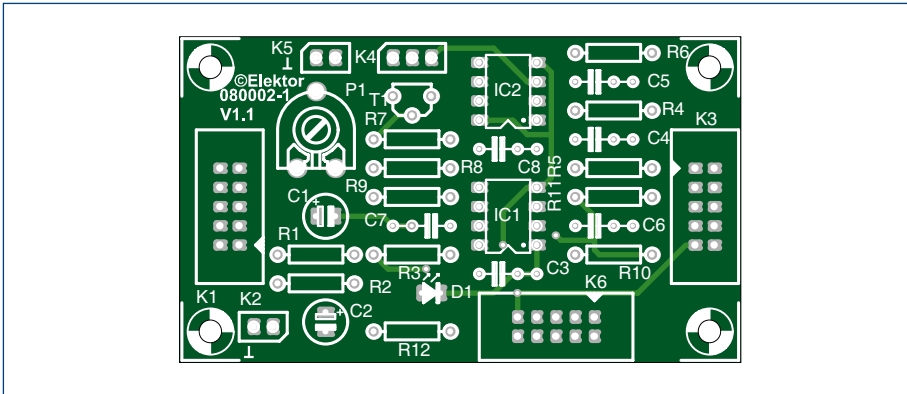


Figure 4. PCB design for the interface. The copper track layout is a free download.

How this acts like a potentiometer is illustrated in **Figure 6**. If the ball is at the left end of the beam, the voltage between the wires is (close to) 0 V. This voltage keeps increasing as the ball moves to the right, until getting to a maximum of 1.3 V.

The servo used is the Futaba type S148 or equivalent. It is connected to K4 on the Ball & Beam Interface Card. The servo's white wire connects to pin 1 of K4, the red one to pin 2 and the black one to pin 3.

Starting up

The USB DAQ Card connection to the PC and the installation of the corresponding driver is explained in [1].

Once the USB DAQ is installed, you can launch the Ball & Beam PC program. Make sure that the application is stopped (Status: STOP). Connect the 5 V, 1 A external power supply and adjust preset P1 until the 'C' arm (see mechanical assembly document) gets horizontal — the beam must be horizontal too. Click on the START button (Status: RUN); this will take controls $r(n)$ and kp to their highest position (the latter in the $\times 10$ scale), whilst checking that the 'C' arm is at an angle of 30° to 50° relative to the base. Then stop the application (Status: STOP).

Now put the ball on the beam and connect the 1.3 V/1 A auxiliary power supply. Move the ball by hand to the far right of the beam, keeping it there, and write down the voltage measured across resistor R2. This should be approximately 1.3 V. Adjust the aux power supply to get exactly 1.3 V. Now everything is ready for the first try.

Maiden run

Push the START button on the program and slide reference $r(n)$ to the middle. Slowly raise the kp proportional constant until the ball rocks slowly on the beam. Carefully increase the derivative constant until the ball is stable. If so, push it a little by hand — the system should respond by keeping the ball steady.

Now increase the integral constant little by little until the error is eliminated and the ball is steady as before, but this time approximately in the middle of the beam. Got it! PID in action... tell everyone about it at College and in the Elektor forum!

From here, you and your classmates can try as much you want, for example:

COMPONENTS LIST

Resistors

- R1 = 120k Ω
- R2,R7,R12 = 1k Ω
- R3 = 10 Ω
- R4,R5 = 47k Ω
- R6 = 220k Ω
- R8,R9 = 2k Ω
- R10 = 270k Ω
- R11 = 1k Ω
- P1 = 5k Ω preset

Capacitors

- C1 = 22 μ F 16V radial
- C2 = 100 μ F 16V radial
- C3,C6,C7,C8 = 100nF
- C4,C5 = 100nF

Semiconductors

- D1 = LED, low current, 3mm
- T1 = BC557B
- IC1,IC2 = TLC555 or ICM7555 (do not use plain 555)

Miscellaneous

- K1,K3,K6 = 10-way boxheader
- K2,K5 = 2-way SIL pinheader
- K4 = 3-way SIL pinheader
- PCB, ref. 080002-1 from www.thepcbshop.com
- PCB artwork, free download from www.elektor.com/080002
- Project software, free download from www.elektor.com/080002

block schematic.

The second chart, located in the lower part of the screen, shows the evolution of a selected (n) function. The signal can be any one of those included in the VARIABLE or TERM CHART. By clicking on its name, it will appear represented.

The program was written using C++/CLI with the free of charge Visual C++ 2008 (Express Edition) compiler. The most important function is called 'Void timer1_Tick' and it is found in the archive 'Form1.h'. In this function, among others, sits the discrete PID controller code.

The free of charge .NET XYGraph was also used for the control of componentXtra.com.

Ball & Beam mechanics

Parts lists, parts photos and details of the mechanical assembly of the Ball & Beam scale model may be found in a supplementary document that can be downloaded free of charge from the project web page as archive file 080002-W.zip. The document also has

an interesting discussion on selection of the ball material (steel) and its weight (approx. 64 g).

The beam has two wires made of nickel-chrome (NiCr 80%/20%) between which the ball rolls. The steel ball representing the wiper, the lot acts like a linear potentiometer (or 'rheostat') that's perfect to determine the ball position on the beam. The resistance wire is normally used for manufacturing and repairing heating elements. The wire has a diameter of 0.5 mm. Resistivity for the nickel-chrome at 80%/20% is about 1.1 Ω mm²/m. The beam length being 40 cm, the resistance works out as

$$R = \rho \cdot \frac{L}{S} =$$

$$1.1 \cdot \frac{40 \cdot 10^{-2}}{196.35 \cdot 10^{-3}} = 2.24 \Omega$$

$$S = \pi \cdot r^2 =$$

$$\pi \cdot \left(\frac{0.5}{2}\right)^2 = 196.35 \text{mm}^2$$

- choose different positions for the ball using $r(n)$.
- Make the system respond slower or quicker, with increased or reduced accuracy, with more or fewer tendency to oscillation, and so on, by changing k_p , k_d and k_i .
- study the system's maths and adjust the constants for determined starting premises.

About Windows

MS Windows is not a real-time operating system. In fact, it's constantly waiting for events coming from peripherals (keyboard, mouse, etc.) and from applications. This can affect our system's sampling frequency F_s hence cause irregularities in the operation (the Ball & Beam Interface Card LED will be our witness).

To counteract this inconvenience as much as possible, certain precautions must be taken:

- Use a PC with fast CPU and a vast amount of RAM memory.
- Execute the Ball & Beam PC program only. Pull the plug on MSN & Co.
- Give your application a high level of priority in the Windows multitasking scheme (this is done by the program).
- While the Ball & Beam PC program application is executing, do not maximize not minimize windows or push the Start button, etc. Allow the PC to interact with the application only.

If you stick to the above guidelines, the sampling frequency will be practically free from irregularities.

If something does not properly work


If something does not work, take some time to read this section, it will help you locate the cause either in the PC program, the interface card, or the mechanical assembly.

First, make sure of a running, fully updated Windows XP or Vista. Ball & Beam does not work under Windows 2000 or lower. Also check if you have the latest update of .NET Framework (from version 3.5).

The executable program Ball_Beam.exe is in the same folder as mpusbapi.dll and XYGraph.dll. To run the program under Windows Vista, right-click on 'Ball_Beam.exe' and from the context menu choose 'Execute as Administrator'.

(ICM)7555 astable multivibrator

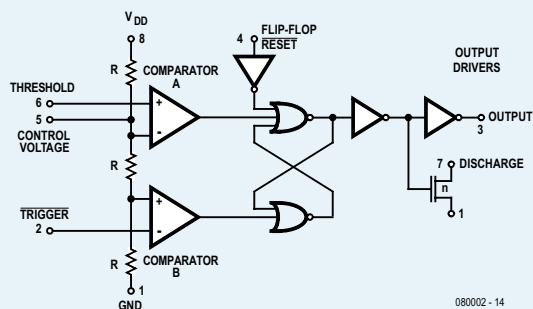
The (ICM)7555 chip is the CMOS low-power version of the renowned LM555/NE555. With it, RC timers can be easily designed. Its functional schematic is given below.



For some later calculations, it is necessary to know the value of R. For the present application, measurements indicate that a value of 100 kΩ is best.

The signal generated by the astable multivibrator around IC1 is periodical but with the High level time much longer than the Low level time. The Low level pulse is used for triggering a second 7555 (IC2) wired as a monostable multivibrator.

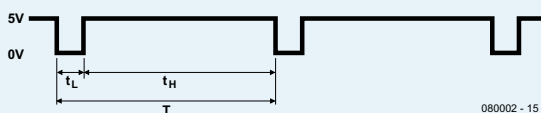Theoretically, the signal the astable should supply at its output (pin 3 of IC1) is:



$$t_H = (R10 + R11) \cdot C6 \cdot \ln 2 = (270k + 1k5) \cdot 100n \cdot 0.69 = 18.7ms$$

$$t_L = R11 \cdot C6 \cdot \ln 2 = 1k5 \cdot 100n \cdot 0.69 = 103.5 \mu s$$

$$T = t_H + t_L = 18.7ms + 103.5 \mu s = 18.8ms$$

$$F = \frac{1}{T} = \frac{1}{18.8ms} = 53.2Hz$$

The actually measured values are:

$$t_H = 18 ms$$

$$t_L = 100 \mu s$$

$$T = t_H + t_L = 18.1ms, \text{ hence } F = 1/T = 55.2 Hz$$

The program has been successfully tested on Windows XP and Vista PCs without encountering any problem. However, the program may indicate some error if there is a problem with the USB Data Acquisition Card. If so, go back to ref. [1]. Note that a correction was published for the project.

If the program is modified, it must be compiled again with the Visual C++ 2008 Express Edition — do not use the 2005 version. Besides, you should have NET XYGraph and Visual C++ 2008 Express Edition, all correctly registered.

The program needs a screen resolution of at least 1280×1024 so send the old 15 inch CRT off to recycling along with the 486 or Win98 PC.

On the Ball & Beam Interface Card it may happen that it is impossible to get the adjustment done properly. This is probably due to tolerances, mainly in the internal voltage divisor of the (ICM)7555 or TLC555 integrated circuit (in the prototype we used a Philips IC). With an oscilloscope, check up the signal on IC1 pin 3 (0 V and 5 V levels, frequency between 50 Hz and 60 Hz, low level of some 100 μs). If not, IC1 is probably at fault or you have mounted a wrong component value.

If it proves impossible to get the 'C' arm horizontal by adjusting P1, change C8 to a different value (47 nF or 150 nF). If during the start-up the 'C' arm is noticeably higher than 30-50° relative to the base, try different values for R4 and R5 (68 kΩ or 100 kΩ).

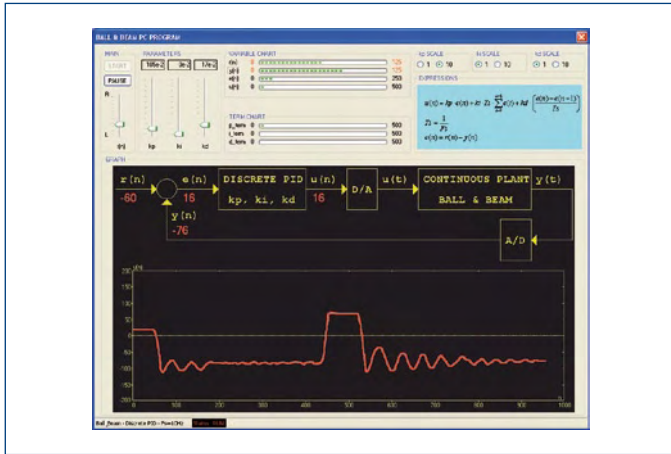


Figure 5. The Ball & Beam PC software in action.

Food for C++ programmers and quite a lot to tweak to get the ball stable on the beam!

If it's


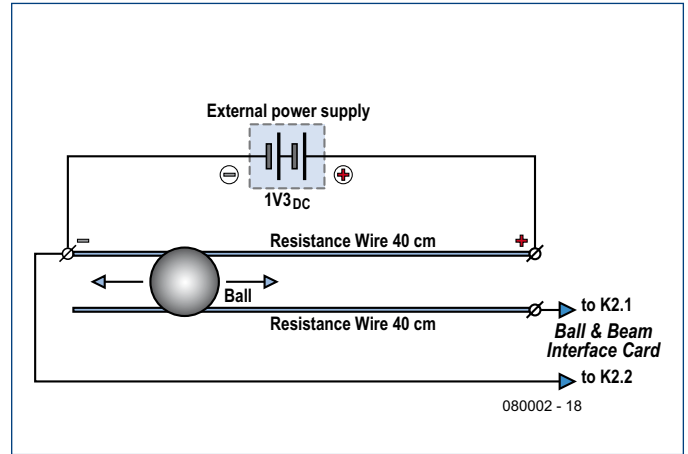


Figure 6. The position of the ball on the beam is read by a DIY rheostat or wire potentiometer.

Monostable IC2 dimensioning

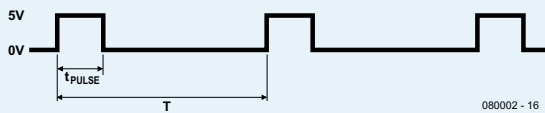The expected signal at the monostable output (pin 3 of IC2) is:



Allowing for a little headroom at either extreme, the servo timing range of 1.0 - 2.0 ms is calculated from

$$t_{PULSE} = \frac{C8 \cdot U_{CV}}{I_{Q1}}$$

$$U_{CV} = 5 \cdot \frac{(2 \cdot R) \parallel R6 \parallel (R4 + R5)}{R + [(2 \cdot R) \parallel R6 \parallel (R4 + R5)]} + U_{CCP1} \cdot \frac{R \parallel R6 \parallel (2 \cdot R)}{(R4 + R5) + [R \parallel R6 \parallel (2 \cdot R)]} = 1.65 + 0.54 \cdot U_{CCP1}$$

R=100K

$$I_{Q1(\alpha=0.2)} = \frac{\left(\frac{5 \cdot R7}{R9 + R7} - U_{\gamma} \right)}{(R8 + \alpha \cdot P1)} = 203 \text{ A}$$

U_γ=0.6V

$$t_{PULSE} = \frac{C8 \cdot U_{CV}}{I_{Q1}} = \frac{100nF \cdot (1.65 + 0.54 \cdot U_{CCP1})}{203 \text{ A}} = \begin{matrix} 0.8ms @ U_{CCP1} = 0V \\ 1.5ms @ U_{CCP1} = 2.5V \\ 2.1ms @ U_{CCP1} = 5V \end{matrix}$$

Note that the variation of t_{PULSE} is linear with respect to U_{CCP1} . In practice, the pulse durations obtained after adjusting P1 are well within the range 1ms to 2ms.

been necessary to change C8, R4 and R5, check the signal at IC2 pin 3 (levels 0 V and 5 V, frequency between 50 and 60 Hz, high level of 1.5 ms). For this last measurement, the Ball & Beam PC program has to be halted (Status: STOP) and P1 adjusted to reach the indicated 1.5 ms.

If everything is correct so far, ask yourself if the Ball & Beam Interface Card and the servo are properly powered, the latter from the 5 V / 1 A supply. Finally, are you powering the wire potentiometer with an external power supply of approximately 1.3 V and a minimum current of 1 A? If so, all that's left to do is verify the mechanical assembly.

(080002-1)

PID maths

$$u(n) = k_p \cdot e(n) + k_i \cdot T_s \cdot \sum_{i=0}^{n-1} e(i) + k_d \cdot \left(\frac{e(n) - e(n-1)}{T_s} \right)$$

$$T_s = \frac{1}{F_s}$$

$$e(n) = r(n) - y(n)$$

Reference

[1] USB Data Acquisition Card, Elektor November 2007. www.elektor.com/070148

About the Authors

Jose Luis Rupérez Fombellida and José Manuel Escobosa Bravo are teachers in electronics at San Blas Secondary School, Madrid, Spain.

We add value to PCBs
when others just sell them.

- One Stop Manufacturing Service
- Free Electronic Components
- Free Prototyping Assembly
- Professional Consultant



Blank PCBs don't work

We make working PCBs

WWW.EZPCB.COM

PCB-FPC-Rigid Flex PCB-Assembly-Keypads-Enclosures-Components-Cables-Metal Fab-Consultant

www.EzPCB.com

Email: sales@ezpcb.com

DCC Command Stati



Digital model control with the ARM7

Patrick Smout

Electronics is making more and more inroads into the domain of model trains. Trains are now controlled with digital codes, and in many cases the entire system can be operated from a computer. In this article we present a design for the device that forms the heart of a digitally controlled model railway: the DCC Command Station. The computing power in this design is provided by a high-performance ARM7 processor.

One of the key elements of a modern digitally controlled model railway is the control unit that produces the digital signals for controlling the locomotives. This device also has several secondary functions, such as communicating with a PC.

This article describes a control unit (called a 'Command Station' in model railway jargon) that employs the DCC standard and is built around a powerful ARM7 processor, which is also used on the *Elektor* 'ARMee' board.

First a brief introduction to the topic. With conventional analogue control of a model railway system, the speed of the locomotives is adjusted by varying the voltage on the track. The simplest arrangement consists of a transformer and a potentiometer, possibly complemented by a rectifier. More advanced systems use pulse-width modulated (PWM) signals. The principal advantage of this approach is improved running characteristics. This is quite nice, but even with these systems it is very

difficult to control other functions in a locomotive, such as sound effects or a smoke generator.

If a decoder is fitted in the locomotive and the transformer is replaced by an electronic control unit with a track booster, we enter the realm of digitally controlled model railways.

The electronic controller that makes all this possible is called a 'Command Station'. The Command Station described here is suitable for systems that employ what is called the 'DCC standard'. DCC is not the only method for digital control of model railways, but it is one of the few methods that is not tied to a specific manufacturer.

The advantages of digital train control can be summarised as follows:

- Dramatically improved locomotive running characteristics, especially at low speeds and on uphill grades.
- Individually switchable auxiliary functions in locomotives, such as sound effects, smoke generators, remote

decoupling, and lighting (including when the train is standing still).

- Several trains can travel on the track or in the same block at the same time.
- A computer can be added for easy automation of control and protection functions.

An additional benefit of the system described here is:

- The standard is widely used, so products from different suppliers can be used 'mix and match' in the same system.

A brief history of DCC

Despite what you might think, DCC (which stands for 'Digital Command Control') is not new. The history of DCC goes back to the late 1980s. At that time a working group of the National Model Railroad Association (NMRA), an umbrella organisation of model railway enthusiasts in the USA, was looking for a standard that could be used

on micro



for digital control of model trains. The commercially available systems at that time were proprietary and mutually incompatible.

After an extensive study of the available systems and a few diversions, in the early 1990s the NMRA decided on a system developed by Lenz, a German company. Reliable data transfer and interference-free operation were naturally the most important criteria for their choice. In addition, the new standard had to be able to evolve with the available technology and satisfy new requirements arising in the model

railway world. The requirements and expectations that the new standard must fulfil were specified by the DCC working group of the NMRA in documents called 'Standards' and 'Recommended Practices' (RPs). The electrical properties that the signals must fulfil, as well as the form and content of the transferred data, are defined precisely. Among other things, the recommended practices define the requirements that must be met by the digital boosters that supply power to the model railway.

Structure of a digitally controlled model railway

A digitally controlled model railway consists of the following functional blocks (see **Figure 1**):

- **Transformer.** Every system needs a source of power.

- **Decoder.** This processes the signals that originate from the Command Station and are placed on the track by the booster. A decoder can be fitted in a locomotive, but it can also be used in a fixed location for controlling components such as turnouts and signals (in the latter case, it is called an accessory decoder). A remarkable aspect of these decoders is that they receive power and digital signals via the same leads, so there is no need for separate power leads. As each decoder has a unique, configurable address, it is easy to connect several decoders to the same track. Each decoder only responds to the information intended for it.

- **Occupancy feedback detectors.** These are used to keep track of which parts of the track are occupied or free. For this purpose, the track is divided into a number of small sections, with one rail of each section electrically insulated from the adjacent sections. The insulated rail of each section is connected to an occupancy feedback circuit. In its simplest form, this is a current detector. If a section is occu-


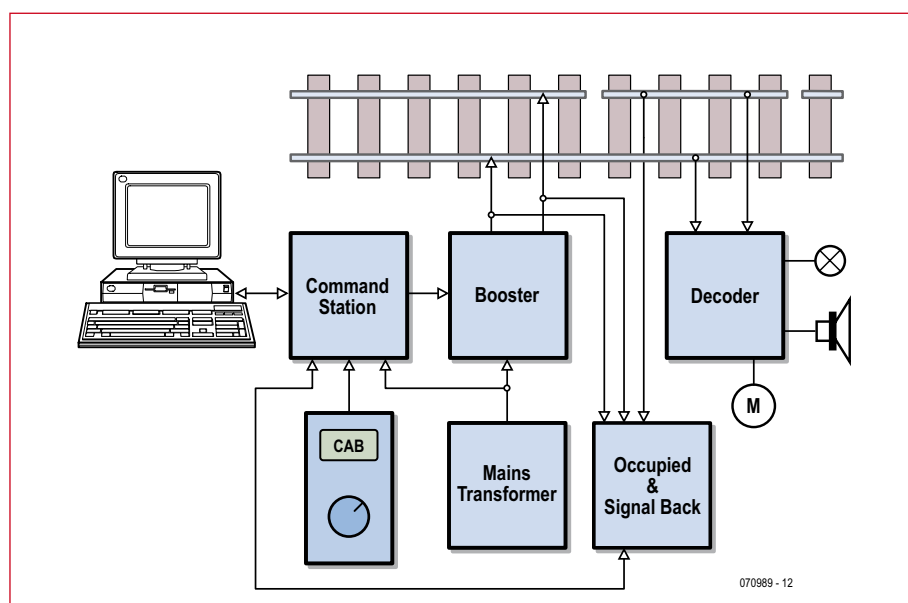



Figure 1. Block diagram of a model railway system with digital control.

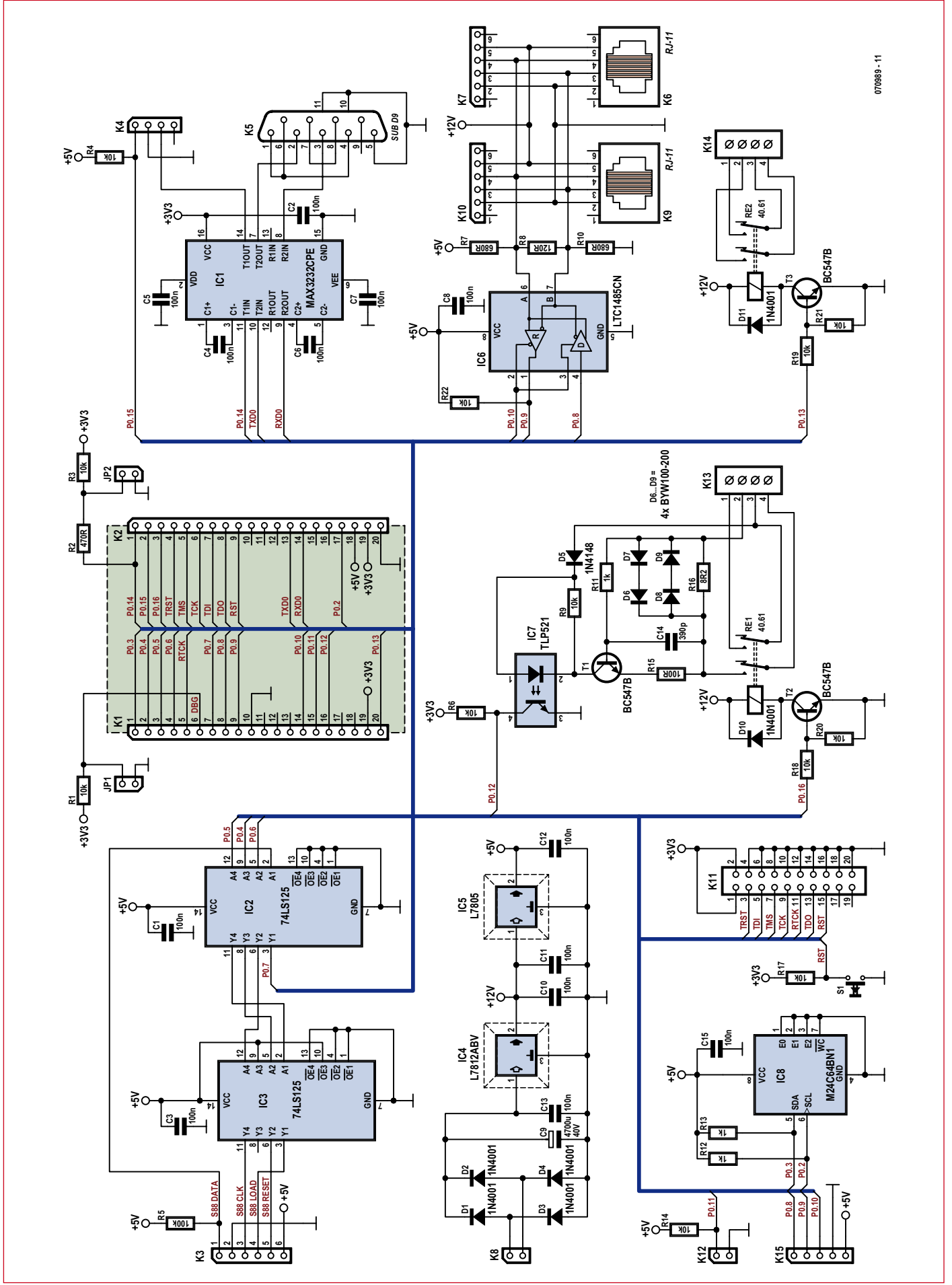

070989 - 11


With useful implemented peripherals, plentiful practical code examples and a broad set of add-on boards, mikroElektronika development boards make fast and reliable tools that can satisfy the needs of experienced engineers and beginners alike.

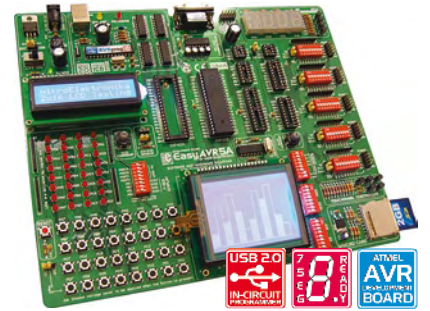EasyAVR5A with on-board USB2.0 programmer



The system supports 8, 14, 20, 28 and 40 pin microcontrollers (comes with ATMEGA16). Each jumper, element and pin is clearly marked on the board. It is possible to test most industrial peripherals on the system: temperature controllers, counters, timers etc. Touch screen controller with connector is available on-board. EasyAVR5A is an easy-to-use Atmel AVR development system. On-board USB 2.0 programmer makes your development easy. Examples in BASIC and Pascal language are provided with the board.

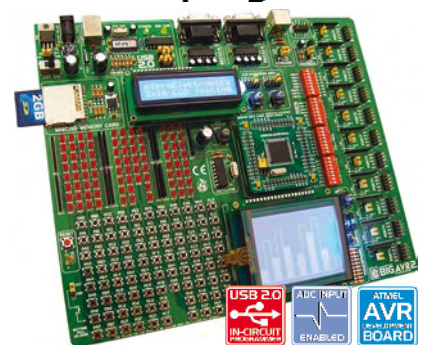





BIGAVR2 with on-board USB2.0 programmer



The system supports 64-pin and 100-pin AVR microcontrollers (comes with ATMEGA128 working at 10MHz). Ready to go examples guarantee successful use of the system. BIGAVR2 is an easy to use Atmel AVR development system. BIGAVR2 has many features that makes your development easy. You can choose between USB or External Power supply. BIGAVR2 also supports Character LCD as well as Graphic LCD. Touch screen controller with connector is available on board.

Add-On Boards

A wide range of additional daughter-boards for development systems

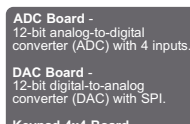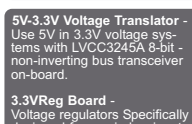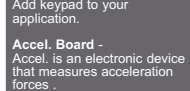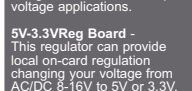 <p>ADC Board - 12-bit analog-to-digital converter (ADC) with 4 inputs.</p>	 <p>5V-3.3V Voltage Translator - Use 5V in 3.3V voltage systems with LVCC3245A 8-bit non-inverting bus transceiver on-board.</p>
 <p>DAC Board - 12-bit digital-to-analog converter (DAC) with SPI.</p>	 <p>3.3VReg Board - Voltage regulators Specifically designed for use in low input voltage applications.</p>
 <p>Keypad 4x4 Board - Add keypad to your application.</p>	 <p>5V-3.3VReg Board - This regulator can provide local on-card regulation changing your voltage from AC/DC 8-16V to 5V or 3.3V.</p>
<p>Accel. Board - Accel. is an electronic device that measures acceleration forces.</p>	

Please visit our web page for more info
<http://www.mikroe.com>

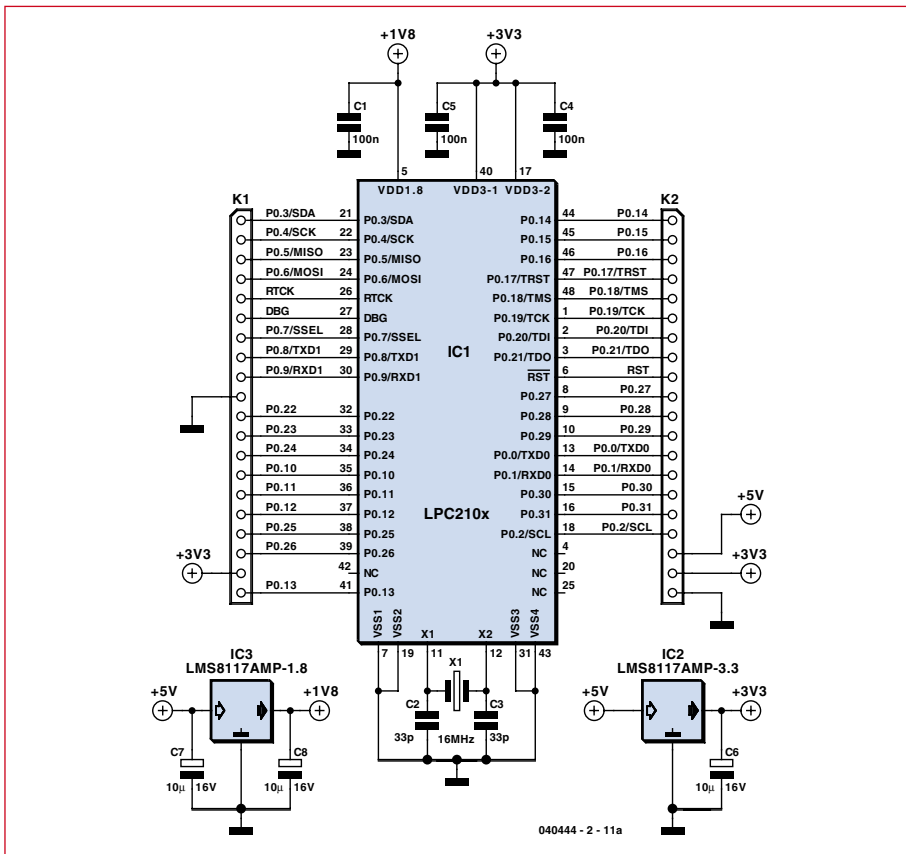


Figure 2b. Schematic diagram of the ARM module.

plied, there will be a measurable current consumption (even if it is relatively small). The measured signal is usually sent to the Command Station in the form of a binary signal.

- **Hand controller** (also called a cab controller, after the driver's cab of a locomotive). The hand controller replaces the traditional rotary knob on the transformer, and it also provides some extra functions, such as switching lights and sound effects on and off. Each controller can control its own locomotive, but it is also possible to operate several locomotives with a single controller.

- **PC**. Although a PC is not absolutely necessary, including a computer in the system adds a lot of extra scope to digital model railroading. In the simplest case, it can be used to display the track occupancy data. Naturally, a lot more is possible. There are various software packages available, both commercial and free, that can handle the entire control and protec-

tion functions of a railway. This certainly doesn't have to spoil the fun of a model railway – while you are piloting a goods train through the marshalling yard just like a real engine driver, the PC ensures that no disasters occur in other parts of the system.

- **Booster**. As a respectable model railway system can consume a considerable amount of current, one or more boosters are used to supply power to the track. If several boosters are used, they are all driven from the same Command Station. In this case, each booster supplies power to a portion of the track system.

- **Command Station**: the heart of the system. Its most important task is generating the digital signals that control the locomotives and all other digital components in the railway system. In addition, the Command Station looks after communication with one or more hand controllers, which are usually connected to a bus. The bus used here is called XpressNET, which is a polled single-master EIA 485 bus. A link to the occupancy feedback detectors is also essential. A separate bus can be used for this purpose, but in

Figure 2a. Schematic diagram of the DCC Command Station. The ARM module is fitted onto connectors K1 and K2.

DCC: what and how

A DCC signal consists of an AC voltage in which the digital information is encoded in the lengths of a series of pulses.

The half-bit time for a '1' bit is 58 μs, so the transmission time for a '1' bit is 116 μs.

The half-bit time for a '0' bit is at least 100 μs. In principle, the two half-bit times for a '0' bit should be the same to avoid producing a DC potential on the track. However, the standard allows the stretching of '0' bits in order to intentionally superimpose a DC voltage on the traction voltage. This can be used to operate an analogue locomotive without a decoder on the track at the same time. This possibility is not utilised in the Command Station described here, and the half-bit time for a logic '0' is set to a fixed value of 116 μs. The transmission time for a '0' bit is thus 232 μs with this Command Station.

Messages are sent in the form of data packets. The structure of a standard packet can be described briefly as follows:

- Preamble: a series of at least 14 '1' bits preceding the start of a new packet.
- Packet Start Bit: a '0' bit that marks the end of the preamble and the start of the address.
- Address Byte: a series of 8 bits that indicates the address (or part of the address) of the decoder for which the data is intended.
- Data Byte Start Bit: a '0' bit that marks the start of the data.
- Data Bytes: several groups of 8 data bits with '0' bits as separators between the groups. This part of the package contains the supplementary address, instructions, data, and a checksum.
- Packet End Bit: a '1' bit that marks the end of the packet.

Example:

An order for setting the direction of travel and the speed (in 28 individual steps) is constructed as follows:


11111111111111	0	AAAAAAA	0	01DSSSS	0	EEEEEEE	1
Preamble		Address		Instruction		Checksum	

- AAAAAAA Address of the target locomotive for the instruction
- D Direction of travel (1 = forward)
- SSSS Speed
- EEEEEEE Checksum (XOR of the previous bytes excluding the preamble – in this case [AAAAAAA] ^ [01DSSSS])

A bit stream for setting locomotive number 83 to forward motion with a speed of 0 thus takes the form:

11111111111111	0	01010011	0	01100000	0	00110011	1
----------------	---	----------	---	----------	---	----------	---

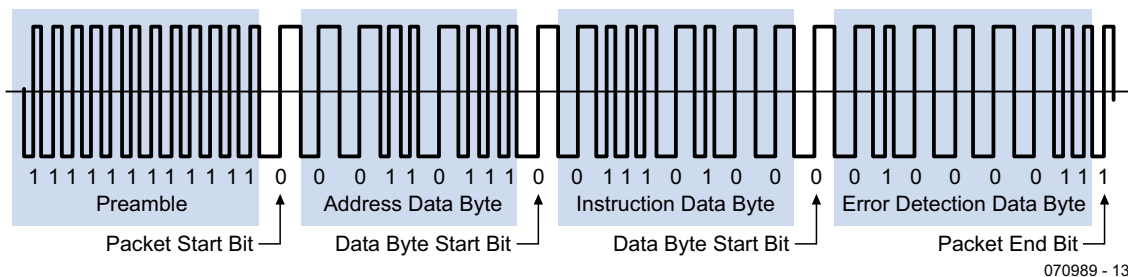The signal waveform of an order could be:



A complete description of the standard, including a summary of all the instructions, is available at the NMRA website (www.nmra.org) on the DCC working group activities page

practice these devices sometimes share the cab bus. We decided to use a separate bus for this in our design: the S88 bus.

Finally, there is the link to the computer, which in this case is an RS232 port. Thanks to the use of an open protocol that is supported by a variety of software packages, expansion is problem-free.

Schematic diagram

The circuit shown in **Figure 2** is built around an LPC2106. This is a powerful 16/32-bit NXP microcontroller based on an ARM7TDMI-S processor core with a maximum clock rate of 60 MHz. The microcontroller has 128 kB of flash EEPROM and 64 kB of RAM, which are more than adequate for quite a few projects. There are also two 16C550-

compatible serial ports, two versatile 16-bit timers, an I²C interface, and an SPI interface. A maximum of 32 I/O lines are available for connection to the outside world.

The microcontroller is shown in the middle of the schematic diagram in the form of a separate daughterboard, which some readers will certainly find familiar. This board (o/n 040444-1) was

used earlier in another *Elektor* design: the 'ARMee' project published in April 2005. Practically all important signals are fed out via two connectors (K1 and K2). The board is powered from +5 V. The 1.8-V and 3.3-V supply voltages required by the microcontroller are generated on-board. The 3.3-V supply is also made available via the connectors for I/O devices that require a lower supply voltage.

Unfortunately, the LPC2106 does not have an internal EEPROM. As quite a few things must be stored in non-volatile memory in the Command Station, we remedied this shortcoming by using a small external EEPROM (IC8, 8 k × 8). Fortunately, the link to the microcontroller is quite simple because we can take advantage of the microcontroller's standard I²C interface. As there is only one device on the I²C bus, addressing is unnecessary, so the E0, E1 and E2 address pins of the EEPROM are tied to ground. R12 and R13 are pull-up resistors, which are necessary for proper bus operation.

An RS232 interface is provided for communication with the computer. Half of a MAX3232 powered from the 3.3-V rail provides level shifting for the Transmit and Receive lines of UART 0. Using UART 0 for the computer link also provides a convenient way to download new software via the built-in boot loader. The pin assignments of K5 correspond to a DCE (such as a modem), so a standard one-to-one cable (available in every computer shop) can be used for the connection between the control unit and the computer.

The other half of the MAX3232 provides the level shifting necessary for driving an external track booster. This signal is fed out via K4. This connector also has a pin for a short-circuit feedback signal. If the signal on pin 1 is pulled to ground (by the booster), the control unit will disable the output.

The connectors for the hand controllers, which are driven via XpressNET, are located at the right. The hardware is a standard EIA 485 port implementation. Driver IC8 (LTC1485) provides the signal shaping. Resistor R8 ensures that the line is terminated properly. Although this is not especially critical at the data rate used here, it's better to be safe than sorry. Resistors R7 and R10 hold the Transmit and Receive lines in a defined state when they are not being driven by a device on the bus. This prevents the receivers from

picking up invalid data due to interference coupled into the floating bus lines. RJ-12 6P/4C modular connectors or plug-and-socket connectors can be used to connect the hand controllers to the network.


There are two relays at the bottom middle. The contacts of relay RE2 can be used to connect the traction voltage from the booster to the main line, while the contacts of RE1 can be used to connect the booster output to a separate programming track. This relay is only engaged if the Command Station receives special programming instructions from the programming software. When this happens, relay RE2 is released. This ensures that programming instructions for a locomotive on the programming track are not sent to other locomotives on the main track as well.

This difference in the intended uses of the two relays is the reason for the additional circuitry around relay RE1. This is a simple current detector that senses the acknowledgment pulses generated by the decoder during a programming session. An acknowledgment pulse is generated by causing the current consumption to rise to at least 60 mA for a defined time (approximately 6 ms), for example by briefly switching on the motor. The presence (or absence) of these acknowledgment pulses enables the control unit to put together the response from the decoder. The decoder current flows through R16 during the programming session. This resistor thus determines the sensitivity of the detector. Four fast diodes (two pairs of diodes connected head to tail, since the track booster supplies an AC voltage) limit the voltage across the sense resistor to twice their forward voltage drop. Two diodes connected in series are used here to ensure that T1 can be driven into conduction at a suitable level. R11 and C4 form a low-pass filter that suppresses noise pulses. The LED in optocoupler IC7 is driven by the signal on the collector of T1. The collector current, and thus the current through the LED, is determined by resistor R15. The optocoupler (which provides electrical isolation from the traction voltage) supplies the ack pulses to the microcontroller.

Connector K11 is used for the JTAG port. S1 is reset button. If you want to develop your own software for this

With useful implemented peripherals, plentiful practical code examples and a broad set of add-on boards, mikroElektronika development boards make fast and reliable tools that can satisfy the needs of experienced engineers and beginners alike.

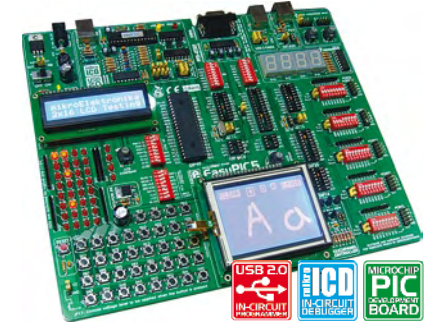EasyPIC5 with on-board In-Circuit USB2.0 programmer & debugger



EasyPIC5 supports 8-, 14-, 18-, 20-, 28- and 40-pin PIC microcontrollers (comes with the PIC16F887). The mikroICD (In-circuit Debugger) enables very efficient debugging. Examples in C, BASIC and Pascal language are provided with the board. EasyPIC5 comes with the following printed documentation: EasyPIC5 Manual, PICFlash2 Manual and mikroICD Manual.

BIGPIC5 with on-board In-Circuit USB2.0 programmer & debugger



System supports the latest (64) and 80-pin PIC microcontrollers (comes with PIC18F8520). Many of ready to go examples in C, BASIC and Pascal language guarantee successful use of the system. A Touch screen controller with connector is available on board. This development board has an on-board ultra fast USB 2.0 programmer, mikroICD (In-circuit Debugger) and integrated connectors for MMC/SD memory cards, 2 x RS232 port, RS485, CAN, on-board RTC, PS/2 connector, DAC etc...

Add-On Boards

A wide range of additional daughter-boards for development systems



- Digital POT** - MCP41010 SPI Interfaced digital potentiometer.
- SmartMP3 Board** - VS1001k MP3 decoder with SPI Interface.
- Serial 7-seg Display 2 Board** - MAX7219 SPI Interfaced, LED Display Drivers with 8 Common-Cathode LED Displays
- LightToFreq Board** - TSL230BR programmable light-to-frequency converter.
- CAN-1 Board** - Interfaces CAN via MCP2551.
- CANSPI Board** - Makes CAN network with SPI interface.
- RS485 Board** - Connects devices into RS-485 network
- Serial Ethernet** - Make ethernet network with SPI Interface (ENC28J60).

Please visit our web page for more info
<http://www.mikroe.com>

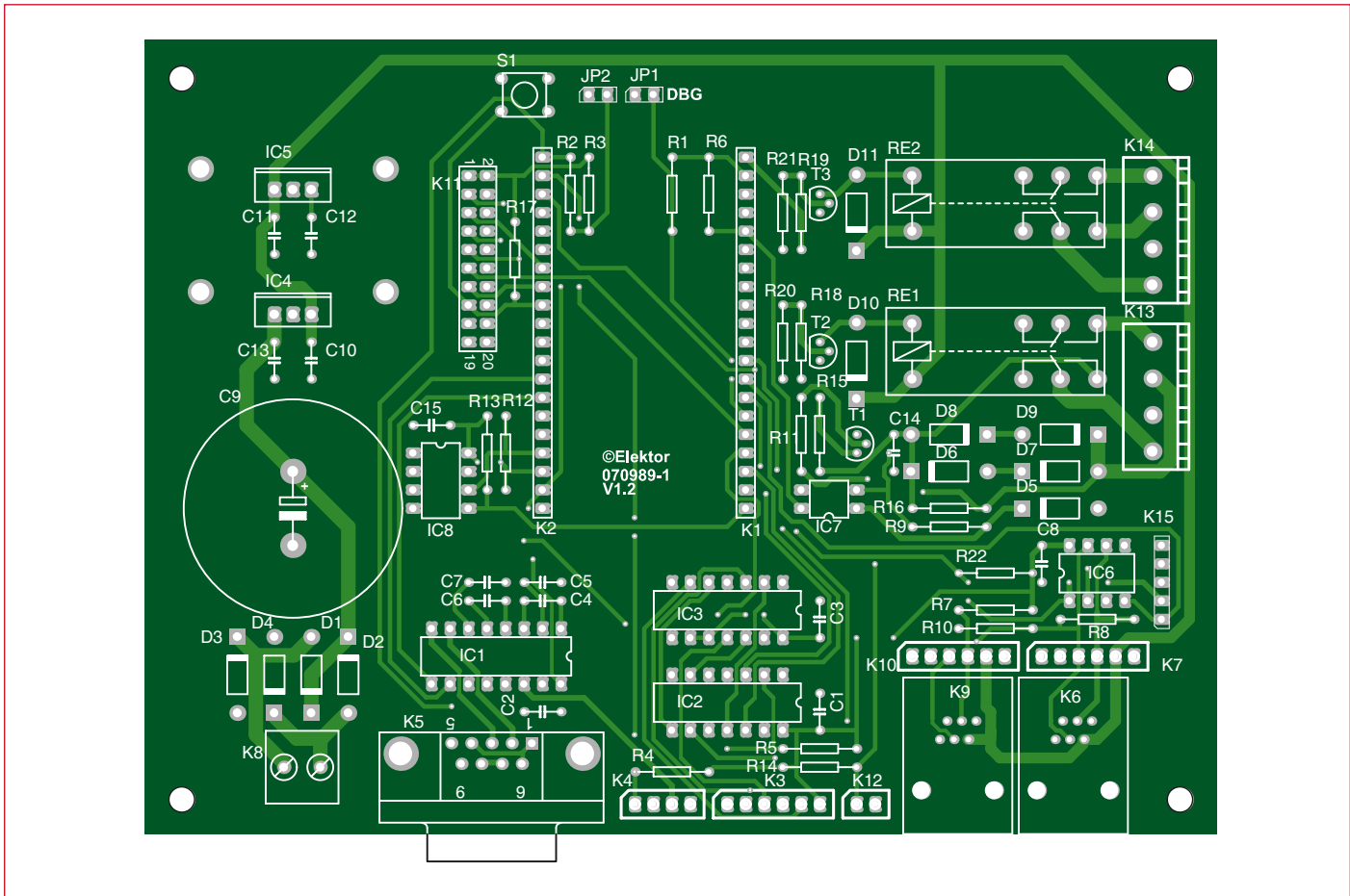


Figure 3. The PCB is designed with a spacious layout to make assembly easy.

project and you have the right tools, you can use this port for downloading and debugging the program code. It is not used during normal operation in and around a model railway. The circuit is powered by a transformer with a secondary voltage of 13 to 14 V connected to K8. A transformer rated at 16 to 20 VA is more than adequate.

A standard model train transformer is not especially suitable for this purpose, since it has a slightly higher output voltage (14–16 V_{AC}), which will cause IC4 to become rather warm. The transformer voltage is full-wave rectified by a set of four diodes, and the DC voltage is smoothed by C9. This voltage is then reduced in two stages, first to

+12 V and then to +5 V. The 12-V supply voltage is used directly to power the two relays and the hand controllers connected to the XpressNET bus. The +5-V supply voltage powers the microcontroller and its peripheral logic. Four ceramic capacitors provide effective suppression of undesirable oscillations.

COMPONENTS LIST

Resistors

R1,R3,R4,R6,R9,R14,R17-R22 = 10kΩ
 R2 = 470Ω
 R5 = 100kΩ
 R7,R10 = 680Ω
 R8 = 120Ω
 R11,R12,R13 = 1kΩ
 R15 = 100Ω
 R16 = 8Ω2

Capacitors

C1-C8,C10=C13,C15 = 100nF
 C9 = 4700µF 40V radial
 C14 = 390pF

Semiconductors

D1-D4,D10,D11 = 1N4001
 D5 = 1N4148

D6-D9 = BYW100-200
 T1,T2,T3 = BC547
 IC1 = MAX3232CPE
 IC2 = 74HCT125
 IC3 = 74LS125
 IC4 = 7812
 IC5 = 7805
 IC6 = LTC1485CN
 IC7 = TLP521-1
 IC8 = 24C64

Miscellaneous

S1 = pushbutton, 6mm, PCB mount
 RE1,RE2 = 12-V relay, 2x changeover, e.g. Finder type 40.52
 Heatsink, Fischer type SK104, 25mm, for IC5
 Heatsink, Fischer type SK104, 35mm, for IC4
 K1,K2 = 20-way SIL socket

K3,K7,K10 = 6-way SIL pinheader
 K4 = 4-way SIL pinheader
 K5 = 9-way sub-D socket (female), angled pins, PCB mounting
 K8 = 2-way PCB terminal block, lead pitch 5mm
 K6,K9 = 6P4C modular connector, PCB mount, e.g. Hirose TM5RE1-66
 K11 = 20-way DIL pinheader
 K12,JP1,JP2 = 2-way pinheader
 K13,K14 = 4-way PCB terminal block, lead pitch 5mm
 K15 = 5-way SIL pinheader
 ARM CPU module (unprogrammed); Elektor SHOP item **040444-91**
 PCB, Elektor SHOP item **070989-11**
 Kit of parts incl. programmed ARM module; Elektor SHOP item **070989-71** (see www.elektor.com)

The circuitry around IC2 and IC3 is used to read the data from the S88 feedback detectors. The S88 bus is designed as a giant shift register composed of the S/R flip-flops of the individual feedback detectors, which register their 'occupied/free' status until they have been read out serially. Most of this work is done by software running in the microcontroller. The contribution of the hardware to this process is limited to buffering the control signals. IC3 buffers the outgoing signals (Clk, Load, and Reset), while IC2 buffers the incoming signal (Data). The serial data is clocked in at rate of 5 kHz. With the maximum number of detectors that can be connected to the bus (4096 inputs), this means that a full set of inputs can be read 10 times each second.

This all works as follows:

- Data supplied to the feedback detectors in parallel format is loaded from the S/R flip-flops into the shift register by setting the Load signal high and issuing a clock pulse on the Clk line.
- The S/R flip-flops are reset by setting Reset High, after which they are ready to register new data.
- The microcontroller then reads in the serial data by issuing a series of clock pulses on the Clk line.

These signals are output by a 6-way connector (K3). The +5-V supply voltage on this connector is used to power the connected feedback detectors.

Finally, there is one more connector (K15) at the bottom left of the drawing. It supports an alternative bus for the hand controllers and feedback detectors. Stay tuned for more information about this.

PCB assembly

The PCB layout for the Command Station is shown in **Figure 3**. Assembling the board is quite straightforward, as there are no components that require special attention. If you allow yourself sufficient time and work attentively, you are bound to achieve a good result. Fit the low-profile components first, followed by the high-profile components. As the final step, solder the electrolytic capacitor, IC4 and IC5 with their heat sinks, and relays RE1 and RE2.

It is advisable to fit IC1, IC2, IC3 and IC6 in sockets, since they provide the interfaces to the outside world. They

bear the brunt of any inadvertent short circuit, and you can replace them easily if they are fitted in sockets. The following components are optional:

- JP1 and K11 can be omitted if you do not intend to use the JTAG interface.
- For K7/K8 and K9/K10, fit only the connector or connectors that you personally prefer. All four of these connectors are wired in parallel.

Initial use and testing

Connect the transformer to K8 and switch on the mains voltage. Check the +5-V supply voltage (e.g. between pins 5 and 8 of IC6) and the +3.3-V supply voltage (e.g. between pins 15 and 16 of IC1).

The next step is to download the application code to the DCC Command Station. You can use a standard NXP tool for this (LPC2000 Flash ISP Utility). This tool enables you to download code to the processor via the PC serial port. The instructions for using this tool are described in detail in the supplementary information for this article on the *Elektor* website. You can also download the hex code for programming the processor from the website. Alternatively, if you buy the *Elektor* kit for this project you will receive a pre-programmed module.

When the Command Station is started up the first time, it reconfigures the non-volatile data stored in the EEPROM. This can take a while (around 20 seconds), so you can take a short break before continuing with the next step.

Now connect a pushbutton with a make contact (normally-open) between the two pins of K12. This is the Stop / Go / Cold Start button.


If you press this button, relay RE2 should engage so the digital signal for driving the booster is present on connector K4. Now the DCC Command Station is ready for normal operation. If you press the button again, relay RE2 is released, and the digital signal is no longer routed to K4.

You can also use the pushbutton to perform a system reset. If the Command Station stops responding, even after the supply voltage is interrupted,

With useful implemented peripherals, plentiful practical code examples and a broad set of add-on boards, mikroElektronika development boards make fast and reliable tools that can satisfy the needs of experienced engineers and beginners alike.

UNI-DS3

UNIVERSAL DEVELOPMENT TOOL

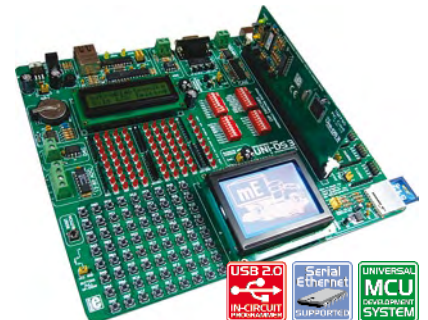

Thanks to many features **UNI-DS3** is the world's easiest to use development board for different types of microcontrollers. The system supports **PIC, dsPIC, AVR, 8051, ARM and PSoC** microcontrollers with a large number of peripherals. In order to continue working with different chip in the same development environment, you just need to switch a card. You can choose between USB or External Power supply. Each MCU card has its own **USB 2.0** programmer!

PICPLC16B


with on-board In-Circuit **USB 2.0** programmer & debugger



Minimize your time from prototype to final product by using the market-proven **PICPLC16B** development board. **PICPLC16B** is a system designed for controlling industrial systems and machines. 16 inputs with **optocouplers** and 16 **relays** (up to 10A) can satisfy most industrial needs. The ultra fast **mikroICD** (In-Circuit Debugger) enables very efficient debugging and very fast prototype development. Features: **RS485, RS232, Serial Ethernet, USB 2.0** programmer and **mikroICD** (In-Circuit Debugger) are available on-board.

Add-On Boards

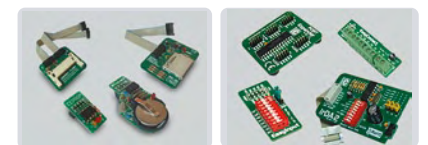A wide range of additional daughter-boards for development systems



CF Board - Easy way to use Compact flash in your design.

MMC/SD Board - Easy way to use MMC and SD cards in your design.

EEPROM Board - Serial EEPROM board via I2C interface.

RTC Board - PCF8583 RTC with battery backup.

EasyConnect Board - Connects your peripherals easily and fast using connectors.

IrDA2 Board - Irda2 serves as wireless RS232 communication between two MCU's.

Port Expander Board - MCP23S17 is the 16-bit port expander with SPI interface.

EasyInput Board - Make input levels easy and fast using high quality DIP switch.

Please visit our web page for more info
<http://www.mikroe.com>

you can restore it to proper operation by holding the button depressed while switching on the power. This causes all non-volatile data stored in the Command Station to be reset to its default values. This process takes approximately 20 seconds.

Now you're ready to connect the Command Station to the track booster. You can use a DIY booster, such as the one described already in *Elektor* (EEDTs or EEDTs Pro Booster), or you can use a commercial model (such as the Lenz LV102). The basic setup requires two leads to be connected between the Command Station and the booster: 0 V from pin 2 of K4 and the DCC signal from pin 3. The short-circuit feedback signal can be connected to pin 1 if desired. When a short circuit occurs, this pin must be pulled to ground, which causes the Command Station to disable the digital signal.

Control software

Various programs are available for using the Command Station described here with a PC to control a model railway system. There is a very nice 'native Dutch' program available called 'Koploper', which is entirely free (www.pahasoft.nl). It is supported by an active forum where users can find answers to their questions (www.koploperforum.nl). We're sure these users won't mind the odd question in English.

You can use the 'PT' program (also a Dutch product) to program DCC decoders. This program also provides extensive functions for testing feedback detectors and accessory decoders. You'll find it at <http://people.zeelandnet.nl/rossoft>.

You can also use ADaPT (Advanced Driving and Programming Tool) from STP Software (www.stp-software.at) to program decoders. Although this software (available in English and German versions) is not free, it can also be used for locomotive management.

Of course, you can also take on the challenge of writing your own software. A sample program for Microsoft Visual Studio Express 2008 is available and can be downloaded free of charge from the project page on the Elektor website.

Let us and other readers know how you get on — a simple message in the *Elektor* forum does the trick.

(070989-1)

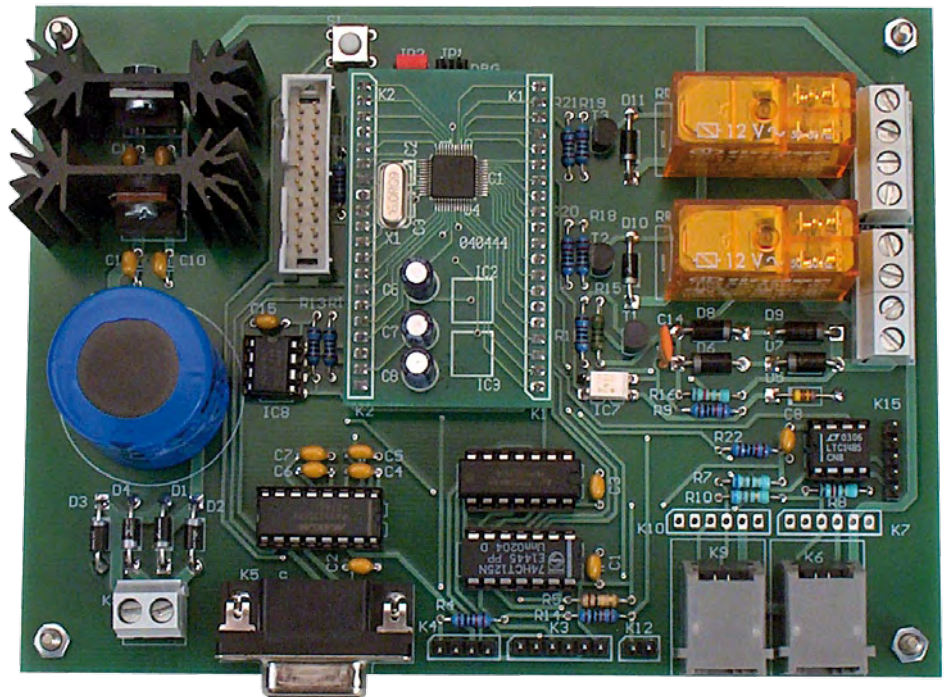


Figure 4. Fully assembled prototype with the ARMeE module installed.

Web Links

- DCC:** www.nmra.org/standards
- XpressNET:** www.lenz.com
- P50x:** www.uhlenbrock.com
- Koploper:** www.pahasoft.nl
- PT:** <http://people.zeelandnet.nl/rossoft>
- NXP:** www.nxp.com

About the author

After the completion of his studies in Telecommunication & Microprocessors, Patrick Smout has been actively involved in electronics product development (hardware and software) since 1985. In recent years his focus has moved away from hands-on engineering, and he is now the coordinator of the development department.

His first electronic construction projects included the Elektor Junior Computer and all of its subsequently published extensions. These were complemented by DIY extensions, such as a graphics card.

His hobbies are model trains and (naturally) electronics and embedded software.

According to Patrick, the nicest thing about this profession is seeing how a design slowly comes to life, right from the incipient stage, and then watching it travel around the world as a full-fledged product.

E-mail: dcccommandstation@versateladsl.be





850A+ SMD Rework Station



Online Price £44.95

932 Vacuum Pick Up Station



Online Price £29.95

937+ 45W Soldering Station



Online Price £37.95

Range Of Tools & Accessories



2738 CPU Controlled PCB Work Station



Online Price £139.95

Kit Includes:
Hot Air Gun
6 x Air Nozzles
70W Soldering Iron with Fume Absorber
Soldering Iron Stand
Soldering Iron Tip with Heating Element
Vacuum Suction Pen
Heat Resistant Pad
IC Removal Tool
2 x Carbon Filters

2900 70W Soldering Station



Online Price £74.95

Soldering Iron Tips & Air Nozzles



Wide Selection Available

853A Quartz Infrared Preheater



Online Price £69.95

950 SMD Hot Tweezers & Station



Online Price £44.95

710 Infrared Welding Station



Online Price £750.00

TEST-PINS.CO.UK

Suppliers of Test-pins, Receptacles & Probes...



For Test-pins & Probes
Visit www.test-pins.co.uk
Above discount code also applies

www.pcb-soldering.co.uk

Allendale Electronics Ltd, 43 Hoddesdon Industrial Centre, Pindar Road, Hoddesdon, Hertfordshire. EN11 0FF.

T: +44 (0)1992 450780 W: www.pcb-soldering.co.uk
F: +44 (0)1992 450781 E: sales@pcb-soldering.co.uk

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

1 EUROCARD

(160 x 100 mm)

+ Tooling

+ Photoplots

+ VAT

€49

Price example
Any size and contour possible!

Optional:

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

FREE LAYOUT SOFTWARE!



Freephone **0800-3898560**

Tel.: +353 (0)61 701170
Fax: +353 (0)61 701165
pcb-pool@beta-layout.com

Over 18,000 Customers

LEAD FREE



Simply send your files and order ONLINE:

PCB-POOL.COM

PEAK electronic design ltd

tel. 01298 70012
fax. 01298 70046
www.peakelec.co.uk
sales@peakelec.co.uk

Handheld Test Gear - Cool, Smart.

Atlas DCA **£55**



Atlas DCA Model DCA55
Semiconductor Analyser
Identifies type and pinout!

Atlas ESR **£85**



Atlas ESR Model ESR60
ESR and Capacitance Meter
Resolution of 0.01 ohms!

Atlas LCR **£79**



Atlas LCR Model LCR40
Inductor, Capacitor, Resistor Analyser
Automatic part identification.

Atlas SCR **£99**



Atlas SCR Model SCR100
Triac and Thyristor Analyser
Auto gate test current up to 100mA

UK: Please add £1.00 p&p to your order. Prices include UK VAT.
Please see website for overseas pricing.

Luxury LED Bicycle

Brighten your beam and banish burnt-out bulb blues

Dr Thomas Scherer

Having treated himself to a new bicycle fitted out with all mod cons including a shiny hub dynamo, the author was looking forward to many miles of pedalling pleasure. But then disaster struck: after just a couple of hours use the bulb in the front light burned out! Not finding the prospect of repeated replacement attractive, he set out to substitute a power LED for the bulb.

It is not in an engineer's nature to be satisfied with a simple solution, such as replacing the bulb.

It is much more satisfactory to understand the problem properly from the ground up, and of course a problem like this can be viewed as an opportunity for a good rummage in the junk box to look for components that might be useful in devising a proper solution.

Tuning up

It often saves considerable effort to spend a few moments with Google before trying to solve a problem for oneself. The author found that the properties of hub dynamos had already been investigated in great depth by others, such as at [1]. However, the Internet is not a complete substitute for a proper fault

diagnosis. **Figure 1** shows that on the author's lighting set a semiconductor device is wired across the bulb. The type P6KE7.5CA 'transient voltage suppressor' [2] is in effect two Zener diodes back-to-back, designed to clamp excess voltages. From the information in [1] it became clear what had happened. A hub dynamo, even at normal speeds, develops more than the specified 6 V. The suppressor

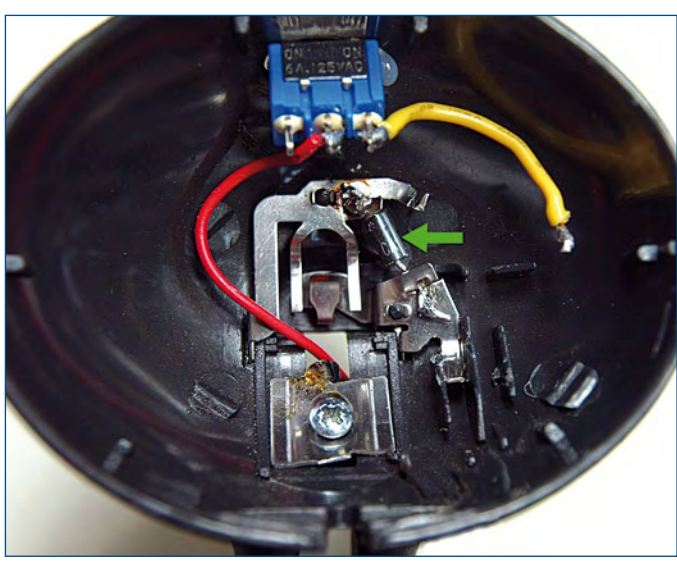


Figure 1. A suppression diode is wired in parallel with the filament lamp in the front bicycle light.

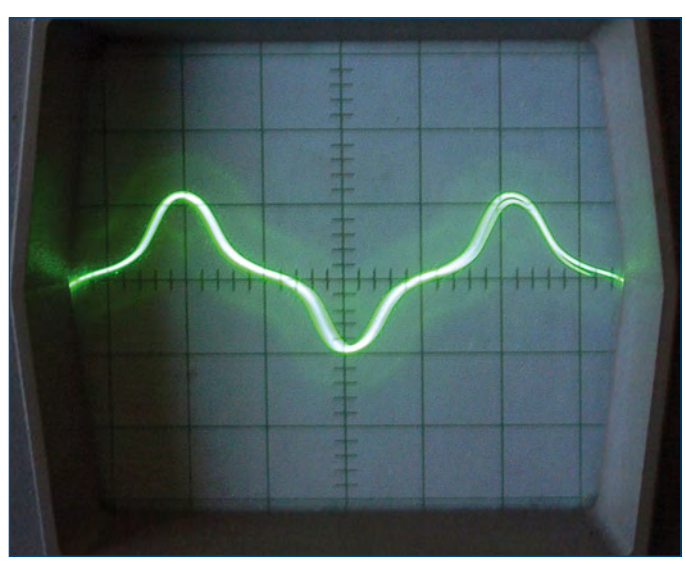


Figure 2. The voltage waveform from a hub dynamo is far from sinusoidal.

Light



increases linearly with applied voltage rather than exponentially, and so are more resilient to excessive voltages than bulbs.

Overture

The author had previously experimented with white power LEDs for bicycle lighting. At that time only 1 W devices were available, and, when used with a rim dynamo, the LED was not bright enough. Despite its higher efficiency the 1 W LED was not as bright as a 2.4 W filament bulb, although the whiter light was distinctly more noticeable and lifetime was of course better.

Act I: Power LED

Since then, 3 W LEDs have become available with efficiencies of over 110 lm/W, which is better than fluorescent lamps: a good start. A simple circuit using a 3 W LED is shown in **Figure 3**. The circuit achieves just slightly greater brightness than a halogen bulb. The current sourced by a hub dynamo is rarely much more than 0.5 A, and so a typical 3 W LED with a forward voltage of 3.3 V will be dissipating only around 1.6 W. However, the high efficiency of the device means that its light output is nevertheless greater than that of a 2.4 W halogen bulb.

Entr'acte

For maximum brightness the 6 V output of the dynamo needs to be converted down to 3.3 V to 3.8 V for the

sor, which is supposed to protect the bulb, is specified for a dissipation of 5 W, and begins to conduct at 6.5 V. At 0.5 A the voltage across the device will be about 7.5 V. (The dynamo can be thought of as a current source; without the suppressor a voltage of between 8 V and 10 V would appear across the bulb.) Even 7.5 V was, in the author's case, enough to destroy the bulb. Furthermore, the plot of

dynamo output voltage against time (see **Figure 2**) is far from sinusoidal. An enquiry at a nearby shop confirmed the author's hunch that he was not alone in his experience: 6 V bulbs were strong sellers.

It was interesting to note that the rear light, which used LEDs, had not failed. LEDs with a series current limit resistor dissipate a power that

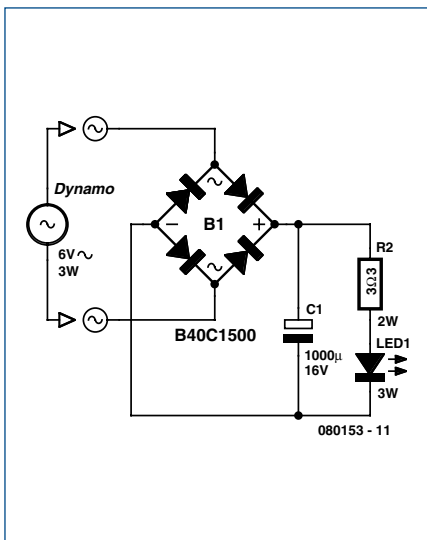


Figure 3. The first experimental circuit for using a 3 W LED in a bicycle light.

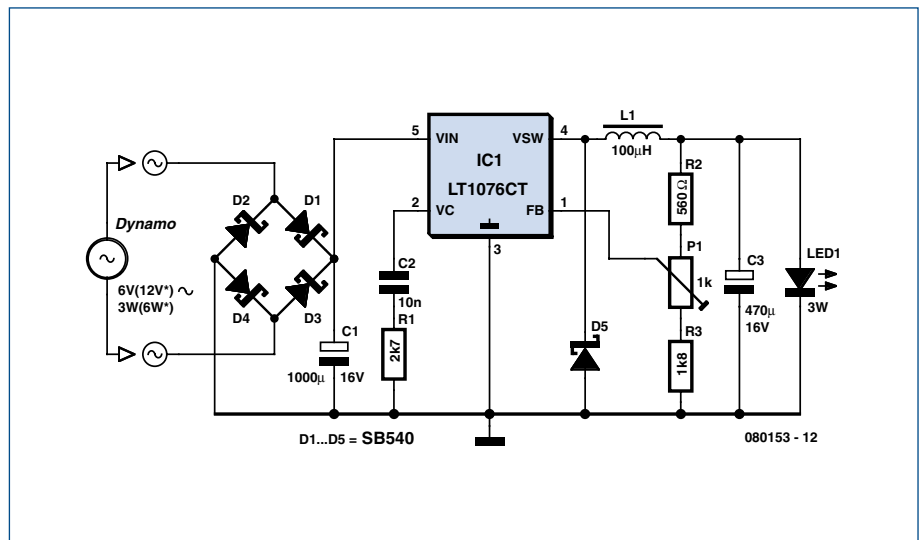


Figure 4. This final circuit for the bicycle light gets the maximum possible illumination from the 3 W LED.

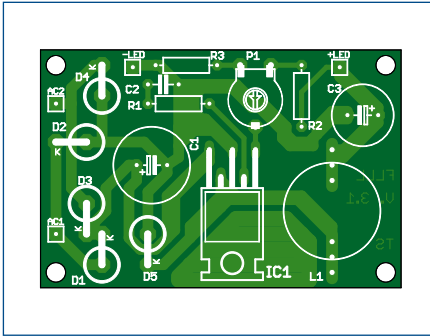


Figure 5. Eagle design files for the printed circuit board are available for download.

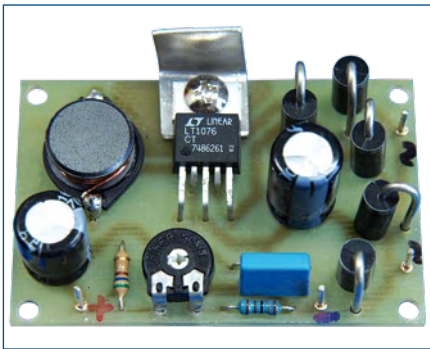


Figure 6. Very compact prototype of the switching regulator.

LED with as little power loss as possible, with a corresponding increase in current to 700 mA.

At such low voltages an ordinary step-down converter will operate at an efficiency of around 80 %. Rectifying the AC voltage from the dynamo using a bridge consisting of Schottky diodes will cost a voltage drop of twice 0.4 V, giving an additional power loss of 0.4 W at 0.5 A. Allowing 0.1 W for the rear LED light leaves us with just 2.5 W; 80 % of that is 2 W. Compared to



Figure 7. The LED (mounted on its carrier board) and lens are bolted to a piece of aluminium angle to make the lighting module.

COMPONENTS LIST

Resistors

- R1 = 2kΩ7
- R2 = 560Ω
- R3 = 1kΩ8
- P1 = 1kΩ preset, miniature, horizontal mounting

Capacitors

- C1 = 1000µF 35V, radial, lead pitch 5mm
- C2 = 10nF
- C3 = 470µF 16V, radial, lead pitch 5mm

Semiconductors

- D1-D5 = SB540 (Schottky)*
- LED1 = 3W power LED, white*

Miscellaneous

- L1 = 100µH 1A (e.g. Reichelt L-PISR 100µ)*
- Optics for power LED (20°-type)*
- PCB # 080153-1 (artwork download on www.elektor.com)

* see text

the circuit in **Figure 3** we have gained a meagre 0.4 W.

So, theoretically at least, things are not looking good. However, according to [1] hub dynamos can develop up to 12 V. At 0.5 A that corresponds to a power of 6 W.

This is more than enough: working backwards from the 3 W required for the LED, we divide by 80 % to obtain an input power to the switching regulator of 3.6 W. At 0.5 A this means a voltage of 7.2 V. Adding on the 0.8 V dropped by a Schottky rectifier bridge, and we need 8 V at the output of the dynamo, which is well within its capabilities.

The switching regulator gives us a further advantage: it protects the LED from excessive current and, above a certain dynamo speed, ensures that the light output provided is constant.

Act II: The circuit

Figure 4 shows a type LT1076 step-down converter [3]. The device requires a minimal number of external components and draws only 8.5 mA to power its internal circuitry. It operates at 100 kHz, can start up from an input voltage of 3.5 V and can deliver up to 2 A.

D1 to D4 form the bridge rectifier, and D5 is the flyback diode. At 5 A the SB540 is somewhat overspecified for this application; at 0.5 A the diode only drops 0.33 V. Good 1 A Schottky diodes such as the SB140 can be substituted for D1 to D5, with a resulting drop in overall efficiency of around 2 %.

The RC network comprising R1 and C2 connected to pin 2 of IC1 provides frequency compensation. The regulator compares the voltage on pin 1 with its internal reference (2.21 V), and so the adjustable voltage divider comprising R2, P1 and R3 allows the output voltage to be adjusted from 2.7 V to 4 V.

L1 is a fixed 100 µH inductor designed for operation at 100 kHz and 1 A. A low

ohmic resistance increases overall efficiency. However, the component is not particularly critical, and even a 100 µH toroidal suppression choke will give an efficiency of over 75 %.

Act III: Construction and test

The printed circuit board (**Figure 5**) makes construction straightforward. The layout design was done using Eagle, and the design files and a PDF of the layout are available for download from <http://www.elektor.com>. If IC1 is to be mounted flat against the board its pins must be bent accurately. A small heatsink made from a piece of aluminium angle (**Figure 6**) is adequate. IC1 dissipates a maximum of 0.5 W, so it is also possible to solder the M3 fixing nut to the copper pad on the reverse side of the board.

The coil suggested in the parts list is a low-cost SMD component to which two lengths of wire need to be carefully soldered. The printed circuit board also has pads for other package varieties. After populating the board and checking over the soldering, the circuit can

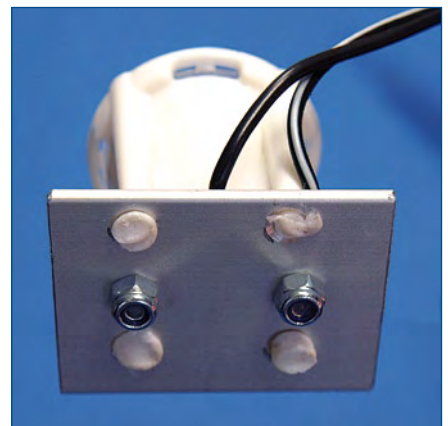


Figure 8. The module from behind: the four plastic lugs of the lens are melted slightly to secure them and the LED is isolated using plastic washers and fixed using M3 locknuts.

be connected to a bench supply or mains adaptor capable of delivering 9 V to 12 V at 0.5 A or more. The output is loaded using a 4 W 4.7 Ω resistor. It should be possible to adjust the output voltage over the range given above and IC1 should become gently warm to the touch. With 10 V at the input and 3.75 V across the 4.7 Ω resistor the overall efficiency of the circuit should be about 75 %: 4 W in and 3 W out.

Before turning the circuit off, adjust P1 to obtain the minimum output voltage so that when the LED is connected it is not immediately overloaded when the circuit is switched back on. Before wiring up the power LED it, and the printed circuit board on which it is mounted, should be bolted to a length of aluminium angle (not forgetting a dash of thermally conductive paste). It is best if the lens is also fixed to the aluminium angle. This makes a compact lamp module (see **Figure 7** and **Figure 8**) which has the advantage of not immediately damaging your retina

if you look directly into it. The module can be built into the old bicycle lamp enclosure with the filament bulb and suppressor removed. **Figure 9** shows the author's prototype where, with a judicious bit of filing, he managed to attach the module to the inside of the original lens in the lamp. The electronics can be mounted in a separate plastic enclosure.

by putting a meter in series with the LED the resistance of the meter will significantly affect accuracy, and so instead we connect the LED module directly to the output and measure the input current. Starting at the bottom of the adjustment range (P1 set to the far left position) we gradually adjust it until the input current is 0.4 A at 10 V, for a total input power of 4 W. Since the overall efficiency of the circuit is approximately 75 %, this means that the power delivered to the

Never look directly into a power LED when it is on!

Finale: Adjustment

As explained in the text box, the voltage across the power LED needs to be adjusted so that the correct current (approximately 0.7 A) flows through it. For maximum LED lifetime (over 20,000 hours) it is essential that this value is not exceeded. With adequate cooling, however, some devices can be run at up to 1 A. The adjustment is straightforward. If we try to measure the current directly

LED is approximately 3 watts. If a 12 V input, for example from a mains adaptor, is used the corresponding input current is 0.33 A. The forward voltage of the LED falls with increasing temperature, and so the current though it will rise. P1 will therefore need to be adjusted several times until, after perhaps five minutes, thermal equilibrium is reached. The adjustment is then complete. **Warning: never look directly into the LED.** The LED also gets hot!

Advertisement



Parallax

Helping bring your ideas to reality since 1987.

Microcontrollers and accessories for the engineer, hobbyist, and student.

PARALLAX
www.parallax.com

Milford Instruments
(+44) 1977 683665
<http://www.milinst.com>

Encore!

At low road speeds a hub dynamo delivers a low frequency AC voltage. At 5 km/h the LED blinks, becoming steady as the speed rises to 10 km/h. The circuit has not been tested with rim or other types of dynamo.

With a bit more pedalling effort (at speeds of over 30 km/h) the voltage from the dynamo, without suppressor diode, can reach 12 V. This will not cause any problems for the LED, which is protected by the circuit; however, if an ordinary 6 V 0.6 W filament bulb is used in the rear light it will soon be

destroyed. It is therefore recommended to use an off the shelf LED-based rear light as well.

The attitude of the governments of some European countries towards our efforts to equip our bicycles with bright and reliable lamps is hardly what one might call 'enlightened': in the author's home country the law specifies the use of filament bulbs in bicycle lights, notwithstanding the fact that a brightly-shining home-made light is a definite improvement on an off-the-shelf regulation-compliant light, and much bet-

ter again than an ordinary light with a blown filament!

(080153)

Links and References

- [1] **Hub dynamo laboratory test:**
www.vintagebicyclepress.com/VBQgenerator.pdf
- [2] **P6KE7.5CA data sheet:**
www.fairchildsemi.com/ds/P6%2FP6KE7V5CA.pdf
- [3] **LT1076 data sheet:**
www.linear.com/pc/downloadDocument.do?navId=H0,C1,C1003,C1042,C1033,P1007,D2659

Light show


The power LED is the most important component in this circuit. The photographs show sample devices from three manufacturers, all offering efficiencies of between 90 lm/W and 110 lm/W, around the same as a good fluorescent light. Cheaper, but decidedly inferior, 3 W LEDs are also available on the market, but purchasing these is a false economy. It is also best to avoid the 'warm white' variants, which have lower efficiency. The devices shown come mounted on a small printed circuit board which includes an aluminium slug that simplifies extracting heat. When run at 3 W some 2 W is dissipated as heat and a power LED not equipped with cooling will have rather a short life.

There are good reasons for operating LEDs at a constant current rather than at a constant voltage. A typical differential resistance for an LED of the kind used in this project might be as low as 0.2 Ω, which means that a voltage step of 20 mV gives rise to a current step of 0.1 A. Now, 20 mV is not a large quantity, and the sharp temperature dependence of the LED's forward voltage means that a temperature change of 10 °C could easily lead to a current change of more than 0.1 A.


Unfortunately most switching regulator ICs are designed for constant voltage rather than constant current operation. The internal reference voltage of the IC used here is 2.21 V, which is too large to allow the construction of a simple current feedback loop using a series sense resistor: at 0.75 A the power dissipated in the sense resistor would be in



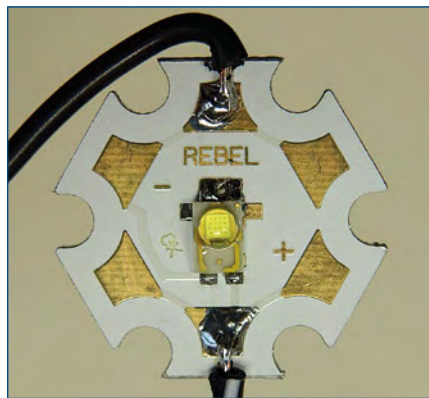This 3 W power LED from Cree is also an attractive piece of electronics in its own right.




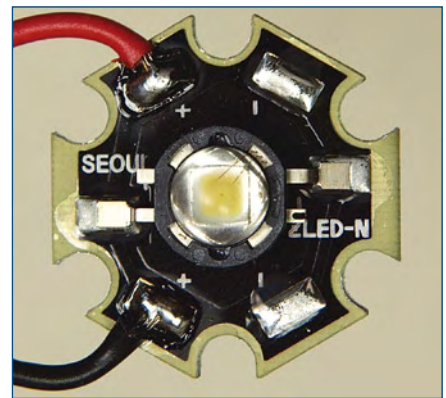The Luxeon Rebel is particularly small and is mounted on a ceramic substrate.



The Seoul Z-LED is encapsulated not in hard plastic but in a silicone resin which offers long-term resistance to dulling.

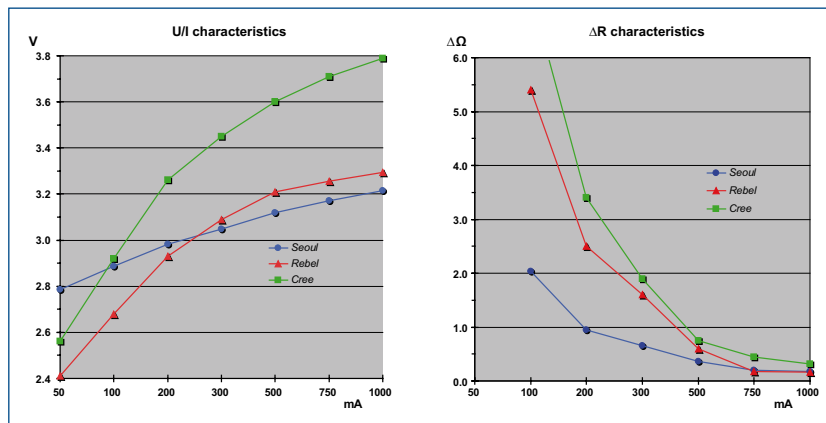In order to examine the differences between the various makes of LED, we made some measurements on a sample of each. The resulting characteristic curves are shown here. It is clear that the forward voltages are very different from one another and that the differential resistance of the LED is very low at currents of around 0.75 A. The consequences of this are as follows.



LED characteristic curves: voltage (left) and differential resistance (right) at various currents.

the region of 1.6 W. We therefore must resort to controlling the current via the output voltage of the regulator, adjusted via P1 to suit the particular LED used. This is sufficiently accurate if the differential resistance is around 0.2 Ω.

ANTEX

Antex offer a wide choice of input voltages and bit profiles for our soldering iron range

visit: www.antex.co.uk



60+ years of experience

www.antex.co.uk

FREE shipping on all orders

It may surprise you but buying an Antex soldering iron costs less than you think in the long run. British made to exacting standards, they last significantly longer than many imported brands. With a wide range of thermally balanced models, and temperature controlled irons too, you can always be sure to find an iron that meets your needs.

A large range of replacement tips are available for most irons, and technical help is on hand from our offices in Devon UK.

Buy Online

Our new website has all of our irons, and soldering spares and accessories available 24hrs a day. Most items are shipped next day, and we offer free carriage throughout Europe. Why not give antex.co.uk a try!

Antex Electronics Ltd
2 Westbridge Industrial Estate
Tavistock, Devon PL19 8DE, UK
Tel: +44(0)1822 613565
Fax: +44(0)1822 617598
Email: sales@antex.co.uk
Web: www.antex.co.uk

Electronics Engineers - Join A Winning Team! UK, Europe and Middle East

The Lektronix Group of Companies are the worlds leading provider of Industrial Automation repairs with an enviable reputation for the best in technical excellence and customer service.

Due to the huge demand for our services, and our future expansion plans, we need to employ additional engineers at all our workshops to keep pace with the additional work we are receiving.

We are looking for English speaking Electronic Repair Engineers, Electronic Repair Technicians and Electronic Component Level Repair Engineers in all the following locations:

- Walsall, UK
- Newry, Northern Ireland
- Brno, Czech Republic
- Bridgend, UK
- Katowice, Poland
- Dubai, UAE

Do you have an interest in electronics?
Have you any experience in the field of practical electronics?
Have you experience in Radio/Television/Home Electronics?
Does your hobby/interest include electronics?
Are you willing to learn new tricks – electronic engineering?
Do you want work in an exciting and challenging environment?
Do you have any experience with Machine Tool Systems - PLC's - Servo Drives - Servo Motors - Monitors-VDU's - AC Drives - DC Drives - Temperature Control - Digital Electronics – Analogue Electronics?

We offer a competitive salary and all the other benefits normal with a go ahead company.

Lektronix



Please Contact:
Mr Brian Stewart - Group Technical Director
Lektronix International Ltd, Unit C1, Lockside,
Anchor Brook Ind Park, Aldridge, West Midlands,
WS9 8EQ, United Kingdom.

For an application form please either:
Telephone +44 (0)1922 455555, or apply online
at www.lektronix.net/about/careers




Light as Air

Using the ATM18 to control a magnet levitation device

Udo Jürß and Wolfgang Rudolph

Overcoming gravity is an age-old dream, which we can't expect to see fulfilled anytime soon. However, we can come closer to making it reality on a small scale. Commercial levitation devices that cause a small piece of metal – often with some sort of covering – to hover in the air have been available for many years. A coil provides the lifting force, and a light barrier is used to regulate the levitation height. This causes the levitated metal object to maintain a defined distance from the core of the coil. Many of these devices are more expensive than need be. We also want to make something hover, but here we take a slightly different approach. Instead of a light barrier, we use a Hall sensor to detect the position of the levitated object.

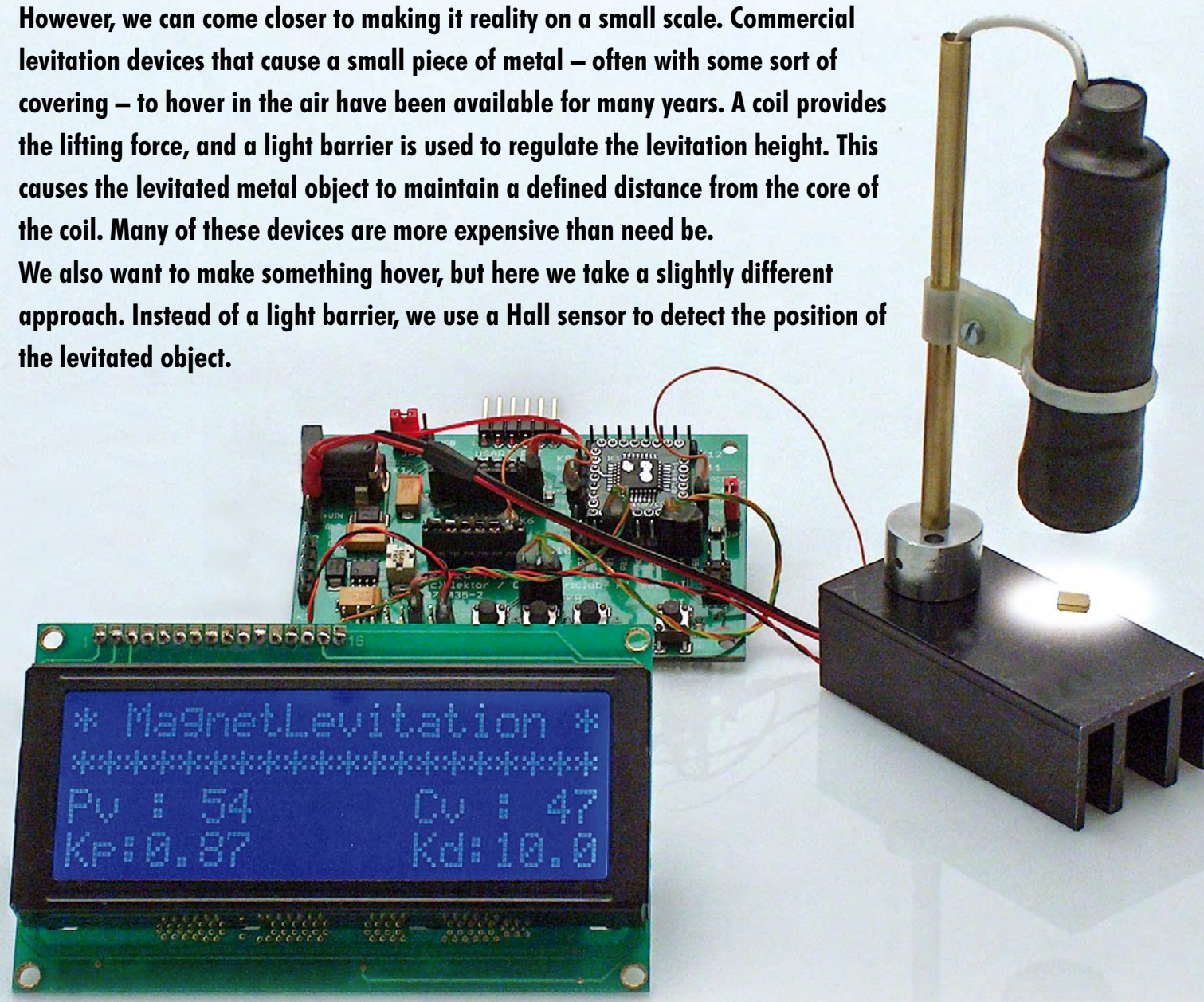

With the usual levitation devices, which have already been described in DIY articles in past issues of *Elektor*, the beam of a light barrier is more or less obstructed by the 'floating' object. The amount of light received by the sensor of the light barrier is used to control the amount of current flowing through the coil. The mechanical and electronic construction of the device is designed to maintain the levitated metal object in the prescribed position. Distance control using a Hall sensor is based on a completely different principle.

Magnetic field sensor

A Hall sensor is a semiconductor device that generates a voltage proportional to the strength of the surrounding magnetic field. The voltage produced by the actual sensor element is very small (in the millivolt region), so a sophisticated bridge amplifier is also necessary. We use a Micronas HAL815 integrated magnetic sensor housed in a low-profile TO-92UT package in our levitation controller, so this is already taken care of. The amplifier, temperature compensation and a filter are incorporated in the IC (**Figure 1**). All of the parameters can be programmed by superimposing digital signals on the supply voltage (with pulses that increase the voltage from 5 V to 8 V). For instance, the measuring range can be adjusted from ± 30 mT to ± 150 mT. Programming is not necessary in this case, because the device is factory-configured for the ± 30 mT range – which is exactly right for this application. With a supply voltage of 5 V, the output voltage is 2.5 V with no magnetic field present. The output voltage varies by plus or minus 2.5 V depending on the direction and strength of the magnetic field, for a total range of approximately 0 to 5 V. Only one direction is needed in this application, so only the range between 2.5 V and 5 V is used.

Controller

If we bring a magnet close to the Hall sensor with the magnetic field lines perpendicular to the surface of the sensor, the output voltage of the sensor varies in proportion to the magnetic field strength. This makes it possible to determine the distance between the sensor and a magnet with a known field strength. With this information, a controller can adjust the current in

The ATM18 project on Computer:club²

aTM18 was developed jointly by Elektor and Computer:club² (www.cczwei.de) with contributions from Udo Jürss, the main developer of www.microdrones.de.

Each month, the latest developments and applications of the ATM18 system are presented by Wolfgang Rudolph of CC²-TV in a TV broadcast on the German NRW-TV network. The levitation controller with the ATM18-AVR board described in this article can be seen in **instalment 12** of CC²-tv, initially broadcast on 26 June.

CC²-TV is also broadcast as a Livestream on the Internet at www.nrw.tv/home/cc2.

CC²-TV Podcasts are available from www.cczwei.de and – a few days later – from sevenload.de

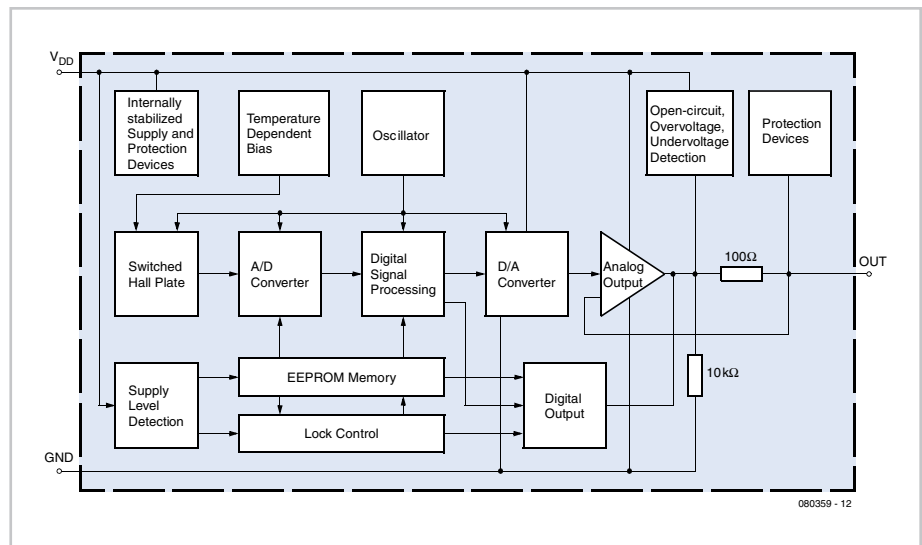


Figure 1. Block diagram of the sensor.

Hall effect

The American physicist Edwin Herbert Hall discovered this effect, which was later named after him, during his doctoral work in 1879. The Hall effect is based on the Lorenz force. Moving charges are deflected in a magnetic field, and this produces a potential difference perpendicular to the direction of current flow.

Hall sensors are made from small, thin sheets of semiconductor material with a low charge carrier density in order to achieve high electron velocity. This results in a relatively high output voltage. If a current flows through the sensor and it is placed in a magnetic field with the field lines perpendicular to the surface of the semiconductor, the sensor voltage changes. The output voltage of the sensor is proportional to the product of the current and the magnetic field strength. As the value of the current is known, the magnetic field strength can be determined from the measured voltage. These sensors are usually integrated in a package with a signal amplifier. The thermal sensitivity of the sensor is also compensated in such devices.

the coil to keep the magnet 'floating' in the air. The current is adjusted around 1000 times per second. This continual adjustment requires certain rules. PID controllers (proportional, integral and differential – see the inset) are used in electronic systems for this purpose. In our case the 'I' component is not necessary, so we can use a PD controller. However, it is not implemented as an analogue circuit with opamps

for this ATM18 project, but instead with software in the form of a controller program. Every minute departure of the levitated magnet from its intended position, every air movement, every change in temperature, every vibration, and many other things can directly affect the levitated behaviour. If the magnet moves a bit closer to the solenoid coil, the current in the coil must be reduced immediately. If the

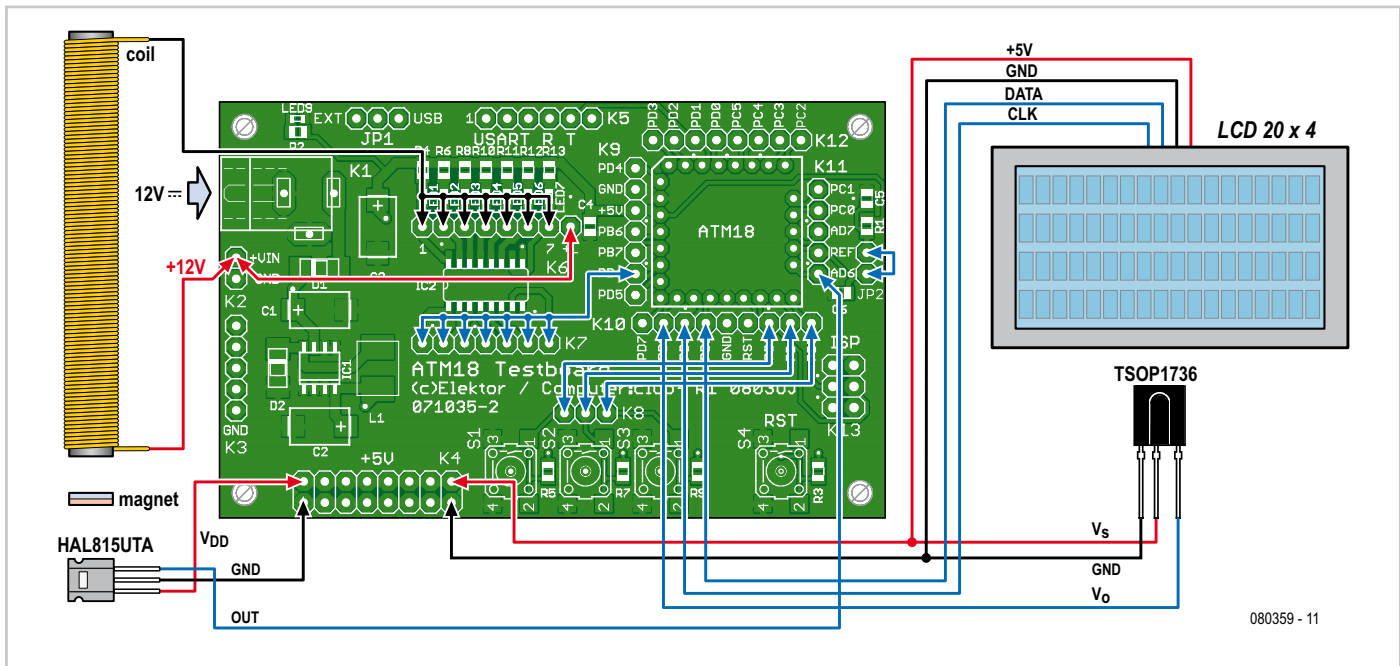


Figure 2. Schematic diagram of the experimental circuit

magnet moves even a small distance away from the coil, the current must be increased immediately. As the coil is connected to the PWM (pulse-width modulated) output of the microcontroller via a UL2003, this is done by changing the duty cycle. The pulses are integrated in the ferrite core and coil to yield an average current level.

Figure 2 shows the structure of our prototype. The Hall sensor is connected to ADC6. The PWM output on PD6 drives one or more inputs of the ULN2003 power stage. The coil is connected between the open-collector outputs and +12 V. It is important to connect pin 8 to K6 so the internal protection diodes in the ULN2003 can limit the inductive spikes from the coil. Pushbutton switches S1–S3 are used to configure the control parameters. This lets you raise or lower the levitation position of the magnet by up to 10 mm. Alternatively, you can use an RC5 infrared remote control unit to operate the device via an IR receiver connected to the circuit. The parameters are constantly shown on the LCD display.

General requirements

Making a magnet hover in the air is not a trivial task. If it comes too close to the coil, it will immediately be pulled all the way to the coil, and the controller can't do anything to stop it. This means that the coil must be mounted at a sufficient height. On the other

hand, the magnetic field of the fully energised coil must be strong enough to lift the magnet from its lowest position. This means that you have to wind the right coil on the right core and use a magnet that is as small and light as possible, but also strong. And you have to adjust the device for a suitable levitated distance.

Another difficulty is that the output voltage of the sensor is not proportional to the distance between the coil and the magnet. Nonlinear controlled systems can lead to stability problems. On top of this, the magnetic field of the lifting coil also affects the sensor. The severe requirements imposed by the controlled system make the job of the controller more difficult. Here a bit of help in the form of damping can't hurt. It arises in a rather unobvious manner due to the aluminium heat sink, under which the sensor is mounted. Every motion of the magnet creates an eddy current in the aluminium, and this produces an opposing magnetic field. In this way, magnet oscillations are damped by eddy-current losses.

Magnet and coil

The magnet must be very light and very strong. A neodymium magnet with a mass of less than 0.3 g is quite suitable. We used a type Q-CDM50-G from www.supermagnete.de (mass 0.23 g) in our various prototypes. Another potential source of small, strong

magnets is cannibalised CD drives. A preliminary test with the solenoid coil will tell you whether a particular magnet is suitable. With an applied voltage of 12 V, the coil should be able to lift the magnet from a height of at least 3 cm, but 4 cm or more is better.

A ferrite rod such as is commonly found in medium-wave radios is used for the coil. It should have a diameter of 10 mm and a length of 80 to 100 mm. Don't try to rush things when constructing the coil. As you can see from **Figure 3**, you start by sliding a length of heat-shrink tubing over the ferrite rod (a) and shrinking it in place (b). You can also use electrician's tape instead. After this, you can start winding the coil (c). It consists of four layers of 400 turns each, wound with 0.2-mm enamelled copper wire. You can wind the coil entirely by hand, or you can use an electric drill running at a very low speed (d). After you finish winding the coil, secure both ends with heat-shrink tubing (e), making sure to feed out the free ends for the leads (f). Finally, you can fit another length of heat-shrink tubing over the entire coil to protect it (g).

If you want to avoid counting turns and would rather wind the coil 'helter-skelter', you can wind the ferrite rod over a length of 50 mm with 0.2-mm copper wire until the winding reaches a diameter of 18 mm. The coil will then have a resistance of 40 to 50 Ω, so the

current will not exceed 300 mA with a 12-V supply voltage (this only holds true for DC current). When the coil is driven by the PWM output of the processor, amplified by the ULN2003, the current is pulsating DC instead of pure DC. The average value of the current is thus less, and the coil characteristic is similar to that with AC operation, with the result that a distinctly lower current flows through the coil. This completes the coil. After you have carefully protected the leads and the ends of the coil with electrician's tape, you can simply use the alligator clips

of a 'third hand' (soldering aid) to hold the coil for initial testing. This makes it easy to adjust the height to the proper value (Figure 4).

Practical aspects

Our prototype (see the photo at the head of the article) was built around an aluminium heat sink with the sensor mounted underneath. A brass rod was fitted to the heat sink, and the wiring that conducts the current to the coil was routed along this rod in a suitable manner. A plastic bracket

was fitted to the rod, and the coil was clamped to the bracket. The details are shown in Figures 5a–d.

After the coil has been secured, you can connect everything to the prototyping board and start your levitation tests. Two ready-made sample programs are available on the Elektor website for downloading. One of them was written in Code Vision, and the other in BASCOM.

The best approach is to start with the C program, since it shows all the par-

PID controllers

Our objective here is to use an electromagnet to attract a permanent magnet exactly enough to levitate it at a particular height. As the magnet levitation system is an unstable, nonlinear controlled system, it must be stabilised as well as regulated. We use a PD controller for this purpose. The task of a closed-loop controller is to continually and independently control a physical quantity in order to maintain a specified setpoint value – in our case the magnet position – and eliminate the effects of disturbances. For this purpose, the controller constantly compares the actual value (the position of the magnet) with the setpoint value (the desired position of the magnet). The control error determined in this manner is used to generate the control output, which acts to minimise the control error when the control loop is in balance. However, it takes a certain amount of time for a system of this sort to respond and for the control output to take effect, and for this reason it must overreact at first and then underreact immediately afterward in order to avoid overcompensation that would cause control failure. This requires the control output to have a damping effect, depending on the system characteristics. The behaviour of the controller is described by differential equations.

The magnitude of the P component varies in proportion to the control error (difference between the actual value and the setpoint value). This only affects the proportional gain factor.

The D branch of a controller is a differentiator that must always act together with the P component (or the I component). The D component arises from variations in the control error over time and is multiplied by the integral action time. It does not depend on the control error, but instead on the rate of change. A large integral action time cause a large change in the control output and often causes instability in the control loop.

An integral component is used when the control error must reduced to zero (or as close to zero as possible). It is not used here because the levitation device always works with a control error and only the control gain is adjusted. The slope of the control curve decreases as the distance from the sensor increases, which is offset by increased gain. This compensates for the nonlinear characteristic of the controlled system.

Listing

Example BASCOM PD controller

```
, Atm18 PD regulator
, S1 At Pb3 = Up
, S2 At Pb4 = Down

$regfile = „m88def.dat“
$crystal = 16000000

Dim N As Byte
Dim X As Integer
Dim Y As Single
Dim Z As Single
Dim Xold As Single
Dim Xp As Single
Dim Xi As Single
Dim Xd As Single
Dim P As Single
Dim I As Single
Dim D As Single

Config Adc = Single , Prescaler = 32 , Reference = Off
` AD-Wandler starten
Start Adc
Config Timer0 = Pwm , Prescaler = 1 , Compare A Pwm =
```

```
Clear Down , Compare B Pwm = Clear Down

P = 0.1
D = 60


Do
  If Pinb.3 = 0 Then P = P + 0.0002
  If Pinb.4 = 0 Then P = P - 0.0002
  X = 0
  For N = 1 To 8
    X = X + Getadc(6)
  Next X
  X = X / 8

  If X < 512 Then X = 512
  Xp = X - 512
  Xp = Xp * P

  Xd = X - Xold
  Xold = X
  Xd = Xd * D

  Y = Xp + Xd
  Y = Y / 2
  If Y > 255 Then Y = 255
  If Y < 0 Then Y = 0

  Pwm0a = Int(y)
Loop
```

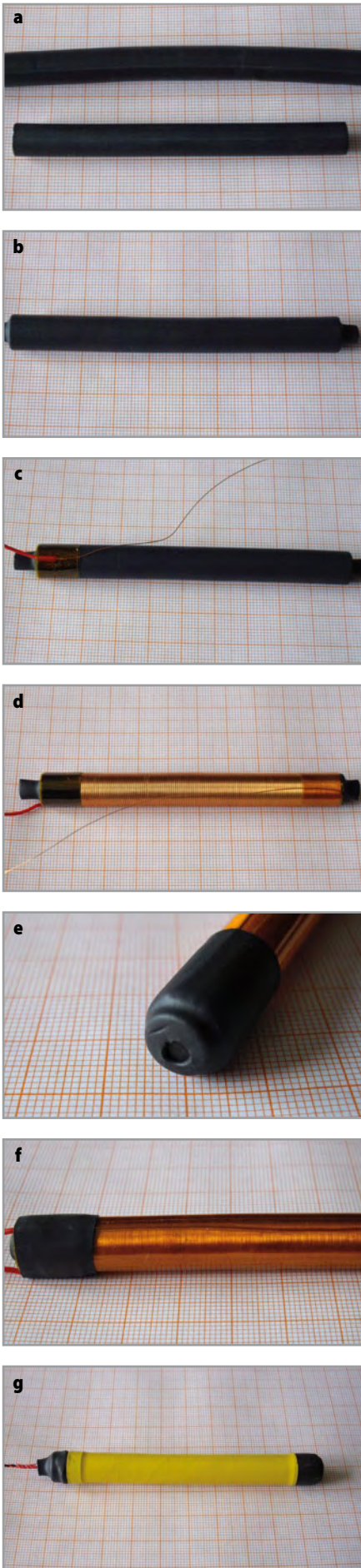

ameters on the display. Right after you switch on the supply voltage or reset the circuit, no current flows through the coil because the proportional factor of the controller is zero. Place the magnet above the sensor, orient it to obtain a maximum reading for the displayed Pv value, and press button S1. This should cause the current to increase. You can also see this from the increasing brightness of the LEDs on the outputs. If nothing happens, the magnet is probably the wrong way round. Turn it over and repeat the experiment.

The longer you press S1, the more the coil current will increase. Suddenly the magnet will start to rise and then remain suspended in a stable position. You can press S1 to make it rise even higher. If you press S1 and S2 at the same time, it will drop gradually. At some point, you will doubtless overdo the levitation height and the magnet will fly up to the ferrite rod with a bang. Now you know the maximum levitation height. You can probably increase the levitation height slightly by carefully adjusting the position of the solenoid coil. The coil should be just high enough that it can still lift the magnet from the surface of the heat sink. S1 adjusts the proportional factor of the controller, which effectively means the control gain. You can also use S3 to alter the proportion of the differential component, which is important for stability. However, in most cases the default value is suitable.

If the magnet refuses to lift, the direction of the magnetic fields may be to blame. Try reversing the polarity of the coil. You can also use a voltmeter to check the output voltage of the sensor. It should be close to 2.5 V with no magnet present, and the value with the magnet lying above the sensor should be more than 4 V. Some other possibilities are that the magnet is too weak or too heavy. However, this should have already been sorted out by the initial test without the controller.

MLC in C

The C program for the magnet levitation controller (MLC) is very large and can only be described here in general terms.

Figure 3. Coil construction stages: ferrite rod with heat-shrink tubing (a) shrunk onto the ferrite rod (b); start of coil winding (c); fully wound coil (d); coil ends covered with heat-shrink tubing (e) and with the leads fed out (f); finished coil covered with heat-shrink tubing (g).

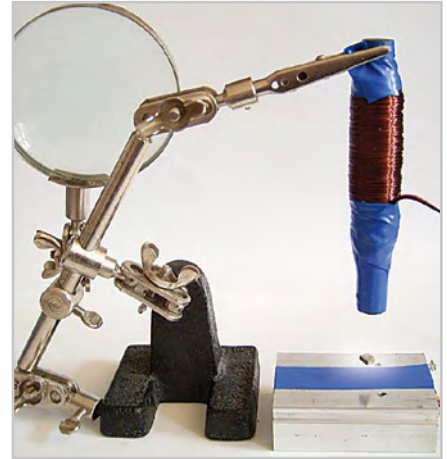


Figure 4. A simple experimental setup.

Hall sensor data acquisition and timing generator

The A/D converter is used to acquire the Hall sensor data and as a timing generator. Eight sensor readings are acquired in an interrupt routine within 1 millisecond. After this the 'adc_ready' flag is set. The main program loop uses this flag for synchronisation. The function 'adc_get_average()' calculates the average of the eight sensor readings, which forms the current actual value for the PD controller. This averaging suppresses noise on the measured signal.

Controller

The PD controller is recalculated 1000 times each second. Due to this constant time interval, the control algorithm does not have to calculate the time, which saves processing time. The average sensor value is first calculated in the function 'mlc_update'. The P component is calculated from this actual value. The D component is calculated as the difference between the previous and current actual values. The control output (the pulse width of the PWM signal) is formed by adding the two components.

Actuator

Here the actuator for the controlled system is the electromagnet in the form of a ferrite-core coil. A PWM signal with a pulse rate of 32 kHz drives the power stage (ULN2003). The coil is switched to ground. Thanks to the high PWM frequency and the large inductance of the coil, the coil current is strongly filtered (integrated). This yields a constant magnetic field with a low ripple component.


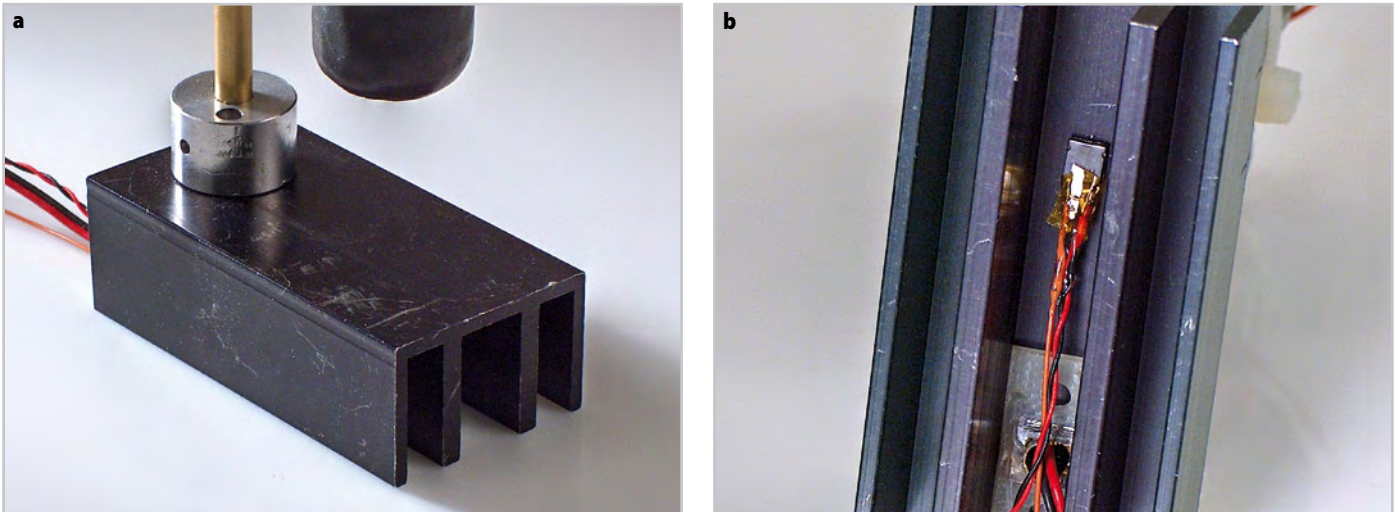


Figure 5. Details of the prototype assembly: (a) base plate (aluminium heat sink), (b) Hall sensor, (c) brass rod with coil leads, (d) coil bracket with cable ties.

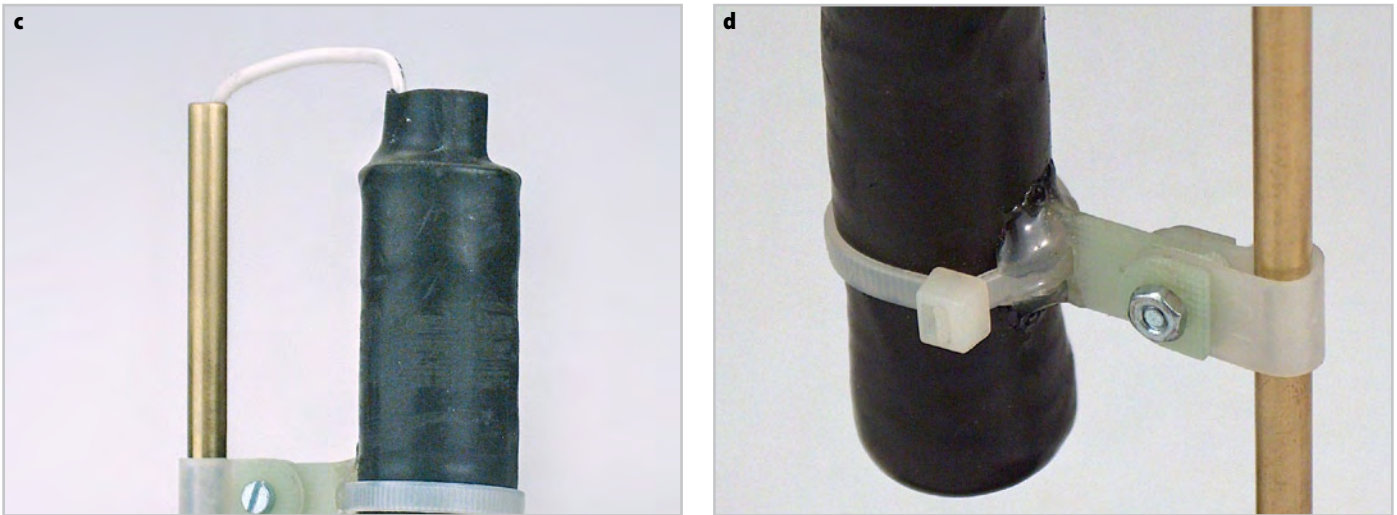

Display output

To avoid reducing the control frequency as a result of time-consuming display outputs, the outputs are divided into many individual jobs. The function 'mlc_write_lcd()' uses a state machine to perform a single display output in each control cycle.

Control process

After the individual modules have been initialised, the same process is executed repeatedly in an endless loop:

1. Update the control loop:
mlc_update(); // Update magnet levitation control
2. LC display output:
mlc_write_lcd(); // Do a single LCD operation
3. Scan control parameter buttons:
mlc_scan_buttons(); // Check the Kp and Kd pushbuttons
4. Synchronise with A/D converter:
while (!adc_ready) // Synchronise

the control loop

5. Start the next control cycle at step 1

RC5 control

With an IR receiver connected, you can use an RC5 infrared remote control unit to operate the device remotely. Button 1 increases the P value, while button 4 decreases it. Button 3 increases the D value, while button 6 decreases it. In addition, button 0 acts as an emergency stop and causes the P value to be set to 0.

BASCOM example

The Basic program (see listing) has intentionally been kept simple, so it does not include the LCD and remote control functions. Only the P factor (and thus the effective levitation height) can be adjusted using the S1 and S2 buttons. When the program is started, P is assigned the value 0.1 to provide a certain amount of gain so you can place

the magnet exactly above the sensor by positioning it to obtain maximum coil current.

The controller performs its calculations with real numbers (single precision). Here again the actual value is obtained by averaging eight individual readings. The controller can only use the range between 512 and 1023. The lower the magnet position, the higher the measured value. The measured value is multiplied by the P factor to yield the setting for the PWM value. The system would also work without a D component, but the motion is damped if this component is added. If the magnet rises quickly, the controller anticipates an imminent overshoot and reduces the current accordingly.



(080359-1)

Assembly note

A parts kit with a ferrite rod, HAL815 and magnet is available from www.elektor.com.

BASCOM AVR Course

Programming the ATmega controller

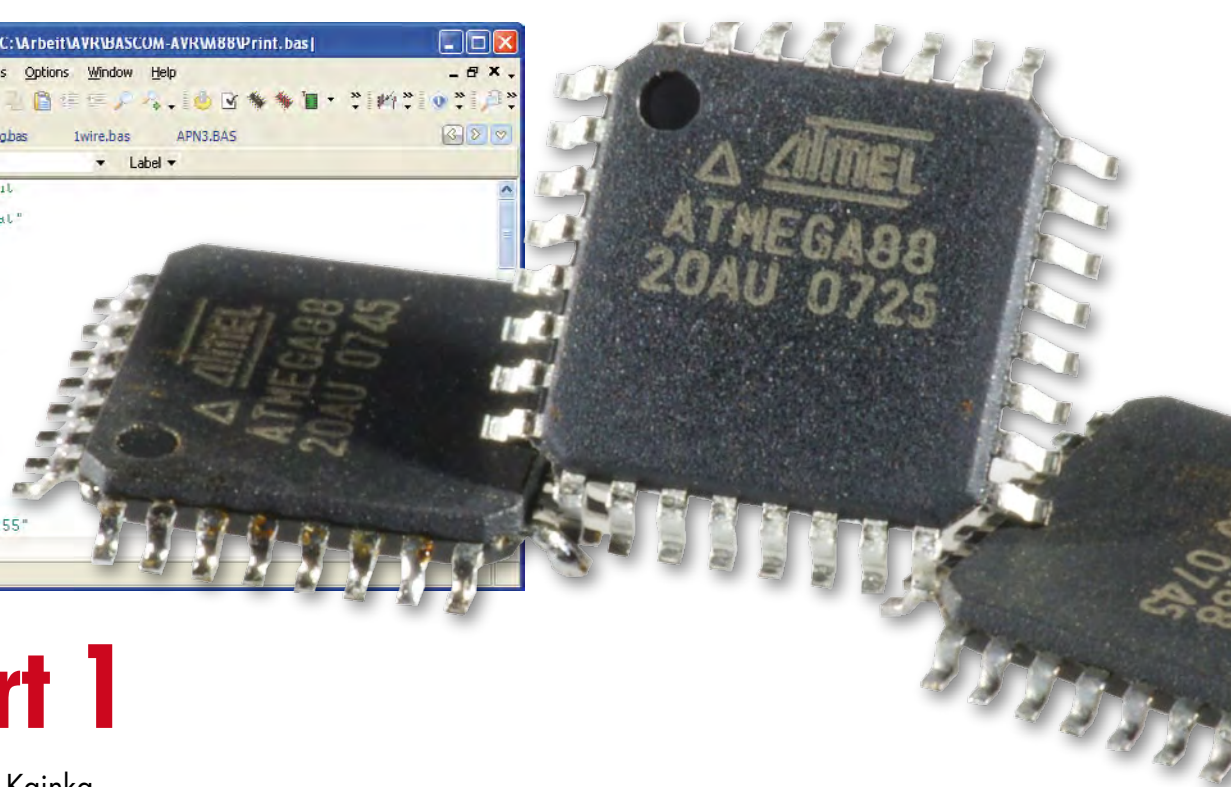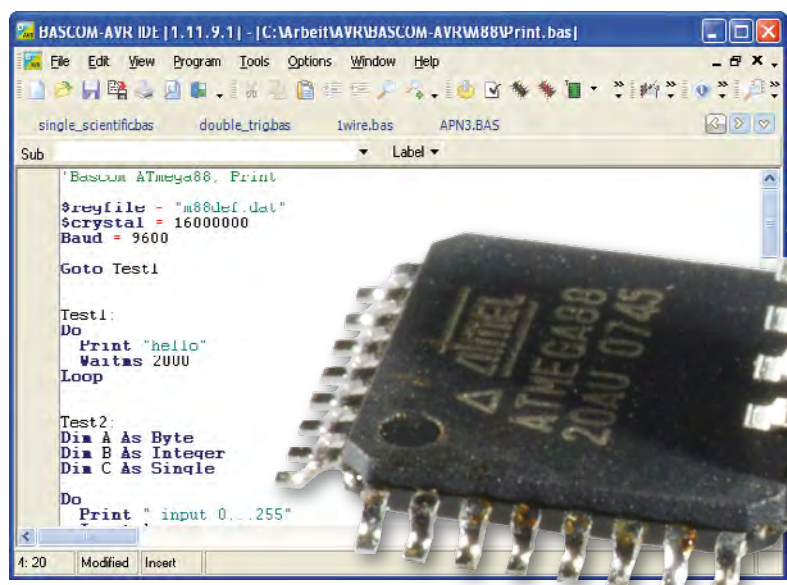

Part 1

Burkhard Kainka

The AVR series of microcontrollers from Atmel are very popular. Many projects already featured in Elektor have an ATmega beating away at their heart. In this mini course we turn the spotlight onto software development for these controllers. BASCOM is an ideal programming language for the newcomer; it has a steep learning curve ensuring that your path to success (and a working prototype) is reassuringly short.

The ATmega controller and BASCOM together make a strong team! Whatever application you have in mind, controllers from the ATmega range are sure to have the majority of the necessary peripheral hardware already integrated on-board: ports, timer, A/D converter, PWM output, and UART are all standard together with a choice of RAM, ROM and EEPROM size. BASCOM is one of the easier languages to use and makes interfacing to peripherals using LCDs, RC5 and I²C a simple task requiring very few instructions. There is a good range of development hardware for this microcontroller family. The STK500 from Atmel or the Elektor CC² ATM18 AVR board [1] are both suitable platforms for this course. Alternatively there is no reason why you should not experiment with your own homebrew design built on a

piece of perfboard. It also makes little difference whether you choose a Mega8, Mega88 or even the larger Mega16 or Mega32. They all basically have the same core; the main differences are in the number of port pins and the amount of internal memory space. In this first instalment of the course we look at the controller's UART and A/D converter.

The serial interface

All of the ATmega series have a built-in serial interface (UART) using pins RXD (PD0) and TXD (PD1). The signals are TTL compatible so it is necessary to add an RS232 interface buffer such as the MAX232 to implement a true

RS232 interface. These buffers are already implemented on the Atmel STK500 development system. A suitable serial to USB Adapter can be connected directly to the Elektor ATM18 AVR board for serial communication [2]. The PC will need to be running a terminal emulator program before serial communication from the ATmega can be viewed on the screen. The serial interface is covered here first because the software routine is very simple and can be easily modified if required.

Listing 1 shows all the elements necessary for all of the BASCOM programs. The first line \$regfile = "m88def.dat" indicates which controller the code will be running on; in this case it is the ATmega88. The line can be omitted and the controller type specified using the Options/Compiler/Chip menu but this method will generate an error if a different AVR system is used. It is far better to declare the controller type clearly in the program header with any program that you write. It also has priority and overwrites any setting defined in the Options menu.

It is also important to specify the crystal frequency (\$crystal = 16000000 for 16 MHz). It influences both the division ratio necessary to provide the requested communications baud rate clock (Baud = 9600) and also the timebase used to count milliseconds in the 'wait' statements (Waitms 2000 for 2 s).

One feature of the test program given here is the use of the unconditional jump instruction Goto Test1. It is normally good programming practice to avoid using Goto statements because they interrupt the program structure. In this instance we have included several programming examples in the same source code so it is only necessary to alter the first Goto Test1 to Goto Test2 or 3, etc. (depending on which example you want to run) and then recompile. This avoids the need to compile individual source files for each example and reduces the number of files generated in the compilation process. Additional test programs can simply be added to the code and run using an appropriate Goto statement.

The small program example used for Test1 forms an endless loop between the Do and Loop statements. The program outputs a 'hello' message every two seconds. A terminal emulator program like HyperTerminal is needed to receive the message.

Calculating

The program in **Listing 2** is used to calculate the area (C) of a circle where 'A' is the given radius:

$$C = A^2 * 3.1415$$

'A' must be an integer variable, which is dimensioned as a byte and input via the serial interface. The value of 'A' (in the range 0 to 255) is first multiplied by itself. The resultant intermediate value 'B' can be up to a word long (0 to 65535). The result 'C' is a real value and is dimensioned as single which requires four bytes to store its value.

Anyone familiar with other dialects of BASIC may be wondering why the calculation has not been written as C = 3.1415 * A * A or Print 3.1415 * A * A.

The reason is that BASCOM only allows one calculation per expression so it is necessary to break down complex

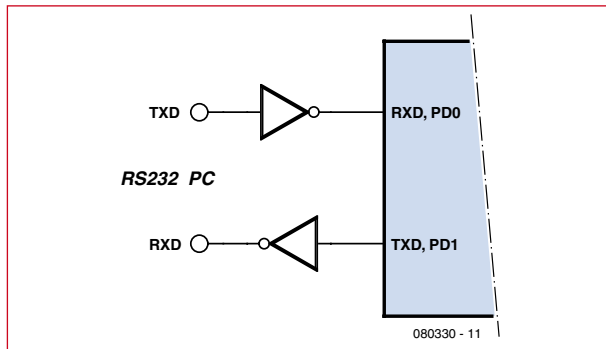


Figure 1. The serial interface.

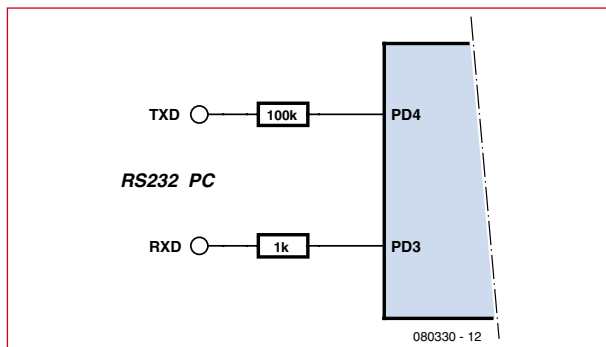


Figure 2. The simplest serial interface without an inverter.

calculations into series of single steps to avoid violating this rule.

Procedures

The A/D converter in the ATmega has a 10-bit resolution. **Listing 3** shows an example of how the converter is initialised:

Config Adc = Single , Prescaler = 64 , Reference = Off.

The converter clock frequency is defined here as 1/64 of the processor clock, i.e. 250 kHz with a processor clock of

Listing 1

Print 'hello'

```
,Bascom ATmega88, Print
$regfile = „m88def.dat“
$crystal = 16000000
Baud = 9600
```

```
Goto Test1
```

```
Test1:
Do
  Print „hello“
  Waitms 2000
Loop
```

```
Test2:
...
Test3:
...
End
```

Listing 2

Calculating in BASCOM

```
Dim A As Byte
Dim B As Word
Dim C As Single

Do
  Print " input 0...255"
  Input A
  B = A * A
  C = B * 3.1415
  'not allowed: C = 3.1415 * A * A
  Print C
Loop
```

Listing 3

Using a procedure

```
Declare Sub Voltage
Dim N As Byte
Config Adc = Single , Prescaler = 64 , Reference = Off
Start Adc

Do
  N = 0 : Voltage
  Print "ADC(0) = " ; U ; " V"
  N = 1 : Voltage
  Print "ADC(1) = " ; U ; " V"
  Print
  Waitms 500
Loop

Sub Voltage
  D = Getadc(n)
  D = D * 5
  U = D / 1023
End Sub
```

Listing 4

Using the Software UART

```
Baud = 9600
,Open "comd.3:9600,8,n,1" For Output As #2
Open "comd.3:9600,8,n,1,INVERTED" For Output As #2
Config Adc = Single , Prescaler = 64 , Reference = Off

Do
  N = 0 : Voltage
  Print #2 , "ADC(0) = " ; U ; " V"
  N = 1 : Voltage
  Print #2 , "ADC(1) = " ; U ; " V"
  Print #2 ,
  Waitms 500
Loop
```

16 MHz. The internal reference voltage is not used but is derived externally and applied to pin AREF. In most cases the 5 V stabilised supply voltage can be used.

A procedure is used to input the ADC measurement and convert it to a voltage reading. It is only worthwhile using a procedure if it can be reused by different parts of the main program body. In this example two voltage measurements are displayed. The new procedure is called Sub Voltage. Before the procedure can be called it must first be declared: Declare Sub Voltage.

The program fragment shown here does not conform to good software writing practice. In Visual Basic it is usual to pass the channel parameter 'N' when the procedure is called: Voltage(N). Alternatively a function could be written and then called using: U = Voltage(N). In the example here we are using only global variables so that D, N and U are accessible from all parts of the program including other procedures. All of the accepted software guidelines indicate that this is not good programming practice but in this instance it simplifies the job for the compiler and controller. Experience has shown that even large programs occupying 100% of the flash memory of a Mega32 and using a large number of global variables are completely stable in operation and run without problem. Passing variables to procedures can sometimes generate errors which are quite difficult to trace.

The software serial interface

One of the many highlights of the BASCOM compiler is its software serial interface. Say you are already using the hardware serial interface with the RXD and TXD pins and you require another COM interface? Alternatively it could be that you do not have any RS232 interface inverter chip (e.g. a MAX232) on your board but still need to provide a connection for an RS232 cable. In both cases BASCOM has a solution to the problem. Any available port pins can be defined in software as serial interface pins for the software serial interface.

The example **Listing 4** uses PD3 as a serial output. Communication speed is set to 9600 Baud and the interface number 2. To output a simple message you can use Print #2, 'hello' for example.

Using the INVERTED parameter allows the interface to be built without the need for a MAX232 interface inverter. BASCOM inverts the signal so that inactive level is a logic Low. The PC interface RXD signal can then be connected directly. The signal levels are not truly RS232 but it provides a useable interface solution and can, for example, be used to interface a USB to serial adapter to the Elektor ATM18 AVR board without the need for a MAX232.

(080330-1)

References

- [1] ATM18 AVR Board, *Elektor* April 2008.
- [2] USB <-> RS-232 Cable, *Elektor* July/August 2008.

Downloads and further information

The programming examples and more information for this course can be downloaded from the project page at www.elektor.com. We also welcome your feedback in the Elektor Forum.

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full range and Pdetails.

Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£12.95**
Assembled Order Code: AS3179 - **£19.95**



Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£17.95**
Assembled Order Code: AS3158 - **£27.95**



Bi-Directional DC Motor Controller (v2)

Controls the speed of most common DC motors (rated up to 32Vdc, 10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£17.95**
Assembled Order Code: AS3166v2 - **£27.95**



DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£13.95**
Assembled Order Code: AS3067 - **£21.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 £8.95

8-Ch Serial Isolated I/O Relay Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs. 4 isolated digital inputs. Useful in a variety of control and sensing applications. Controlled via serial port for programming (using our new Windows interface, terminal emulator or batch files). Includes plastic case 130x100x30mm. Power Supply: 12Vdc/500mA. Kit Order Code: 3108KT - **£54.95**
Assembled Order Code: AS3108 - **£64.95**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - **£17.95**
Assembled Order Code: AS3145 - **£24.95**
Additional DS1820 Sensors - **£3.95 each**



Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - **£44.95**
Assembled Order Code: AS3180 - **£54.95**



DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. Not BT approved. 130x110x30mm. Power: 12Vdc. Kit Order Code: 3140KT - **£54.95**
Assembled Order Code: AS3140 - **£69.95**



Infrared RC Relay Board

Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12Vdc/0.5A
Kit Order Code: 3142KT - **£47.95**
Assembled Order Code: AS3142 - **£59.95**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) **£14.95**
18Vdc Power supply (PSU010) **£18.95**
Leads: Parallel (LDC136) **£3.95** / Serial (LDC441) **£3.95** / USB (LDC644) **£2.95**

NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. Wide range of supported PICs - see website for complete listing. ZIF Socket/USB lead not included. Supply: 16-18Vdc. Kit Order Code: 3149EKT - **£39.95**
Assembled Order Code: AS3149E - **£49.95**



NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB lead not included. Assembled Order Code: AS3128 - **£44.95**



"PICALL" PIC Programmer

"PICALL" will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC16C5x family) programmed PIC micro controllers. Free fully functional software. Blank chip auto detect for super fast bulk programming. Parallel port connection. Supply: 16-18Vdc. Assembled Order Code: AS3117 - **£24.95**



ATMEL 89xxxx Programmer

Uses serial port and any standard terminal comms program. Program/ Read/ Verify Code Data, Write Fuse/Lock Bits, Erase and Blank Check. 4 LED's display the status. ZIF sockets not included. Supply: 16-18Vdc. Kit Order Code: 3123KT - **£24.95**
Assembled Order Code: AS3123 - **£34.95**



Projection over Hundre

Laser projector with servos



Gert Baars

We've already covered a laser projector in an earlier instalment of this series. This time however, we use a different projection mechanism. With a few servos, a laser module from eBay, a microcontroller and a little dexterity we can make a laser projector which, depending on the laser, can be seen from several hundreds of metres.

Laser projectors are often used for light effects at, for example, places of entertainment. These generally use powerful laser beams which generate striking light patterns. These types of laser projectors are not cheap however and even the individual parts such as laser modules and fast servos are not really that attractive either, considering their price. The alternative then, naturally, is to make your own.

Laser diodes and modules

Through eBay and the like, laser pointers and modules are frequently on offer for less than 10 pounds. These are typically red lasers with a power of less than 5 mW. This is more than enough to project something indoors during the day and outdoors at night up to a distance of about 100 metres. More powerful lasers, such as green lasers rated at 30 mW, can be used outdoors during the day over hundreds of meters and at night over several kilometres. Using this type of laser is not recom-

mended, in principle, because of safety considerations.

You can also use a single laser diode. But you will need a so-called collimator to obtain a parallel light beam.

Controller

The heart of the control system (see **Figure 1**) is an ATmega88 controller. Although it would be possible to drive the servos with a purely analogue system, from a music source for example, using a microcontroller offers additional possibilities such as the projection of text.

Analogue signals are required to drive the servos. We generate these with two PWM DACs (X-Servo and Y-Servo). The 78 kHz PWM frequency is strongly suppressed with a four-stage RC-filter. The two ADC inputs (X-in and Y-in) allow for analogue control, for use as a XYZ-plotter and an X-T oscilloscope. The Z-input (with internal pull-up) is

used to turn the laser on and off. An RS232 interface is added so that an LCD and keyboard interface are not required.

The HyperTerminal program that is part of any standard Windows installation can be used to communicate with the projector. The correct port settings are 9600 baud, 8 bits, 1 stop bit, no parity and no flow control.

The schematic for the laser controller shows that the laser is driven with a constant current. R_1 defines the laser current and the quiescent current can be set with P1. This is sometimes better because laser diodes start to work at a certain threshold current but only produce optimal light when operating at a certain temperature. By setting the idle current just under the threshold current the light output is increased when used as a projector.

On pin 6 of the controller there is also an output called 'TTL optional'. This is because some laser modules are supplied with a control PCB which has a

ds of Metres

ALWAYS BE VERY CAREFUL WHEN WORKING WITH LASER TYPES III-A AND III-B AND GREEN DPSS LASERS. LOOKING INTO THE BEAM CAN PERMANENTLY DAMAGE YOUR RETINA!

separate modulation input that can be driven directly.

Laser modules, such as the ones used in laser pointers, often have a photo diode which is used to control the laser current. These common modules are usually intended for 3 V battery operation. If you measure the current of the module at 3 V you can use this to determine what the value for R_i should be. In this case it is better if R_i is selected to be slightly smaller.

The servos

Making your own servos that are reasonably fast is not all that difficult. Servos targeted for the model-building world are not an option because they are too slow and inaccurate for this application. The servos for the laser projector can easily be made from a small DC motor that is often found in older CD/DVD drives. We refer here to the motor that opens and closes the tray, but sometimes a CD/DVD drive contains multiple motors of the same type.

To turn the DC motor into a servo an angle sensor is required. This angle sensor measures the rotation of the motor shaft. The result of this measurement is used to correct the position of the motor shaft. In a standard servo the angle sensor is generally a potentiometer which is connected to the motor shaft. This, however, creates a lot of friction and is not very accurate. The servos for the laser projector use a combination of a magnet and a Hall-effect sensor as the angle sensor. The magnet is an especially powerful Neodymium miniature magnet which measures only $2 \times 2 \times 2$ mm.

There are several possibilities for attaching the little magnet to the spindle. Here we used the clamp from a plastic terminal strip as the coupling (see Figure 2). These have an internal diameter of 2.2 mm while the motor shaft has a diameter of 2 mm. Not really ideal, but the clamp can be fixed in place with the screw and the little magnet is easily glued to it. When gluing the magnet you need to make sure that the north- or south-pole

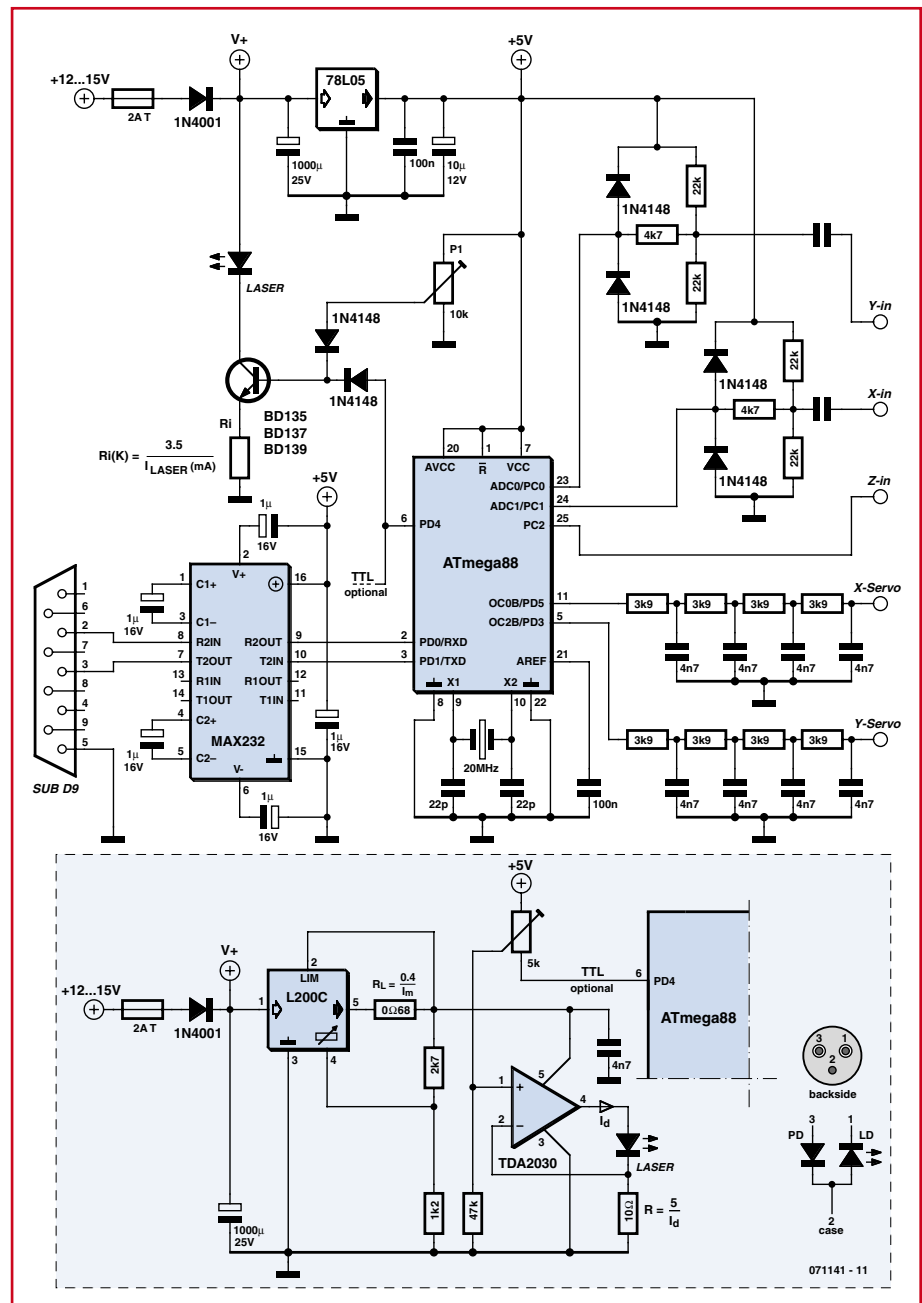


Figure 1. The schematic for the laser controller. The optional driver circuit can be used for larger lasers.

of the magnet does not face the shaft but is perpendicular to it. It is as if the side of the magnet is glued and not the end. Whether the North or South pole faces to the left or right does not matter. It is merely a case of reversing the motor wires to make everything right again. Finding the poles is not that hard. These are the sides where the

magnet is most powerful. When two magnets grab each other the joined surfaces are always the poles. The mirror that deflects the laser beam can be attached with instant glue. When the motor shaft rotates from its neutral position, the polarity of the magnetic field in front of the sensor rotates as well. This is necessary for

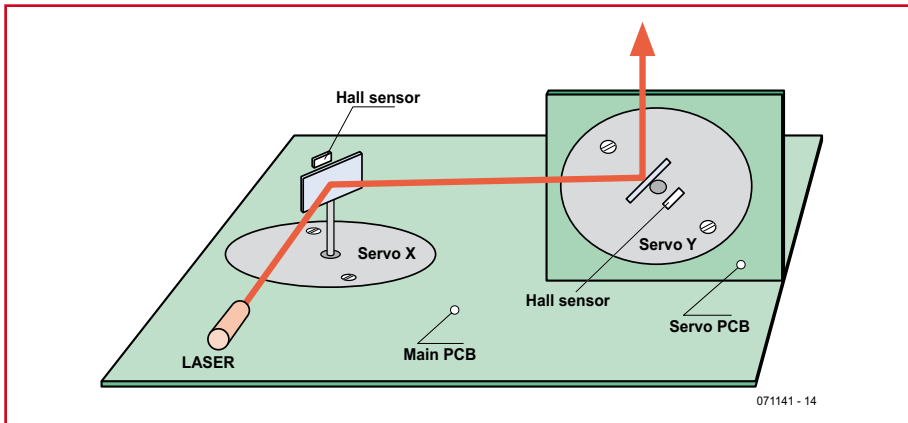


Figure 4. To enable control in both the x- as well as the y-direction the servos can be positioned like this.

mounted and are in the form of two pieces of wire, cut from a resistor lead, for example. These can be soldered onto the motor PCB to the left and right of the screw for the shaft coupling. This completes the servo.

Servo control

The electronics for the servo drive can be kept quite simple (see **Figure 3**). P1 is used to set the input signal sensitivity and determines the maximum projection format. P2 sets a DC-offset, which is used to move the projection image a little, for example. IC1a amplifies the difference between the signal from the magnet sensor and the input signal. When this difference is positive, the motor turns in the opposite direction compared to when this signal is negative. In this way a closed loop is created which is necessary for controlling the servo. IC1b is a proportional-differential (PD) amplifier. This is indispensable to correct the phase of the feedback loop.

IC2 and IC3 are connected as a bridged amplifier for driving the motor. These

ICs, type TDA2030, are intended as an audio amplifier but are functionally just big difference amplifiers that can deliver about 3 A. More than enough for this type of motor. Four diodes prevent the inductive flyback voltage of the motor from damaging the IC.

The power supply voltage for these ICs is provided by a 7809 regulator. With a 9-V power supply, IC2 and IC3 can drive the motor with plus and minus 6 volts. In the prototype IC2, IC3 and the 7809 were all mounted without insulation on a common heatsink.

The current consumption of the servos depends on the amount of drive. This is typically not more than 100-200 mA each. The average power consumption of the entire projector including a 5 mW red laser module is about 300 mA. Batteries will therefore not last very long, but powering from a mains adapter or a small lead-acid battery for 'in-the-field operation' are good options.

Adjusting the servos


When a servo is connect to the drive PCB for the first time, all the potenti-

ometers have to be set to their centre positions. When the power supply is connected, and all is well, the motor now turns such that the magnet is exactly opposite the sensor. If the magnet turns away from the sensor then the motor wires need to be swapped around.

Using HyperTerminal we can send commands via the serial port to the projector. There are two commands for adjusting the step response of the servos: AX and AY (adjust X/Y). After issuing an AY command the step response of the Y-servo is projected. The potentiometers for the PD controller and motor driver now need to be adjusted so that the projection is a nice, clean pulse waveform without showing any oscillation artefacts. The same is true for the X-servo after issuing the AX command. Repeat the adjustment of both servos once more. Measured with an oscilloscope (at the sensor output), the step response time of the prototype was about 2-4 ms, depending on the step size. The -3 dB sine response is about 150 Hz.

In operation

Once the servos are working and are adjusted properly, the projector itself can be tried. The serial port of the projector is connected to the serial port of a PC/laptop. Start HyperTerminal and enter the COM-port settings. A connection can now be established with the ATmega88. You can now enter commands using the keyboard. With the LC command (list commands) the list of available commands is displayed on the screen. Each command consists of two (capital) letters. If there are no parameters this is then immediately followed by pressing the enter key. Commands with parameters are

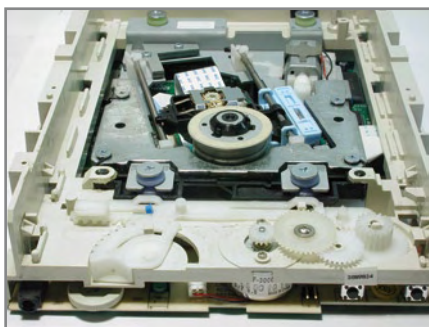


An opened CD-drive. The little DC-motor under consideration sits at the front in the middle.



The little DC-motor as removed from the CD-drive (keep the little mounting screws).



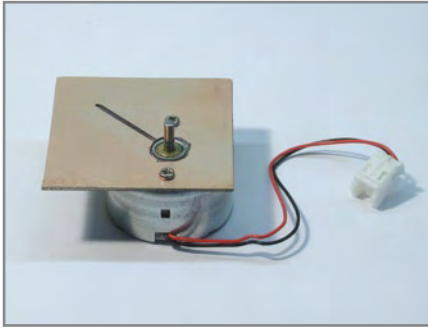
All parts of the servos together: mirror, shaft coupling, magnet sensor and the little magnet.



The little motor mounted on a piece of printed circuit board with the 45-degree line where the magnet sensor has to come.



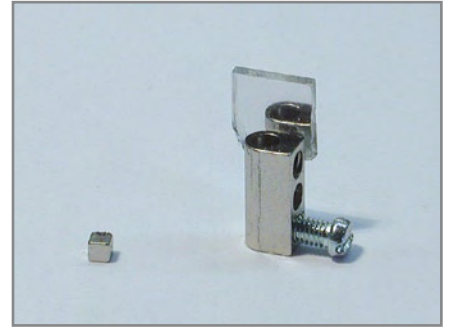The mirror, the shaft coupling and the little magnet, ready to be glued together.



The mirror glued to the shaft coupling; the magnet is next.

entered by typing the command, followed by a space, then a parameter, then another space, etc. Parameters are a number, usually 0-9. There is no checking of the input and therefore there are no error messages either! Using the command MS (mode set), one of four modes can be selected. If the projector is used on an occasion where music is played, it can be nice to show the music as an oscilloscope image on the wall. In this case the sound output from a CD-player, or from a microphone with pre-amplifier, is connected to the Y-input of the controller. After issuing the command MS 3, the projector operates as a projection oscilloscope. The command SS (save settings) can now be used to save everything. If the projector is now switched back on, after having been switched off, it will continue to operate with these same settings and can therefore operate 'stand-alone'. If the projector is to be used as a non-stop text display this can be accomplished as follows: the text is entered with the TX command. The text size and scroll speed are set with TS. The entered text is now projected as a running text display. If the text is displayed in mirror image or upside down then this can be corrected with the RE

command. Once all is correct, the SS command can be used to store everything (including the entered text). To project text, the MS 1 or MS 2 command need to be issued. In mode 1 the text scrolls letter by letter and in mode 2 word by word. With the latter there is the possibility that a word is too long when the letter size is too large. No error detection for this situation is programmed in, users will have to look out for this themselves. An important adjustment is the timing. The software assumes predictable response times of the servos. These are stored as two parameters. Using the TM command with 2 parameters these can be altered and saved with SS. In the TM command the first parameter is a fixed time and the second causes a delay proportional to the size of the projection. The default is: TM 3 4. The projector works well with the default settings, but experimenting with the settings gives you a better feeling for the workings of the projector. For example, TM 1 4 distorts the projection and with TM 4 4 is slower than necessary. Fine adjustment is possible however and can gain some speed which means that texts with larger scroll widths can be used. These would otherwise be delayed too much which results

in a flickering image. This is however only a problem with large letters and a scroll width of more than about 5 characters. Should this experimenting with the settings result in some problems with the display, the LD command (load defaults) can be used to set everything back to the initial state. Don't forget to store this 'reset' with the SS command.

Positioning

Figure 4 and the photos show how the servos can be positioned. It is advisable that the position of at least one servo and also that of the laser is made to be mechanically adjustable. It is important that no laser light misses the mirrors. With a little bit of adjustment of the laser position (height and direction) all of the correct settings are usually easily found. Note that with laser modules the housing is often the + connection. A little piece of heatshrink sleeving is then required for insulation.

Lasers with larger powers


As mentioned before, working with red lasers can be considered safe for pow-




A small nail holds the magnet in place for gluing.



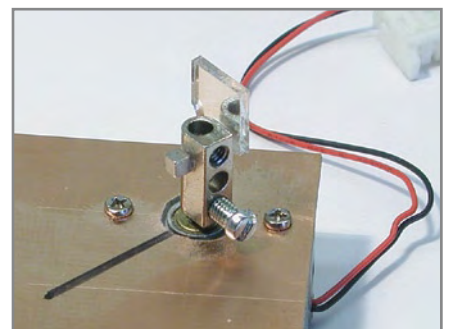
The shaft coupling with mirror and magnet, all glued together.



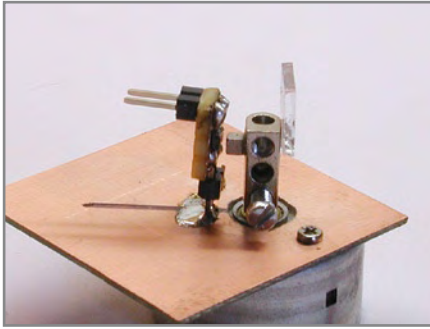
The complete shaft coupling, mounted on the motor shaft. Now the Hall-sensor.



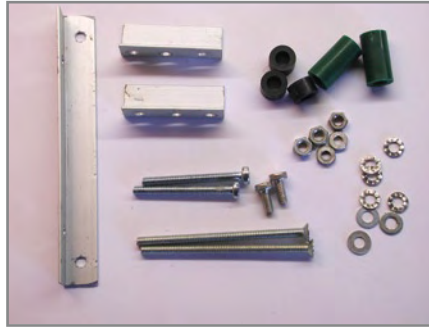The complete servo including the magnet sensor which is held in the correct place with a small PCB.



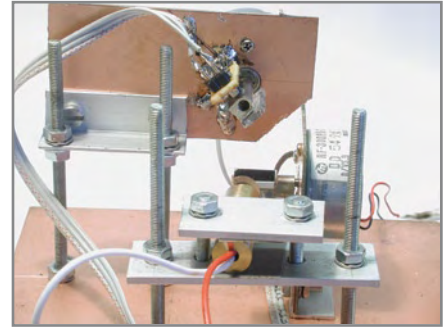We make the mechanical construction with M3 hardware and aluminium angle profile.



The two mounted servos with the laser module in the foreground.


ers up to a few milliwatts (still, never look into the beam). The advantage of a green laser compared to a red one is that the eye is much more sensitive to green light, so that the projection appears much brighter. Green lasers are usually DPSS (Diode Pumped Solid State) types, where the beam of an 808 nm infrared laser diode drives a pair of crystals. These crystals convert the 808 nm beam in two steps to 532 nm (green). The efficiency of this is much smaller than 100% so that, in principle, a big infrared laser diode is required. To illustrate this: a 5 mW red laser diode requires a drive of about 40 mA, a 5 mW green DPSS module needs typically 200 mA.

If you must work with more power, then for a few tens of Euro you can purchase a green laser pointer rated at, for example, 30 mW. These will have to be dismantled, which usually involves sawing to gain access to the driver PCB.

The driver PCB often delivers too little current and/or is too slow. Driving the diode directly with a current source is often the best solution for optimum speed and light output. When the driver PCB is removed, after determining which are the connections to the laser diode, it is best if the laser diode and photo diode are connected in anti-parallel. This is just a case of soldering two pins to each other (usually pin 1 and pin 3, pin 2 is the housing). This is because a laser diode typically has a reverse blocking voltage of no more than 2 V and the photo diode prevents this from being exceeded. Laser diodes are also sensitive to static discharge, so take the necessary precautions. In the circuit of **Figure 1** there is an

additional circuit for driving a bigger laser diode with a constant current and to modulate it. The assumption here is for a current of 500 mA for a 30 mW DPSS module obtained from a laser pointer.

The TDA2030 is configured as a current

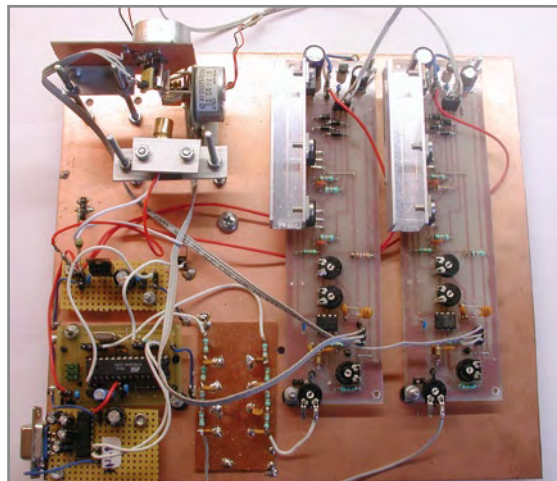

The complete laser projector: the two servo driver PCBs are on the right, the servos are at back left and the controller and RS232 interface are in front on the left.

source which can be modulated with TTL signals and the L200 is added as regulator with current limiter. This is additional safety to protect the expen-

Program fuse settings

```

BOOTSZ = 11
BODLEVEL = 100
CKSEL = 0111
SUT = 11
(brownout VCC = 4,3 V,
ext. full swing XTal)

```

sive laser module from currents greater than about 550 mA. The potentiometer sets the quiescent current which is just below the threshold at which the module starts to 'laser' This serves to slightly increase the average temperature (for optimal light output).

The resistor R is used to set the current through the laser diode and R_L is for the current limit. If the nominal current needs to be 500 mA, for example, it is safe to calculate R_L for 550 mA (500 + 10%).

Applications

There are of course a number of interesting applications for a laser projector. It is, for example, possible to use it for chatting. Two people and two tables with a computer on each can be positioned against opposite walls. The chatters can then see the text of the other person behind/above their monitor on the wall. Using the wall of a larger building it is possible to chat in a group, provided each participant has their own projector, of course.

Another application is the projection of advertising messages in a shop window, for example. This can be done from the inside because the text can be projected mirror-reversed. The text can then be read normally from the outside.

Many other applications can be conceived of, but we leave those up to you.

(071141-1)


Visit

Sponsored by:



Department of
Information Technology
Ministry of Communications
& Information Technology,
Government of India

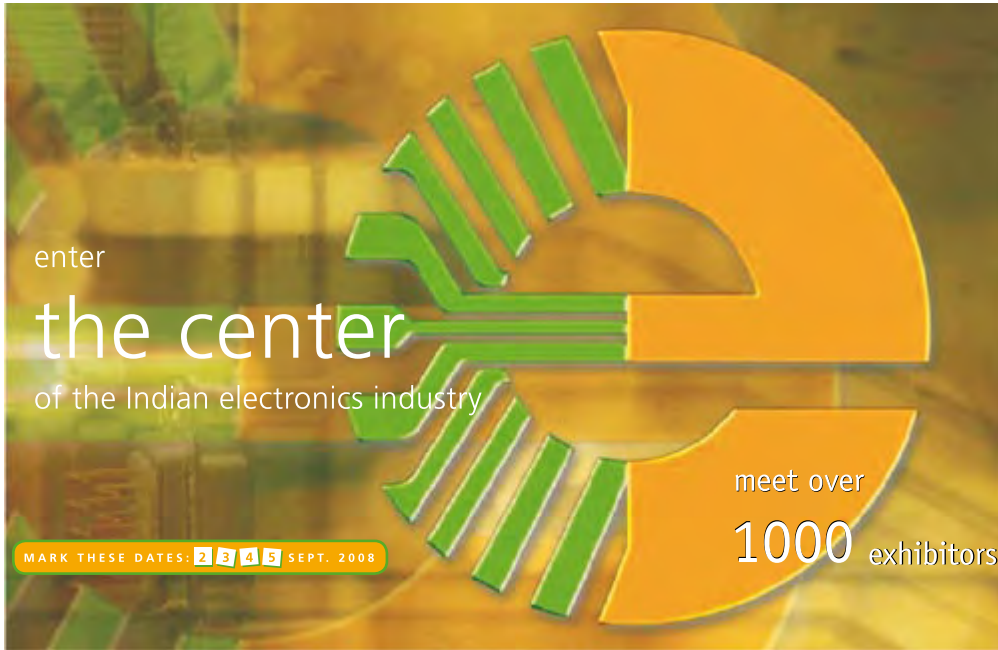India's Largest Show for Electronic Components, Assemblies, Materials and Production Technologies



India's electronics industry is booming in all aspects. Participate in this dynamic growth and exhibit at the 9th electronicIndia in Bangalore, India's "Silicon Valley" and hub to its huge electronics and IT industry. Take advantage of this unique opportunity and present your products and services to a first-rate audience of decision-makers at India's No. 1 electronics forum.

Also Participate in Three International Conferences:

- 1) **EMS/Contract Manufacturing: The Indian Perspective**
- 2) **Symposium: The Trends and Future Requirements in Automotive Electronics**
- 3) **Exploring the Latest Technologies and Tools in Electronics Design**



September 2-5, 2008

Bangalore International Exhibition Centre (BIEC)
Bangalore, India

Platinum Sponsors



Lamp Post Banners Sponsors



Visitor Badge Sponsors



Carry Bag Sponsors



Other Sponsors



Some Key Exhibitors

Almit	ARROW	ASSEMBLEON	Ascent Circuits	AT&S	Bergen Associates Pte. Ltd.	Bergen Systems	Centum	CDIL	CIPSA-RIC India	Digital Circuits	EMS Technologies	EPCOS	Estovir	Farnell	Fuji Electric
Harting	Henkel	Hical	Hynetic	INetNet Resources Pte. Ltd.	INDE Enterprises	IMC	J.A.M.	JUKI	KOMAX	KYORITSU	NMTRONICS	NXP Semiconductors	OK International	PANASONIC	APW President
Relaytronics	RITTAL	SAMSUNG	SCHLEUNIGER	SLN Technologies	SM Electronic Technologies (P) Ltd.	Sumitron	Taiyo Yuden	Tamura Corporation	Tomen Electronics	TRANS-TEC	Truly Electronics Manufacturing Ltd.	Tyco Electronics	Vinyas	Würth	Yokogawa

Co-organisers / Co-sponsors

AEIS	CCPIT	CEIEC	CEAC	CLIK	ELIAP	IET	IGCC	IPCA	TEEMA	VDMA	ZVEI

MMI India Private Limited

23, Deccan Court, S. V. Road, Bandra (West), Mumbai - 400 050. India

Tel.: +91 22 26452101 / 2 / 3, Telefax: +91 22 26516372

E-mail: info@mmi-india.in, info@electronicindia.net URL: www.electronicindia.net



ANDRE LAMOTHE'S
XGAMESTATION
LEARN STEP-BY-STEP HOW TO BUILD
AND DESIGN YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the
Atari 800/2600, Sinclair ZX Spectrum,
Apple II & Commodore 64!

Parallax SX Key Compatible!

INCLUDES:

- Tools, Demos & Utilities!
- Great for Hobbyists AND Students!
- The Fun Way to Learn Embedded Systems!
- Fully Assembled XGS Micro Edition Unit!
- Complete Software Development KIT!
- eBook on Designing the XGS Console!
- Cables and Power Supply included!

WWW.XGAMESTATION.COM
PH: 512.266.2399 | SUPPORT@NURVE.NET






**PCBs in
24 hours
from £30.00**

www.PCBTrain.com

Tel: 01635 40347 Newbury Electronics Ltd
Fax: 01635 35143 Forbury Road, Newbury, Berkshire RG14 2AD
e-mail: enquiries@newburytrain.com www.newburyelectronics.co.uk



**WWW.
elektor.
com**

FLYPCB.com
NOTHING IS IMPOSSIBLE

PCB House
FROM CHINA TO WORLDWIDE

- Start from £30
- Prototype & Production
- No Min Order
- Fast Delivery

IMPOSSIBLE IS NOTHING
SALES@FLYPCB.COM



i-TRIXX

Electronics inside out!

The free e-magazine about internet, computers, hacking, tweaking, modding, gadgets, geekstuff, gaming and DIY electronics. The e-zine you have to check out now!




Receive i-TRIXX in
your mailbox
FOR FREE
each Wednesday!

Play the i-TRIXX Quiz and win!

Test your knowledge about internet, computers and electronics. Take your chance now and play the i-TRIXX Quiz. There are great prizes to win!

From the Elektor labs:

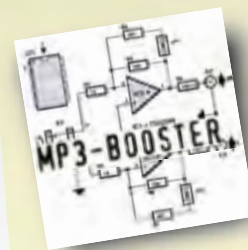

Simple, useful
and fun
electronic
circuits!

Check **i-TRIXX.com** and subscribe now!

Powered by
elektor


E-blocks: Accelerated Design

E-blocks + Flowcode + TINA

John Dobson (Matrix Multimedia)


In this article we take a look at some of the latest techniques you can use to accelerate the design process, in this case of a switch-mode power supply.

Figure 1.
Principle of a step-up ('boost') voltage converter (redrawn from Microchip application note).

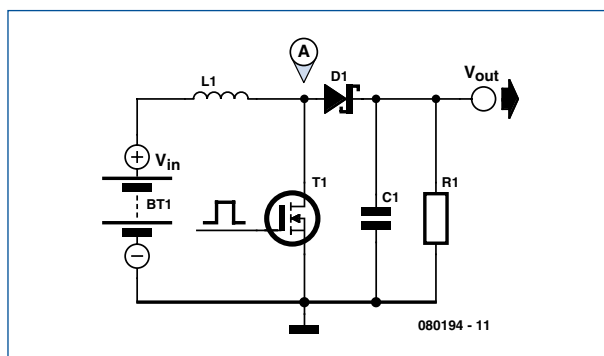

Switched mode power supplies (SMPSUs) are traditionally viewed as a bit of a black art. And with good reason – the mathematics behind the design process is complex, prototyping — often with custom wound inductors — is awkward, and the custom SMPS regulation chips used in the design itself are expensive. However this does not need to be the case: most modern circuits now contain a microcontroller with extra capacity that can be used to control the power supply, and design tools have advanced to a point where virtual prototyping is now possible. Sure, the mathematics is still there – but the use of simulation tools, with a little trial and error, means that if you make a wrong turn, getting back on track is not so difficult. At least that is what we are hoping — we have to assume we're complete novices here!

Figure 2.
Basic circuit of a switch-mode step-up voltage converter (note: schematic for use in TINA, redrawn in Elektor style).

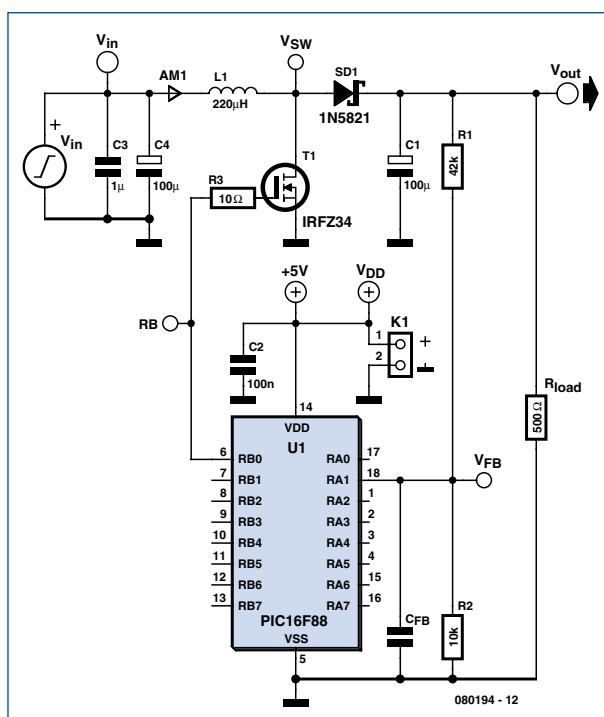

The circuit

We are looking at the possibility of generating a 12 to 15 VDC voltage rail from a 5 VDC supply. This is for an instrument that requires ± 12 V rails. As the application is only for driving a few opamps we only need a few tens of milliamps — if that. Having sniffed around the Internet we came across a Microchip Application Note that describes the use of the elementary circuit in Figure 1.

This is a fairly traditional 'boost converter'. We intend to power the circuit with a 5 V supply — shown as V_{in} . FET T1 is periodically switched on by a pulsed control input — more about this later. At the point where the FET is switched on, a relatively large current is drawn through inductor L1, and the energy stored in the inductor increases. All of this current will be supplied via the 5 V supply — Schottky diode D1 will ensure that no current flows from the second half of the circuit because V_{out} is greater than V_{in} . At the point where the FET turns off, the energy stored in the inductor is released. In this release there will be a voltage surge across the inductor which will result in a larger voltage at point A than the supply voltage. At this time in the cycle diode D1 will start conducting and charge will be pumped across it into C1. As long as the discharge current through the load,

R1, is not too large then the result of this circuit is that the output voltage is larger than the input voltage. So this is a great little circuit that can be implemented relatively cheaply, and will — in theory — do the job we need. Providing that the load is precisely known — and does not change — and a switching waveform of an appropriate frequency and period can be supplied, we are home and dry. Of course these conditions rarely apply — loads vary depending on the actions of the rest of the circuit, components have tolerances and in practice a closed loop system incorporating some method of regulation is going to be needed. A more practical circuit is shown in Figure 2.

This is essentially the same circuit with some additions. As the currents drawn by L1 can be large, a couple of capacitors have been placed across the supply rail for decoupling. The load resistor here is 500 ohms. This will give us around 30 mA as the model load — more than enough for our needs. The FET switching control is governed by a PIC microcontroller output pin. The pulse waveform on this line will determine the charge and discharge of L1. To complete the feedback loop, the circuit output voltage is fed into the PICmicro analogue input pin A1 via a potential divider made up of R1 and R2. The RC network formed by R2 and C_{FB} provides a little smoothing on the feedback signal. The value of C_{FB} can be established empirically.

Software development

The firmware to make the PIC supply the control pulses was developed using Flowcode, the software suite with E-

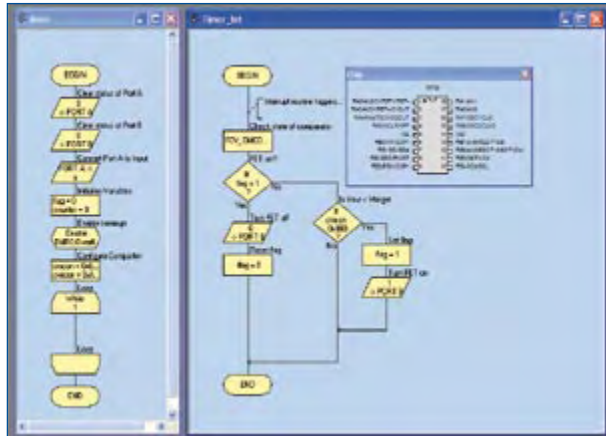


Figure 3. A section of the Flowcode program written for the PIC-controlled SMPSU.

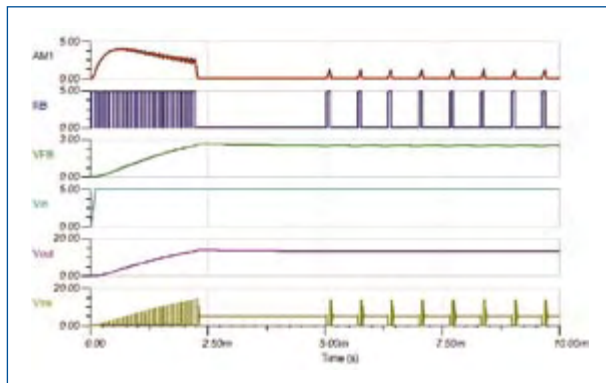


Figure 4. TINA at work showing the response of a virtual circuit running Flowcode-generated ASM code and combining a PIC with analogue components. Now start optimizing without soldering!

Advertisement

See your design in print! Elektor Electronics (Publishing) are looking for Freelance Technical Authors/Designers

If you have

- * an innovative or otherwise original design you would like to see in print in Europe's largest magazine on practical electronics
- * above average skills in designing electronic circuits
- * experience in writing electronics-related software
- * basic skills in complementing your design with an explanatory text
- * a PC, email and Internet access for efficient communication with our in-house design staff;


then do not hesitate to contact us for exciting opportunities in getting your designs published on a regular basis.

Elektor Electronics

Jan Buiting, Editor

P.O. Box 11, NL-6141-AV Susteren, The Netherlands, Fax: (+31) 46 4370161

Email: editor@elektor.com

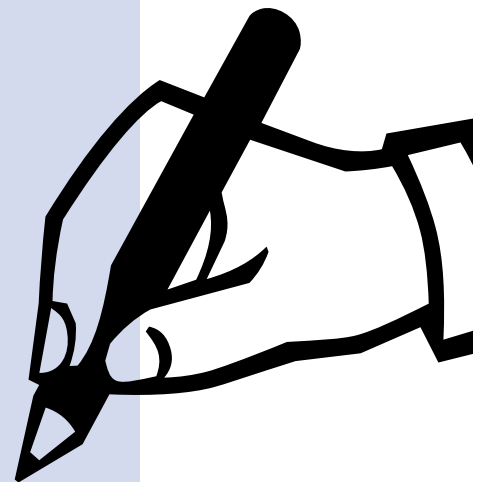

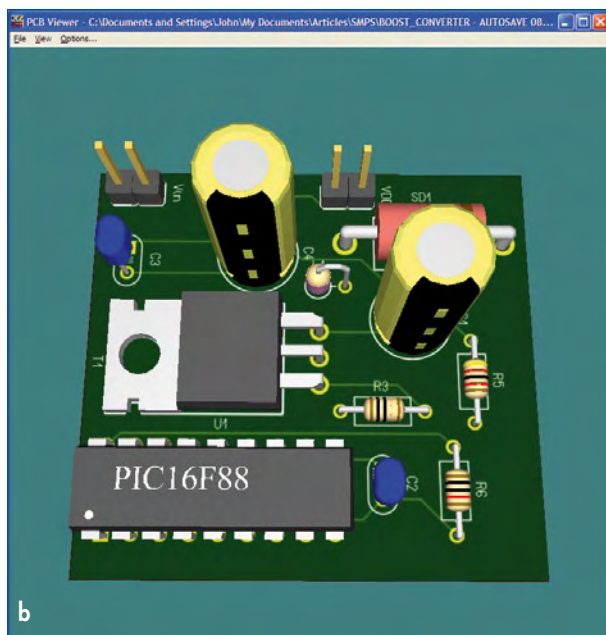
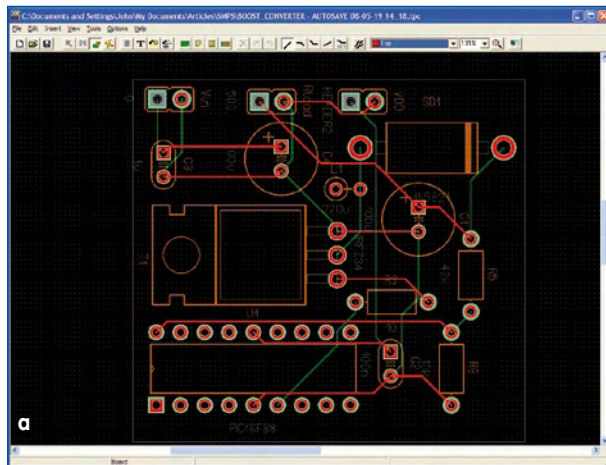


Figure 5. TINA also routes the PCB tracks (5a) and generates a 3-D rendering of the board (5b).

blocks. The program is relatively simple and can be seen in Figure 3. Referring to this and the schematic, here is a description of how the program works. The .fcf file proper sits in archive file 080194.-11.zip on the Elektor website for those that want to study the details.

In the MAIN loop the program sets up the relevant pins as inputs and outputs and sets system variables. An interrupt icon is used to trigger an interrupt at around 10 kHz, equivalent to 100 μ s. Then there is a 'C' icon with the contents:

```
cmcon = 0x02; //set comparator register to compare with internal Vref
```

```
cvrcon = 0xAC; //set internal Vref to Vcc/2
```

A comparator, rather than an A/D, is used because it operates much faster by comparison (the PIC16F88 supports both internal comparators and A/Ds) The last icon in the MAIN flowchart is a While loop which just keeps the program running — all the control is carried out by the timer interrupt routine.

The interrupt routine first reads the internal comparator which compares the feedback at point V_{FB} (on RA1) with

the internal voltage reference. If the voltage is lower than a preset threshold (in this case 80_{hex} which corresponds to about 2.5 volts at pin RA1) then a flag is set and the FET is turned on by pin B0 for one interrupt cycle – around 100 μ s. When the FET is on, current flows through the inductor and when the FET is turned off, the back-EMF produced increases the voltage at point V_{sw} so current flows through the diode. If the voltage at RA1 is above the threshold then the FET is not turned on.

From Hungary comes TINA

Now for the clever bit – the schematic shown in Figure 2 can be entered into in a software package called 'TINA' from DesignSoft [2]. TINA supports a relatively new kind of simulation where you can simulate high-speed analogue circuitry at the same time as simulating your microcontroller running the code you have designed. The process here is simple: design your software using Flowcode, assemble the Flowcode program to ASM code, alter the characteristics of the PIC inside TINA so that the microcontroller is associated with the relevant ASM file and then simulate the circuit. You can see the results of the simulation in Figure 4.

The first trace shows the current drawn at point AM1 through the inductor, the second trace shows the state of RBO, the third trace shows the feedback voltage, the fourth shows the input voltage V_{in} , the fifth trace shows the output voltage, and the last trace shows the voltage at the junction of the FET drain and the inductor. Whilst there is some ripple on the output the voltage is a pretty steady 14 V. The big surprise for me here was the amount of current taken in the first few milliseconds and the size of the subsequent bursts which are more than an amp!

Getting practical (again)

So having got the simulation working we used an E-blocks Multiprogrammer and a Prototype Board to put the circuit together. The system seems to work well with around 13.5 V at 30 mA. If you try to lower the load resistor and draw more current then all sorts of strange things happen as the 7805 regulator we are using starts its impression of a toaster and cuts out at regular intervals resetting the PIC. As an added bonus here it makes a noise like a rat being strangled — stand clear!

The PCB design and 3-D rendering generated using TINA are shown in Figure 5. The exercise once again proves that both Flowcode and E-blocks are far more 'open' products than is often assumed, and right up the street of anyone starting out in microcontrollers, whether PIC as demonstrated here or AVR.

(080194-1)

Web Links

- [1] www.elektor.com/080194 (Free downloads)
- [2] www.tina.com

E-blocks
 E-blocks is a modular system designed to learn microcontroller programming at various levels. The current product range comprises about 70 modules and ancillaries for PIC, AVR and ARM platforms. E-blocks systems employ the 'Flowcode' graphics programming software tool. E-blocks are available from the Elektor SHOP; see www.elektor.com/e-blocks.

E BLOCKS™

LEARN • DESIGN • BUILD

Flowcode has evolved! Flowcode is now available for two new microcontrollers: the Atmel AVR range and the Atmel AT91 ARM 7 range. You can now buy these new products individually or you can buy a bundle of all three - Flowcode ultimate. If you are already a Flowcode user then please contact Elektor for details of how you can upgrade your current version of Flowcode.



FLOWCODE ULTIMATE
Buy three, pay two!

Our range of more than 43 hardware circuit boards, CD-ROMs, sensors and accessories has just got bigger.

In addition to the new versions of Flowcode we now have bundles to allow you to rapidly develop systems based on RFID and Zigbee technology.

BENEFIT NOW!

The retail price of our bundles is at a significant discount to the sum of the individual parts. You'll save a massive 30% discount w.r.t. individual items!

Ordering

Use the order form near the end of the magazine or go to www.elektor.com (shop). E-blocks will be shipped after receipt of payment. Prices are exclusive of postage.

£184.50

Starter Kit Professional for AVR

This bundle consists of a copy of Flowcode 3 for AVR, an LED E-Block (8 leds), a switch E-Block (8 switches), an LCD E-Block (2 line 16 character), an E-blocks AVR board with an AVRISPmk2 programmer, a USB cable and power supply.

£193.85

Starter Kit Professional for ARM

This bundle consists of a copy of Flowcode 3 for ARM, an LED E-Block (8 leds), a switch E-Block (8 switches), an LCD E-Block (2 line 16 character), an E-blocks ARM board, a USB cable and power supply.

£475.60

Easy Zigbee Kit

This bundle includes a copy of Flowcode V3 professional, three E-blocks PICmicro professional, three E-blocks multi-programmers, LCD board, LED board, switch board, three Zigbee boards, two sensor boards, power supply, and three 16F877A devices.

£243.70

Easy RFID Kit

This bundle includes a copy of Flowcode V3 professional, an E-blocks PICmicro professional, an E-blocks multi-programmer, LCD board, LED board, switch board, power supply, two Mirfare type RFID cards, two I-code SLI type RFID cards and a spare 16F877A device.



Ultrasonic Sound Detector

track down high frequencies

Ton Giesberts

Using the circuit described here you can quickly and simply check whether harmful sounds with a high frequency are being produced somewhere nearby, especially important at locations where the so-called ultrasonic teen-deterrents against loitering youths are installed. Ten LEDs indicate the sound pressure of signals with frequencies between 16 and 40 kHz.

These days, to harass loitering youths into leaving, an 'ultrasonic' sound system is often used (such as the Mosquito). Such a system generates, in the vicinity of a popular gathering place, a sound with frequencies between 17 and 20 kHz. This sound appears to be very irritating to youths, with the result that they soon move on. Older people appear to be unable to hear these frequencies and are therefore not bothered by them.

The term 'ultrasonic' is actually not quite correct. Ultrasonic sound is normally used to describe the range of frequencies that are above the range of human hearing, that is, above 20 kHz. Because the frequencies used are below 20 kHz, they are not only audible to loitering youths (insofar as they don't have any hearing damage), but they are even better heard by babies, small children and pets. The sound pressure is not all that high, according to data provided by the manufacturer. But if the ultrasonic deterrent is nevertheless considered to be annoying, it is very likely to be even more irritating to babies and small children (and that is not taking into account the potential hearing damage by prolonged exposure).

Babies and pets cannot say what is wrong (with the exception of parrots perhaps). So if you are walking through the city with a baby there is the chance that the child is exposed to

these types of sound without the parents realising.

So that you can quickly get an indication whether harmful sounds with a high frequency are being produced somewhere, we designed an indicator that can detect these signals and measures their intensity. Ten LEDs show the sound pressure of sound in the frequency range from 16 to 40 kHz. Lower frequencies are suppressed by a fifth-order, high-pass, Butterworth filter so that the indicator will not react to speech and other everyday sounds. When designing the measuring range for the indicator the decision was made for maximum deflection at a sound pressure of 90 dB. If you are exposed to 90 dB for more than an hour then there is the risk of permanent hearing damage. Whether you can also suffer hearing damage from frequencies you cannot hear any more, wear of the auditory ossicles for example, has not been researched yet.

Schematic

The circuit shown in **Figure 1** may look quite involved, but it is really not that bad. The circuit comprises a microphone amplifier, a fifth-order high-pass filter, an active rectifier, a buffer stage and finally the display driver with ten LEDs. For driving these LEDs we used the old, trusty LM3915 in dot-mode (we deliberately did not choose bar-mode because of the current consumption). This IC is configured for its simplest

application with REF ADJ connected to ground. In this configuration the input signal has to be $1.28 V_{DC}$ (typically) for 'full deflection'.

Working backwards from this value and the sensitivity of the electret-microphone that is used, we can calculate the required gain. For the microphone we chose a type that can be obtained from Farnell (the Kingstate type KEEG1542TBL-A). This choice was mainly determined by the frequency response curve shown in the datasheet (which can be downloaded courtesy Farnell). This shows a slight increase towards 20 kHz, which leads us to conclude that it will still be usable at frequencies a little over 20 kHz. While there may be a lot of ripple in the curve above 20 kHz this is not a problem since we're only looking for an indicative measure of sound pressure. At 90 dB the microphone module will give an output of about 8 mV. When we take into account that the rectifier contains a peak detector (makes a difference of $\sqrt{2}$ in the gain) and that the sensitivity of the microphone can vary by up to ± 3 dB, we therefore need a circuit with a minimum gain in the region of 80 to 160.

The input contains a gain stage (IC1A) which amplifies 40 times. This also cuts off the lowest frequencies at the same time (C1 and C4). C3 and C5 compensate a little for the slight drop of frequency response above 20 kHz. For the opamps the ST type TS924IN quad rail-

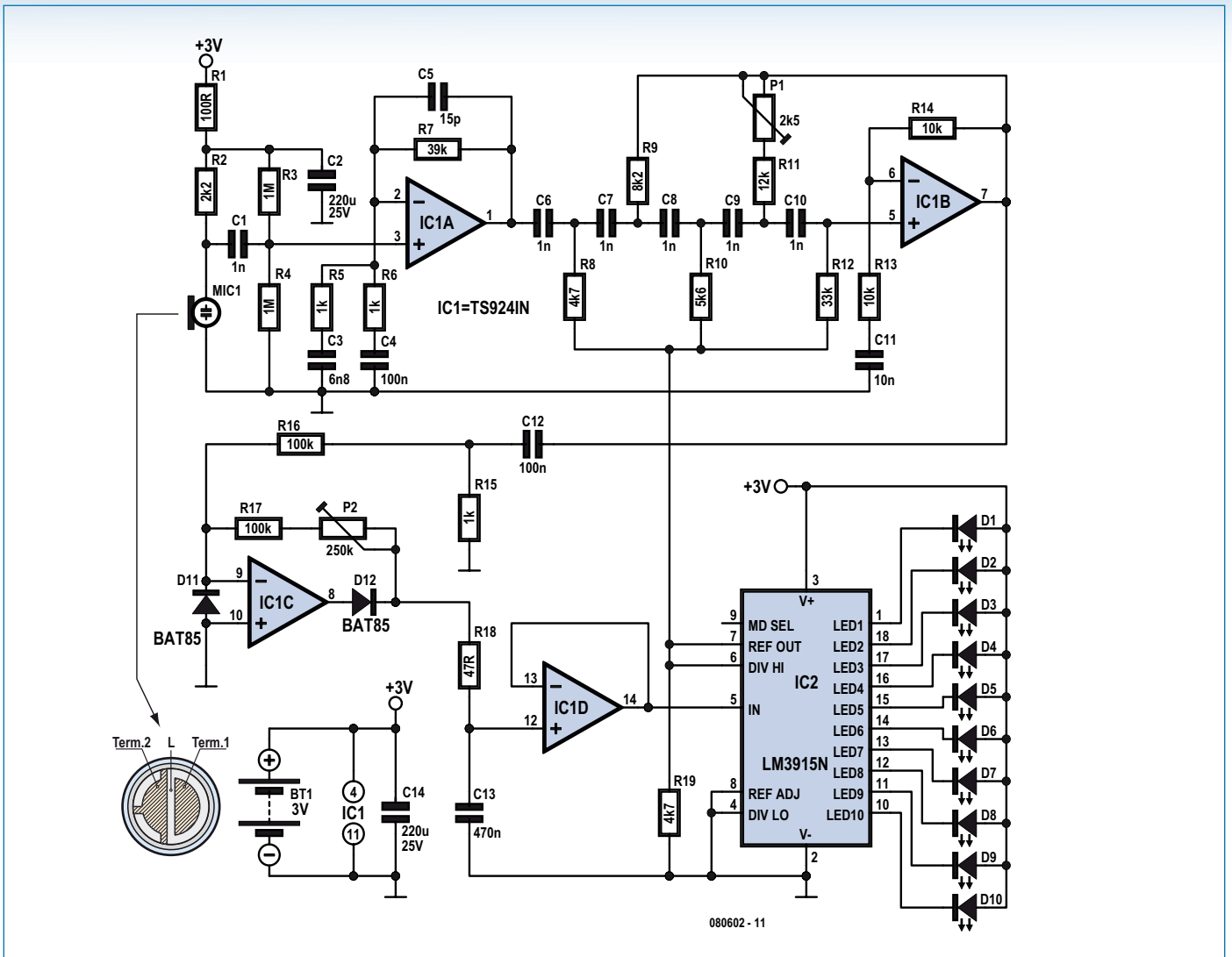
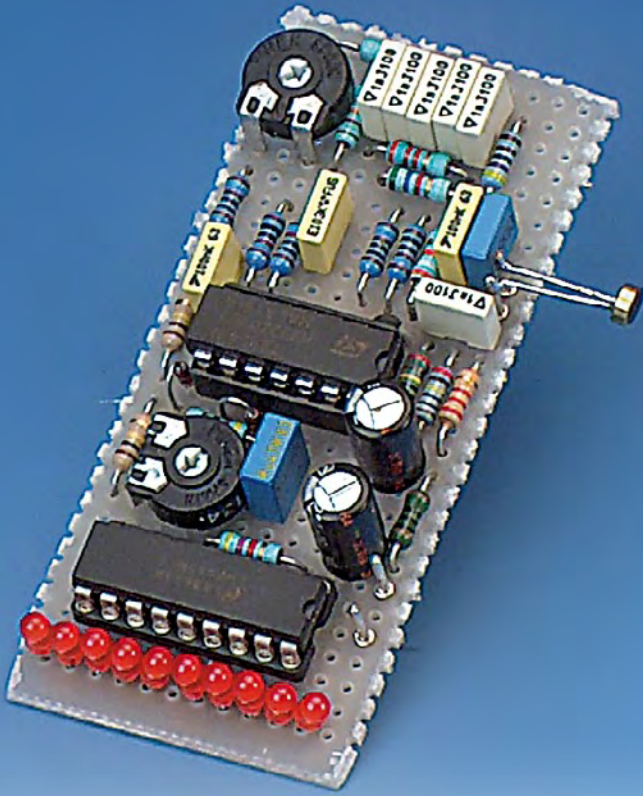


Figure 1. With this circuit you can very easily track down high-frequency audio signals.

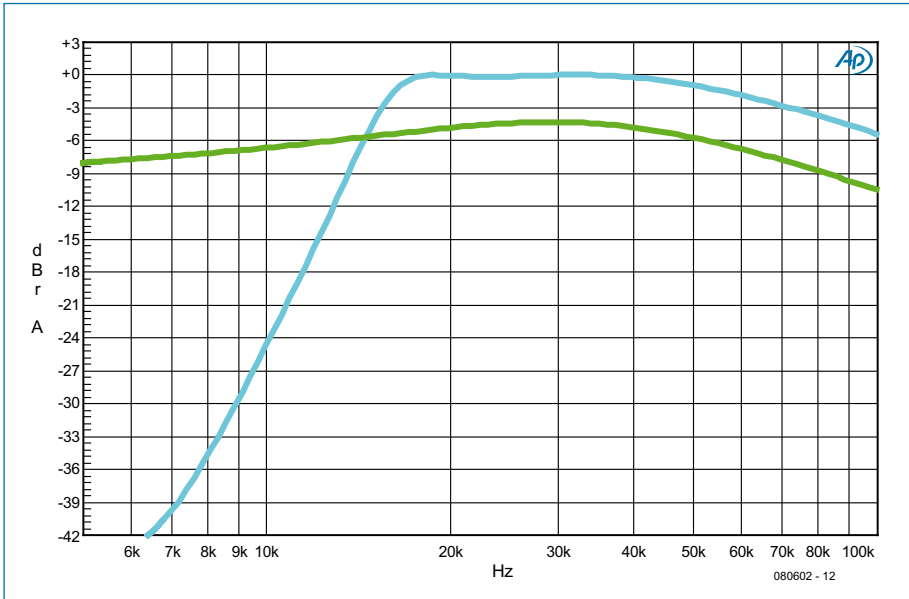


Figure 2. The frequency characteristic of the input amplifier on its own (green) and the input amplifier followed by the high-pass filter (blue).

to-rail device was selected, which can deliver no less than 80 mA. This opamp has a relatively large GBW (gain-bandwidth product) of 4 MHz, so that the bandwidth of the input amplifier at a gain of 40 is still 100 kHz (C5 is only for RF decoupling), more than enough for this application. This is followed by a steep filter built around IC1B that passes only frequencies above 16 kHz (-3 dB). The measurement curves (Figure 2) show the amplitude response of the input amplifier on its own and that of the input amplifier followed by the filter. For the proper operation of the fifth-order filter a buffer is not enough, but the opamp needs to have a gain of 2 (this can be seen clearly in the measurement curves). This is a fortunate circumstance since the

other stages now don't need to have as much gain.

The filter contains an adjustable component to allow for the compensation of component tolerances. P1 can be used to make the curve as straight as possible. If you do not have the means to measure this then you can use the nominal value of 870 Ω for P1 instead. It is still recommended to measure and select C6 through C10 for equal values. The rectifier around IC1C is a standard implementation, where the usual diode between the output of the opamp (pin 8) and the inverting input (pin 9) is not necessary because the output cannot go negative. To ensure correct operation, the rectifier is AC-coupled (R15/C12) to the output of

the filter. D11 protects the input of the opamp from excessive negative input voltages.

The output voltage of the rectifier (cathode of D12) charges capacitor C13 to the peak value via R18. The purpose of R18 is to limit the maximum charging current. With the values as shown, C13 is charged relatively quickly, the RC time-constant is only 22 μs. The total amplification of the circuit can be adjusted over a wide range with P2 so that other (less sensitive microphones) can be used as well. The discharge time of C13 varies somewhat with the setting of P2, but that is not important here.

The fourth opamp (IC1D) is used as a buffer to drive the LM3915.

Although the resolution of the LM3915 is 30 dB (10 × 3 dB) but because of the simple design of the rectifier the voltage across C13 is not exactly proportional to the input signal. The bottom LED D1 lights up at -21 dB compared to the voltage required to turn on the topmost LED (D10).

The current consumption of the whole circuit is between 11 and 15 mA, good for six days of continuous use. The circuit appears to work down to nearly 2 V, so that instead of alkaline batteries rechargeable batteries could be used as well. This is much more environmentally friendly.

If you like to experiment, you could try to make a small parabolic reflector so that you can pinpoint the source of the ultrasonic sound. The microphone needs to be mounted at the focal point of the reflector. Perhaps even a small horn is already enough...

(080602-1)

Advertisement

Your price conscious PCB supplier



Interested? Contact us: +44 2088 167 005
E-mail: euro@eurocircuits.com
www.eurocircuits.com

Online price calculation
Online ordering
Online order tracking
Online 24/24H and 7/7D

Verified

- pooling for standard boards
- up to 6 layers
- from 1 to 1000 pieces
- from 3 working days onwards

A la carte

- pooling with more options
- up to 8 layers
- from 1 to 1000 pieces
- from 3 working days onwards

On demand

- your board, our challenge
- up to 16 layers
- from 1 piece onwards
- from 3 working days onwards

GIGANTIC!



The Elektor PLUS subscription

Keep **£44.80** in your pocket!

Elektor PLUS advantages

- Cheaper than 11 issues from the newsstand
- More than £10 discount on the new Annual CD-ROM
- With every issue subscribers get up to **40% discount** on selected Elektor products
- As a welcome gift you get a **free** 2GB MP3 player worth £31.50
- No queues, travelling, parking fees or "sold out" Elektor is supplied to your doorstep every month
- Always up to date – read your copy before everyone else

You save:	Subscription PLUS
£39.00	10 Magazines
+ £5.80	1 Double Issue (July/August)
+ £17.50	Annual CD-ROM
+ £31.50	2GB MP3 player
<hr/>	
= £93.80	Total value of individual items
- £49.00	Elektor year subscription PLUS
<hr/>	
= £44.80	Your saving

www.elektor.com/subs • Tel. +44 (0) 20 8261 4509

Or use the subscription order form near the end of the magazine.

elektor
electronics worldwide

Hexadoku

Puzzle with an electronics touch

After the colossal — but reportedly not too difficult — AlphaSudoku puzzle in the Summer Circuits edition we cheerfully continue with a regular Hexadoku. As before, do participate! All correct entries received enter a prize draw for an E-blocks Starter Kit Professional and three Elektor Shop vouchers.

The instructions for this puzzle are straightforward.

In the diagram composed of 16 x 16 boxes, enter numbers such that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once in each column and in each of the 4x4 boxes (marked by the thicker black lines).

A number of clues are given in the puzzle and these determine the start situation.

All correct entries received for each month's puzzle go into a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the grey boxes. The puzzle is also available as a **free download** from our website.

SOLVE HEXADOKU AND WIN!

Correct solutions received enter a prize draw for an

E-blocks Starter Kit Professional

worth **£248.55**

and three **Elektor SHOP Vouchers** worth £35.00 each.



We believe these prizes should encourage all our readers to participate!

The competition is not open to employees of Elektor International Media, its business partners and/or associated publishing houses.

PARTICIPATE!

Please send your solution (the numbers in the grey boxes) by email to: **editor@elektor.com** - **Subject: hexadoku 9-2008** (please copy exactly).

Include with your solution: **full name and street address.**

Alternatively, by fax or post to: **Elektor Hexadoku Regus Brentford - 1000 Great West Road - Brentford TW8 9HH United Kingdom - Fax (+44) 208 2614447**

The closing date is **1 October 2008.**

PRIZE WINNERS

The solution of the June 2008 puzzle is: **0EA75.**

The **E-blocks Starter Kit Professional** goes to: John Hall (UK).

An **Elektor SHOP voucher worth £35.00** goes to: Francois Herbert (NZ); Antonescu Alexandru-Florian (RO); Sven Skjenneberg (N).

Congratulations everybody!

F		1			7	9		A			8		4	2	
					0			1		B		7	3		E
A			E	B	5			3	C	7	2		F	1	
7	9		3		1		C						B	A	0
8		5		3	2	F					9	E		0	D
C	1	3		8									2		
				4		C			2				1	5	8
2	E		F		9			D	C	1	3	7		A	
6	3			9			8	C	4		B	5			7
	2			6	3		4			8	D	B	A	F	
		A	8		C			F		5		6			2
	B	C	4	7		E		9					D	3	1
1		0	A		8			D							C
		6			F	0		2	5		E		8		
D	8	7	2			1	B	6		0				9	5
		E	5	2		D	9	4	8				1		B

(c) PZZL.com



7	1	0	5	F	4	2	A	8	C	3	6	D	9	B	E
D	2	8	9	1	0	E	3	B	4	7	5	C	6	A	F
F	4	3	6	D	B	8	C	E	A	1	9	2	7	5	0
A	B	E	C	6	5	9	7	F	0	2	D	4	3	1	8
9	3	2	D	B	7	6	1	4	5	E	A	0	F	8	C
E	C	5	8	2	A	3	4	7	1	F	0	6	B	9	D
B	7	1	A	5	9	F	0	6	D	C	8	3	E	4	2
4	F	6	0	E	8	C	D	2	9	B	3	5	A	7	1
8	A	F	2	C	E	4	5	3	6	9	1	B	0	D	7
0	6	B	7	8	D	1	2	C	E	A	4	F	5	3	9
C	D	4	E	9	3	7	B	5	F	0	2	8	1	6	A
3	5	9	1	0	F	A	6	D	B	8	7	E	C	2	4
5	E	A	F	7	C	D	8	1	2	6	B	9	4	0	3
1	8	C	B	A	2	5	9	0	3	4	F	7	D	E	6
2	9	D	4	3	6	0	E	A	7	5	C	1	8	F	B
6	0	7	3	4	1	B	F	9	8	D	E	A	2	C	5

E1T decade scaler tube (ca. 1954)

Rui Figueiredo

A previous instalment of Retronics discussing the 'Dekatron' decimal counter valve [1] having aroused my attention through feedback published in Elektor's Mailbox section, I thought I'd alert the Editor to another counter tube, the Philips E1T. A good amount of information on the actual use of the device being available on the Internet (see web links), I decided to concentrate on the scientific environment at the time when the E1T was 'prima donna'.

First produced at around 1954, the E1T combines a display, a scratch memory and a counter in one device. Even for those not familiar with electron tubes, the diagram (reproduced from radiomuseum.org) gives an idea about the operation of the E1T and how it fits in a counter cascade arrangement. The E1T may be likened to a small cathode ray tube (CRT) in which the count/display readout (0 through 9) jumps from digit to digit under the control of deflection plates (E) with internal feedback maintaining the position until a new pulse occurs (see dynamic characteristics). The 10th pulse causes the beam to collide with reset anode a1 (D). The resulting negative pulse is processed by an E90CC dual triode connected as a monostable generating two pulses (or 'flags' if you like): a carry bit to drive the next decade, and a cutoff level to reset the E1T to zero. The system,

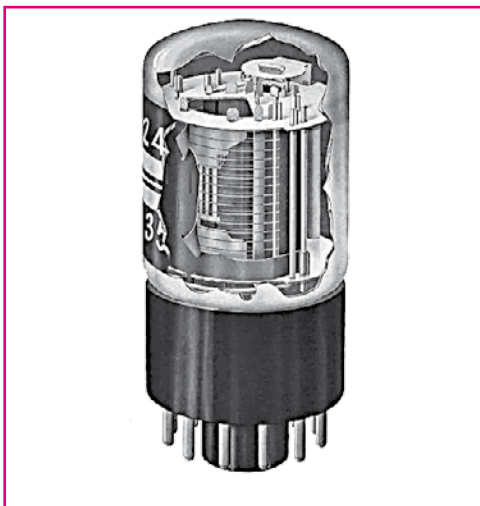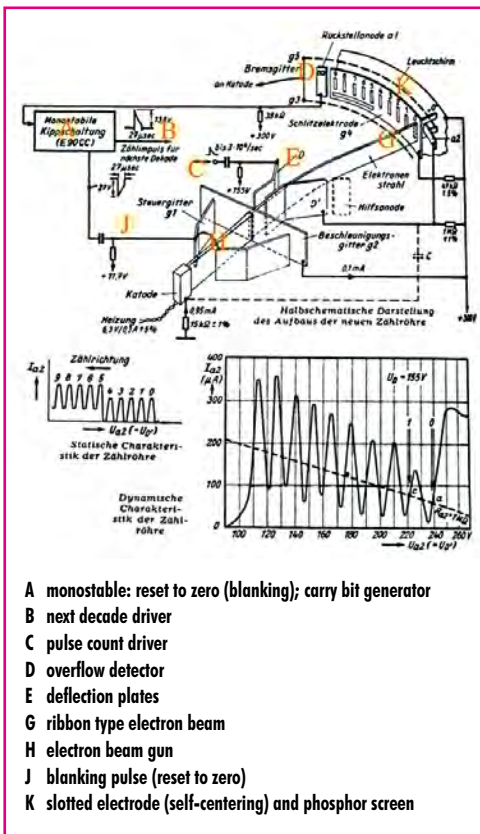

devised almost 60 years ago, is the precursor of 'overflow-with-carry' in a microprocessor!

The use of the E1T seems restricted to Philips' own scientific division as well as high-end professional instruments and equipment including radar, nuclear and x-ray (XRD, XRF). In the latter application (without computers or calculators!) Bragg's law ($n\lambda = 2d \sin \theta$) was traditionally relied on to count pulses. To cope with the tremendous 'intensity' variations expressed as the number of pulses and their amplitude, two techniques became established after some time. The first was counting all pulses coming from the detector (a Geiger or Flow counter), the second, applying the pulses to a pulse level detector set to 'threshold' or 'window' mode. A linear amplifier supplying output pulse levels between (almost) 0 V and 100 V_{pk} was usually inserted between the counter output and the pulse analyser.

The E1T's maximum 'speed' of about 30 kHz was a limiting factor, as well as the 27 μs necessary to reset the decades to zero (minimum safe width for non-selected tubes). This required the use of a prescaler if, say, three E1Ts were intended to constitute a counter readout.

Usually, the prescaler was a pure 8-bit counter using E90CC triodes with neon lamps as bit readers. Thus any value on the three E1T decades has to be multiplied by the prescaler-selected factor and added to

the binary counter for better accuracy.

The E1T was designed conceptually at around 1946 by Adrian van Overbeek of the famous Philips NatLab (PhysLab), based on earlier research by Jan Jonker. Later, another NatLab worker, Kees Van der Velden (now C. Keith Vandervelden) further perfected the device under supervision of the legendary Klaas Rodenhuis of Philips TubeLabs.

Probably due to cost, the E1T was not mass-produced like other Philips tubes. Yet it's not rare and Rodenhuis once said that the 10,000 or so devices around had been ordered from Philips TubeLabs' sample department (!). He also confirmed that 'E' was for 6.3 V heater, 'T' for 'tellerbuis' (counter tube) and '1' for the first device in the series. See, you could count on Philips for consistency in type designations!

(080365-1)

This month's free Retronics download is the E1T datasheet.

Reference

[1] The 'Dekatron' decimal counter valve, Elektor March 2008.

Web Links

- www.radiomuseum.org/tubes/tube_e1t.html
- www.dos4ever.com/trochotron/TROCH.html
- www.dos4ever.com/E1T/E1T.html
- www.tube-tester.com/sites/nixie/different/e1t-tubes/e1t.htm
- www.lks.physik.uni-erlangen.de/diffraction/iinter_bragg.html
- http://www-outreach.phy.cam.ac.uk/camphy/xraydiffraction/xraydiffraction7_1.htm

ELEKTOR SHOWCASE

To book your showcase space contact Huson International Media

Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

ATC SEMITEC LTD

www.atcsemitec.co.uk

Thermal and current-sensitive components for temperature control and circuit protection;

- NTC Thermistors
- Thermostats
- Thermal Fuses
- Current Diodes
- Re-settable Fuses
- Temperature Sensors

Call today for free samples and pricing

Tel: 01606 871680 Fax: 01606 872938

AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple... with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232 interfaces.



See our webpage for more details. From £10.00.

BETA LAYOUT

www.pcb-pool.com

Beta layout Ltd Award-winning site in both English and German offers prototype PCBs at a fraction of the cost of the usual manufacturer's prices.



BOWOOD ELECTRONICS LTD

www.bowood-electronics.co.uk

Suppliers of Electronic Components

- Semiconductors
- Opto Electronics
- Passives
- Enclosures
- Switches
- Stripboard
- PCB Materials
- Popular Special Offer Packs

Online Store, all major cards

Same day despatch upto 3.00pm

Personal Service sales@bowood-electronics.co.uk

Tel: 01246 200222.

C S TECHNOLOGY LTD

www.cstech.co.uk

Low cost PIC prototyping kits, PCB's and components, DTMF decoder kits, CTCSS, FFSK, GPS/GSM, radio equipment and manuals. PCB design and PIC program development.

DECIBIT CO.LTD.

www.decibit.com

- Development Kit 2.4 GHz
- Transceiver nRF24L01
- AVR MCU ATmega168



DESIGNER SYSTEMS

<http://www.designersystems.co.uk>

Professional product development services.

- Marine (Security, Tracking, Monitoring & control)
- Automotive (AV, Tracking, Gadget, Monitoring & control)
- Industrial (Safety systems, Monitoring over Ethernet)
- Telecoms (PSTN handsets, GSM/GPRS)
- AudioVisual ((HD)DVD accessories & controllers)



Tel: +44 (0)1872 223306

EasyDAQ

www.easydaq.biz

- USB powered, 4 relays + 4 DIO channels
- Will switch 240VAC @ 10 amps
- Screw terminal access
- LabVIEW, VB, VC
- Free shipping
- From £38



Design & supply of USB, USB Wireless, Ethernet & Serial, DAQ, Relay & DIO card products.

info@easydaq.biz

EASYSYNC

<http://www.easysync.co.uk>

EasySync Ltd sells a wide range of single and multi-port USB to RS232/RS422 and RS485 converters at competitive prices.



ELNEC

www.elnec.com

- device programmer manufacturer
- selling through contracted distributors all over the world
- universal and dedicated device programmers
- excellent support and after sale support
- free SW updates
- reliable HW
- once a months new SW release
- three years warranty for most programmers



YOUR ELECTRONICS OPEN SOURCE

<http://dev.emcelettronica.com>

Website full of Projects and Resources for Electronics Engineers and DIY.

- Tutorial
- Hardware (Schematic & Gerber)
- Firmware (Asm & C)
- Reference Design



Everyone can submit a story as a useful source! 'Share for life'

FIRST TECHNOLOGY TRANSFER LTD.

<http://www.ftt.co.uk/PICProTrng.html>

Microchip Professional C and Assembly

Programming Courses.

The future is embedded.

Microchip Consultant / Training Partner developed courses:

- Distance learning / instructor led
- Assembly / C-Programming of PIC16, PIC18, PIC24, dsPIC microcontrollers
- Foundation / Intermediate



FLEXIPANEL LTD

www.flexipanel.com

TEAclippers - the smallest PIC programmers in the world, from £20 each:

- Per-copy firmware sales
- Firmware programming & archiving
- In-the-field firmware updates
- Protection from design theft by subcontractors



FUTURE TECHNOLOGY DEVICES

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers, these devices simplify the task of designing or upgrading peripherals to USB



ILP ELECTRONICS LTD

www.ilpelectronics.com

Tel +441233750481

Fax +441233750578

ILP have been manufacturing audio modules since 1971 and apart from our standard range we also offer a custom design service for the OEM market.



products and services directory

LONDON ELECTRONICS COLLEGE

<http://www.lec.org.uk>

Vocational training and education for national qualifications in Electronics Engineering and Information Technology (BTEC First National, Higher National NVQs, GCSEs and GCEs). Also Technical Management and Languages.



MQP ELECTRONICS

www.mqp.com

- Low cost USB Bus Analysers
- High, Full or Low speed captures
- Graphical analysis and filtering
- Automatic speed detection
- Bus powered from high speed PC
- Capture buttons and feature connector
- Optional analysis classes



OBD2CABLES.COM

<http://www.obd2cables.com>

- Thousands of OBD cables and connectors in stock
- Custom cable design and manufacturing
- OBD breakout boxes and simulators
- Guaranteed lowest prices
- Single quantity orders OK
- Convenient online ordering
- Fast shipping

Visit our website, or email us at: sales@obd2cables.com



ROBOT ELECTRONICS

<http://www.robot-electronics.co.uk>

Advanced Sensors and Electronics for Robotics

- Ultrasonic Range Finders
- Compass modules
- Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- Wireless Telemetry Links
- Embedded Controllers



ROBOTIQ

<http://www.robotiq.co.uk>

Build your own Robot!
Fun for the whole family!

- Meccano™ Compatible
- Computer Control
- Radio Control
- Tank Treads
- Hydraulics



Internet Technical Bookshop,
1-3 Fairlands House, North Street, Carshalton,
Surrey SM5 2HW
email: sales@robotiq.co.uk Tel: 020 8669 0769

RADIOMETRIX

www.radiometrix.com

The leading global developer of ISM band, low power radio modules for wireless data transmission:

- Transmitters • Receivers • Transceivers
- RF modems • Evaluation Kits



SCANTOOL.NET

<http://www.scantool.net>

ScanTool.net offers a complete line of PC-based scan tools for under £50.

- 1 year unconditional warranty
- 90 day money back guarantee
- For use with EOBD compliant vehicles
- Fast shipping
- Compatible with a wide range of diagnostic software

Visit our website, or email us at: sales@scantool.net



USB INSTRUMENTS

<http://www.usb-instruments.com>

USB Instruments specialises in PC based instrumentation products and software such as Oscilloscopes, Data Loggers, Logic Analysers which interface to your PC via USB.



VIRTINS TECHNOLOGY

www.virtins.com

PC and Pocket PC based virtual instrument such as sound card real time oscilloscope, spectrum analyzer, signal generator, multimeter, sound meter,



SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £220 + VAT (£20 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description
- For £330 + VAT for the year (£30 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour

image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So-please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for £220 + VAT
- Text and photo for £330 + VAT

NAME: ORGANISATION:

JOB TITLE:

ADDRESS:

..... TEL:

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998

COMPANY NAME

WEB ADDRESS

30-WORD DESCRIPTION

.....

.....


.....

.....

.....

Going Strong

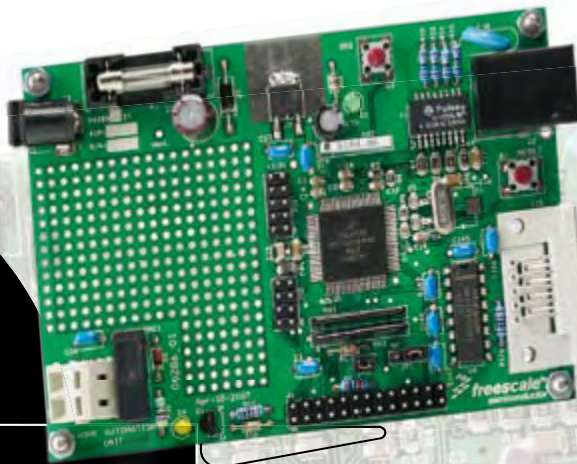A world of electronics from a single shop!



Bestseller!

DigiButler

(May & April 2008)

A low-cost home automation server based on a Freescale Coldfire 32-bit microcontroller. The project has been designed with open source in mind and doubles as a powerful Coldfire development system using free CodeWarrior software from Freescale. DigiButler activates electrical appliances in and around the home, accepting on/off commands from a WAP phone, through an Ethernet network or via a webpage at an allocated IP address and with full access security.

Kit of parts including SMD-stuffed PCB, programmed microcontroller, all leaded parts and CD-ROM containing both Elektor articles, TBLCF documentation, datasheets, application notes and source code files.

Art.# 071102-71 • £29.00 • US\$ 58.00




SAPS-400

(May 2008)

The linear supply. With the SAPS-400 we offer a powerful, adjustable symmetrical supply that's ideal for lightweight audio power amplifiers and happily sits in less than a quarter of the space taken by a comparable supply of conventional design.

PCB, populated and tested, ready-mounted in aluminium U profile

Art.# 070688-91 • £159.00 • US\$ 318.00

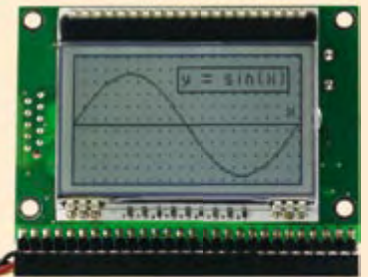

Display Computer

(May 2008)

Programming a graphic display is distinctly more difficult than programming a text display. Our mini microcontroller board features a new display-on-glass module and a high-performance Renesas M16C microcontroller. The board is available fully assembled, and the microcontroller is pre-loaded with a TinyBasic interpreter to simplify the development of graphics applications – even for novices.

PCB, populated and tested

Art.#070827-91 • £78.80 • US\$ 157.60




Elektor Internet Radio

(April 2008)

In the good old days, you had to modulate audio signals onto an RF carrier so they could be received and demodulated to produce something more or less audible. Nowadays things are different. Audio signals are compressed and put into IP packets that are 'streamed', and you can access every Internet radio programme in the world by receiving, buffering and decompressing these packages. This is all very easy with the Elektor Internet Radio: listening to radio programmes with the latest ICs. And all open-source! If you take a look on the Web, you'll be astounded to see that Google presently finds more than 21 million hits for 'Internet radio', so it's obviously a hot topic!

PCB, SMD-populated

Art.# 071081-71 • £115.00 • US\$ 230.00

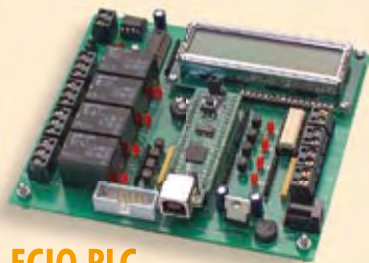


ECIO PLC

(March 2008)

An ECIO acts as the brains of this PLC board that has relays, opto-isolators CAN (!) connectivity and an LCD. All this I/O capacity together with Flowcode allows the board to act as a versatile, powerful PLC for quite complex control and automation projects. The LCD module is used to display ASCII characters to the user as a means of troubleshooting during the software development stage or for monitoring the system.

Kit of parts incl. PCB, ECIO-module and all other components

Art.# 070786-71 • £76.00 • US\$ 152.00

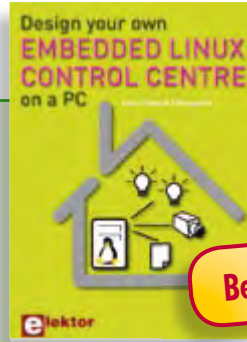


Bestseller!

A DIY system made from recycled components

Design your own Embedded Linux control centre on a PC

This book covers a do-it-yourself system made from recycled components. The main system described in this book re-uses an old PC, a wireless mains outlet with three switches and one controller, and a USB webcam. All this is linked together by Linux. This book will serve up the basics of setting up a Linux environment – including a software development environment – so it can be used as a control centre. The book will also guide you through the necessary setup and configuration of a webserver, which will be the interface to your very own home control centre. All software needed will be available for downloading from the Elektor website.

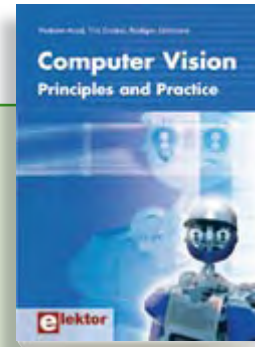234 pages • ISBN 978-0-905705-72-9
£24.00 • US\$ 48.00



Principles and Practice

Computer Vision

Computer vision is probably the most exciting branch of image processing, and the number of applications in robotics, automation technology and quality control is constantly increasing. Unfortunately entering this research area is, as yet, not simple. Those who are interested must first go through a lot of books, publications and software libraries. With this book, however, the first step is easy. The theoretically founded content is understandable and is supplemented by many examples.

320 pages • ISBN 978-0-905705-71-2
£32.00 • US\$ 64.00



Silent alarm, poetry box, night buzzer and more

PIC Microcontrollers

This hands-on book covers a series of exciting and fun projects with PIC microcontrollers. You can build more than 50 projects for your own use. The clear explanations, schematics, and pictures of each project on a breadboard make this a fun activity. You can also use it as a study guide. The technical background information in each project explains why the project is set up the way it is, including the use of datasheets. Even after you've built all the projects it will still be a valuable reference guide to keep next to your PC.

446 pages • ISBN 978-0-905705-70-5
£27.95 • US\$ 55.90

More information on the
Elektor Website:

www.elektor.com

Elektor

Regus Brentford

1000 Great West Road

Brentford

TW8 9HH

United Kingdom

Tel.: +44 20 8261 4509

Fax: +44 20 8261 4447

Email: sales@elektor.com

elektor
SHOP

Books




5.0, 6.0, VBA, .NET, 2005

Visual Basic for Electronics Engineering Applications

This book is targeted towards those people that want to control existing or self-built hardware from their computer. After familiarizing yourself with Visual Basic, its development environment and the toolset it offers are discussed in detail. Each topic is accompanied by clear, ready to run code, and where necessary, schematics are provided that will get your projects up to speed in no time.

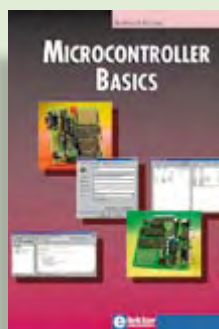476 pages • ISBN 978-0-905705-68-2
£29.95 • US\$ 59.90



More than just an introduction

Microcontroller Basics

Microcontrollers have become an indispensable part of modern electronics. They make things possible that vastly exceed what could be done previously. Innumerable applications show that almost nothing is impossible. There's thus every reason to learn more about them, but that raises the question of where to find a good introduction to this fascinating technology. This book offers more than just a basic introduction! It clearly explains the technology using various microcontroller circuits and programs written in several different programming languages.

ISBN 978-0-905705-67-5 • £19.95 • US\$ 39.90



Bestseller!

Modern technology for everyone

FPGA Course

FPGAs have established a firm position in the modern electronics designer's toolkit. Until recently, these 'super components' were practically reserved for specialists in high-tech companies. The nine lessons on this courseware CD-ROM are a step by step guide to the world of Field Programmable Gate Array technology. Subjects covered include not just digital logic and bus systems but also building an FPGA webserver, a 4-channel multimeter and a USB controller. The CD also contains PCB layout files in pdf format, a Quartus manual, project software and various supplementary instructions.

ISBN 978-90-5381-225-9 • £14.50 • US\$ 29.00



Software Tools & Hardware Tips

Ethernet Toolbox

This CD-ROM contains all essential information regarding Ethernet interfaces! Ethernet Toolbox includes a collection of datasheets for dedicated Ethernet interface ICs from many different manufacturers. It provides a wealth of information about connectors and components for the physical layer (PHY) and specific software tools for use with the Ethernet (Software). To help you learn about the Ethernet interfaces, we have compiled a collection of all articles on this topic that have appeared in Elektor and complemented them with additional documentation and links to introductory articles on Ethernet interfaces. The documents are PDF files.

ISBN 978-90-5381-214-3 • £19.50 • US\$ 39.00




All articles published in 2007

Elektor 2007

This CD-ROM contains all articles published in Elektor Volume 2007. Using the supplied Adobe Reader program, articles are presented in the same layout as originally found in the magazine. An extensive search machine is available to locate keywords in any article. The installation program now allows Elektor year volume CD-ROMs you have available to be copied to hard disk, so you do not have to eject and insert your CDs when searching in another year volume. With this CD-ROM you can produce hard copy of PCB layouts at printer resolution, adapt PCB layouts using your favourite graphics program, zoom in / out on selected PCB areas and export circuit diagrams and illustrations to other programs.

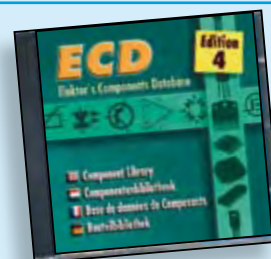ISBN 978-90-5381-218-1 • £17.50 • US\$ 35.00



More than 68,000 components

ECD 4

The program package consists of eight databanks covering ICs, germanium and silicon transistors, FETs, diodes, thyristors, triacs and optocouplers. A further eleven applications cover the calculation of, for example, LED series droppers, zener diode series resistors, voltage regulators and AMVs. A colour band decoder is included for determining resistor and inductor values. ECD 4 gives instant access to data on more than 68,000 components. All databank applications are fully interactive, allowing the user to add, edit and complete component data. This CD-ROM is a must-have for all electronics enthusiasts.

ISBN 978-90-5381-159-7 • £17.50 • US\$ 35.00

September 2008 (No. 381)

£ US\$

+++ Product Shortlist September: See www.elektor.com +++

July/August 2008 (No. 379/380)

Portable Thermometer

080418-41 Programmed controller PIC16F684.....9.00.....18.00

Dimmable LED light

070963-41 Programmed controller AVR2313.....11.90.....23.80

Solar-powered Automatic Lighting

080228-41 Programmed controller PIC12C671.....9.00.....18.00

Battery Discharge Meter

070821-41 Programmed controller PIC16F676-20I/P.....5.90.....11.80

070821-42 Programmed controller PIC16F628-20/P.....9.00.....18.00

Operating Hour Counter

070349-41 Programmed controller PIC12F683.....5.90.....11.80

Lamp in a Wine Bottle

080076-41 Programmed controller ATtiny45.....5.90.....11.80

Energy-efficient Backlight

080250-41 Programmed controller ATmega32.....22.50.....45.00

Deluxe '123' Game

080132-41 Programmed controller ATmega8-PU.....9.00.....18.00

Reaction Race using ATtiny13

080118-41 Programmed controller ATtiny13.....4.90.....9.80

Underwater Magic

071037-41 Programmed controller AT90S8515P.....14.90.....29.80

Flowcode for Garden Lighting

080113-41 Programmed controller PIC16F88.....11.90.....23.80

Tent Alarm

080135-41 Programmed controller ATtiny13V.....4.90.....9.80

Programmable Servo Driver

080323-41 Programmed controller PIC12F675.....5.90.....11.80

Simple USB AVR-ISP Compatible Programmer

080161-41 Programmed controller ATmega8-16AU.....11.90.....23.80

Intelligent Presence Simulator

080231-41 Programmed controller PIC12C508.....5.90.....11.80

LiPo Manager

080053-41 Programmed controller PIC16F84.....11.90.....23.80

GPS Receiver

080238-41 Programmed controller PIC16F876A.....23.00.....46.00

Universal Thermostat

080090-41 Programmed controller PIC16F628.....9.00.....18.00

DTMF-controlled Home Appliance Switcher

080037-41 Programmed controller ATmega8-16PC.....9.00.....18.00

Solar-powered Battery Charger

080225-41 Programmed controller PIC12C671.....9.00.....18.00

RGB Lights

080419-41 Programmed controller PIC12F675.....5.90.....11.80

Microlight Fuel Gauge

080054-41 Programmed controller ATmega8.....9.00.....18.00

Digital Rev Counter for (Older) Diesels

071133-41 Programmed controller AT90S2313.....5.90.....11.80

Golf Tally

080181-41 Programmed controller ATtiny44.....5.90.....11.80

Outside Light Controller

080258-41 Programmed controller PIC16F628A.....9.00.....18.00

June 2008 (No. 378)

Thermo-Snake

070122-41 PIC18F2550, ready-programmed.....13.20.....26.40

SAPS-400

070688-91 PCB, populated and tested, ready-mounted
in aluminium U profile.....159.00.....318.00

USB-to-TTL Serial Cable

080213-71 USB-to-TTL converter cable.....15.90.....31.80

May 2008 (No. 377)

Two-wire LCD

071035-93 SMD-populated board with all parts and pinheaders.....22.40.....44.80

Bestsellers

Books	1	↑	Embedded Linux Control Centre ISBN 978-0-905705-72-9 £24.00 US\$ 48.00
	2	↘	Computer Vision ISBN 978-0-905705-71-2 £32.00 US\$ 64.00
	3	↘	PIC Microcontrollers ISBN 978-0-905705-70-5 £27.95 US\$ 55.90
	4	↘	Visual Basic for Electronics Engineering Applications ISBN 978-0-905705-68-2 £29.95 US\$ 59.90
	5	→	Microcontroller Basics ISBN 978-0-905705-67-5 £19.95 US\$ 39.90
CD-ROMs	1	→	FPGA Course ISBN 978-90-5381-225-9 £14.50 US\$ 29.00
	2	→	Elektor 2007 ISBN 978-90-5381-218-1 £17.50 US\$ 35.00
	3	→	ECD 4 ISBN 978-90-5381-159-7 £17.50 US\$ 35.00
	4	↘	Ethernet Toolbox ISBN 978-90-5381-214-3 £19.50 US\$ 39.00
	5	↘	Home Automation ISBN 978-90-5381-195-5 £13.90 US\$ 27.80
Kits & Modules	1	→	DigiButler Art. # 071102-71 £29.00 US\$ 58.00
	2	↗	SAPS-400 Art. # 070688-91 £159.00 US\$ 318.00
	3	↘	Elektor Internet Radio Art.# 071081-71 £115.00 US\$ 230.00
	4	↘	Display Computer Art. # 070827-91 £78.80 US\$ 157.60
	5	→	ECIO PLC Art. # 070786-71 £76.00 US\$ 152.00

Order quickly and safe through
www.elektor.com/shop
 or use the Order Form near the end
 of the magazine!

elektor
SHOP

Elektor
 Regus Brentford
 1000 Great West Road
 Brentford TW8 9HH • United Kingdom
 Tel. +44 20 8261 4509
 Fax +44 20 8261 4447
 Email: sales@elektor.com

Elektor SMD Reflow Oven

SMDs (surface mount devices) are increasingly used in today's circuit design, but mounting these parts is not easy without industrial tools. However Elektor again comes up with the goods by presenting its very own SMD Reflow Oven. In this specially designed and manufactured oven, the temperature is accurately preset and controlled to maintain a certain curve that's optimised for baking SMDs onto a circuit board using different brands of solder paste. The oven is available commercially from the Elektor SHOP.




DMX512 Dimmer with MSP430

Although this digital lighting control system was originally designed for use in discotheques, it is equally at home at parties or other events. Our dimmer is controlled by the DMX512 protocol.

Some salient features of the circuit:

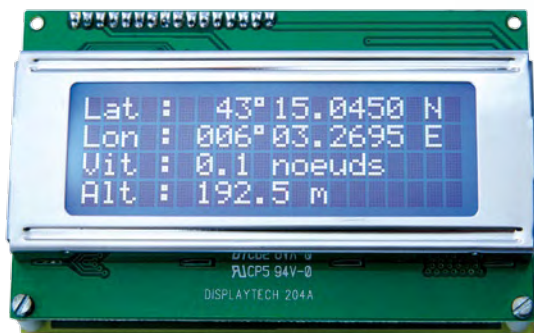- DMX input and output;
- 6 dimmable power output channels;
- Status LEDs and suppressor coils on each output;
- Switch for addressing and a 'copy' option.



Multifunctional GPS receiver

Motorists all over the world have embraced GPS technology for their navigation systems. Due to their small size, GPS receiver modules can be used for other purposes, too, like helping a robot to find its way about. In this article we not only explain how to enable a PC to talk to a GPS system, but also how such a system can be integrated into a robot.

RESERVE YOUR COPY NOW!

UK mainland subscribers will receive the magazine between 20 and 23 September 2008.

The October 2008 issue goes on sale on Thursday 25 September 2008 (UK distribution only).

Article titles and magazine contents subject to change, please check www.elektor.com.

www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com

Elektor on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Shop you'll find all other products sold by the publishers, like CD-ROMs, kits and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor website:

- Electronics news and Elektor announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Surveys and polls
- FAQ, Author Guidelines and Contact



Description	Price each	Qty.	Total	Order Code
Universal Display Book for PIC Microcontrollers NEW	£23.00			
Design your own Embedded Linux Control Centre on a PC NEW	£24.00			
Computer Vision NEW	£32.00			
CD-ROM FPGA Course	£14.50			
PIC Microcontrollers	£27.95			
DigiButler (071102-71)	£29.00			
SAPS-400 (070688-91)	£159.00			
Free Elektor Catalogue 2008				
<i>Sub-total</i>				
<i>P&P</i>				
Total paid				

Prices and item descriptions subject to change. The publishers reserve the right to change prices without prior notification. Prices and item descriptions shown here supersede those in previous issues. E. & O.E.

Name _____



Address + Post code _____

Tel. _____ Email _____

Date - - Signature _____

EL09

METHOD OF PAYMENT
(see reverse before ticking as appropriate)

- Bank transfer
- Cheque (UK-resident customers ONLY)
- Giro transfer
-  

Expiry date: _____

Verification code: _____

Please send this order form to*
(see reverse for conditions)

Elektor
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom
Tel.: +44 20 8261 4509
Fax: +44 20 8261 4447
www.elektor.com
sales@elektor.com

*USA and Canada residents may (but are not obliged to) use \$ prices, and send the order form to:
Old Colony Sound Lab
P.O. Box 876, Peterborough
NH 03458-0876. Tel. (603) 924-6371, 924-6526.
Fax: (603) 924-9467
Email: custserv@audioXpress.com

Yes, I am taking out an annual subscription to Elektor and receive a free 2GB MP3 player*.



- I would like:
- Standard Subscription (11 issues)
 - Subscription-Plus (11 issues plus the Elektor Volume 2008 CD-ROM)

* Offer available to Subscribers who have not held a subscription to Elektor during the last 12 months. Offer subject to availability. See reverse for rates and conditions.

Name _____



Address + Post code _____

Tel. _____ Email _____

Date - - Signature _____

EL09

METHOD OF PAYMENT
(see reverse before ticking as appropriate)

- Bank transfer
- Cheque (UK-resident customers ONLY)
- Giro transfer
-  

Expiry date: _____

Verification code: _____

Please send this order form to

Elektor
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom
Tel.: +44 20 8261 4509
Fax: +44 20 8261 4447
www.elektor.com
subscriptions@elektor.com

ORDERING INSTRUCTIONS, P&P CHARGES

Except in the USA and Canada, all orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. Online ordering: www.elektor.com/shop
Readers in the USA and Canada may (but are not obliged to) send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Old Colony Sound for applicable P&P charges. Please allow 4-6 weeks for delivery.
Orders placed on our Brentford office must include P&P charges (Priority or Standard) as follows: Europe: £6.00 (Standard) or £7.00 (Priority) Outside Europe: £9.00 (Standard) or £11.00 (Priority)

HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

Bank transfer into account no. 40209520 held by Elektor Electronics with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

COMPONENTS

Components for projects appearing in Elektor are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

TERMS OF BUSINESS

Delivery Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. **Returns** Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. **Damaged goods** Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). **Cancelled orders** All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5.00. **Patents** Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor does not accept responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor other than to supply goods as described or, at the option of Elektor, to refund the purchaser any money paid in respect of the goods. **Law** Any question relating to the supply of goods and services by Elektor shall be determined in all respects by the laws of England.

September 2007

SUBSCRIPTION RATES FOR ANNUAL SUBSCRIPTION

	Standard	Plus
United Kingdom	£42.00	£49.00
Surface Mail		
Rest of the World	£56.00	£63.00
Airmail		
Rest of the World	£71.00	£78.00

USA & Canada For US\$-prices please check www.elektor.com

HOW TO PAY

Bank transfer into account no. 40209520 held by Elektor Electronics. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of student-ship signed by the head of the college, school or university faculty. A standard Student Subscription costs £33.60, a Student Subscription-Plus costs £39.20 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twenty-five per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subscriptions cannot be cancelled after they have run for six months or more.

January 2008

Design your own Embedded Linux control centre on a PC



elektor
SHOP

This book is not about X10, ZigBee, Z-wave or any that's available commercially. Instead, it covers a do-it-yourself system made from recycled components. The main system described in this book reuses an old PC, a wireless mains outlet with three switches and one controller, and a USB webcam. All this is linked together by Linux – as it can be obtained free of charge. This book will serve up the basics of setting up a Linux environment – including a software development environment – so it can be used as a control centre. The book will also guide you through the necessary setup and configuration of a webserver, which will be the interface to your very own home control centre. All software will be available for downloading from the Elektor website.

234 pages • ISBN 978-0-905705-72-9 • £24.00 • US\$ 48.00

Elektor
Regus Brentford • 1000 Great West Road
Brentford TW8 9HH • United Kingdom
Tel. +44 20 8261 4509

Order quickly and safe through www.elektor.com/shop

INDEX OF ADVERTISERS

Allendale Electronics Ltd	www.pcb-soldering.co.uk	43	Lektronix	www.lektronix.net/about/careers	49
Antex Electronics Ltd	www.antex.co.uk	49	London Electronics College, Showcase	www.lec.org.uk	79
ATC Semitec Ltd, Showcase	www.atcsemitec.co.uk	78	MikroElektronika	www.mikroe.com	37, 39, 41
Avit Research, Showcase	www.avitresearch.co.uk	78	MQP Electronics, Showcase	www.mqp.com	79
Beijing Draco	www.ezpcb.com	33	Newbury Electronics	www.newburyelectronics.co.uk	67
Beta Layout, Showcase	www.pcb-pool.com	43, 78	Nurve Networks	www.xgamestation.com	67
Bitscope Designs	www.bitscope.com	3	Paltronix	www.paltronix.com	17
Bowood Electronics Ltd, Showcase	www.bowood-electronics.co.uk	78	Parallax	www.parallax.com	47
C S Technology Ltd, Showcase	www.cstech.co.uk	78	Peak Electronic Design	www.peakelec.co.uk	43
Decibit Co. Ltd, Showcase	www.decibit.com	78	Pico	www.picotech.com	11
Designer Systems, Showcase	www.designersystems.co.uk	78	Quasar Electronics	www.quasarelectronics.com	59
EasyDAQ, Showcase	www.easydaq.biz	78	Radiometrix, Showcase	www.radiometrix.com	79
Easysync, Showcase	www.easysync.co.uk	78	Robot Electronics, Showcase	www.robot-electronics.co.uk	79
electronicIndia	www.electronicindia.net	66	Robotiq, Showcase	www.robotiq.co.uk	79
Eltec, Showcase	www.eltec.com	78	RS Components	www.rswww.com/electronics	13
EMCelettronica Srl, Showcase	www.emcelettronica.com	78	ScanTool, Showcase	www.obd2cables.com , www.scantool.net	79
Eurocircuits	www.eurocircuits.com	74	Showcase	78, 79
First Technology Transfer Ltd, Showcase	www.ftt.co.uk	78	USB Instruments, Showcase	www.usb-instruments.com	79
FlexiPanel Ltd, Showcase	www.flexipanel.com	78	Virtins Technology, Showcase	www.virtins.com	79
FLYPCB	www.flypcb.com	67			
Future Technology Devices, Showcase	www.ftdichip.com	78			
ILP Electronics Ltd, Showcase	www.ilpelectronics.com	78			
Jaycar Electronics	www.jaycarelectronics.co.uk	2			
Labcenter	www.labcenter.com	88			

**Advertising space for the issue of 20 October 2008
may be reserved not later than 23 September 2008**

with Huson International Media – Cambridge House – Gogmore Lane – Chertsey, Surrey KT16 9AP – England – Telephone 01932 564 999 – Fax 01932 564998 – e-mail: p.brady@husonmedia.com to whom all correspondence, copy instructions and artwork should be addressed.

The Proteus Design Suite

Celebrating 20 Years of Innovation



- ↓ **1988** Labcenter commences trading with PC-B for DOS

↓ **1989.** First integrated autorouter added for PCB Design.
- ↓ **1990** Schematic Capture added to PCB Layout package

↓ **1991. World First** Schematic Capture for Windows™.

↓ **1992.** Topological route editing for easier PCB layout.

↓ **1993. Proteus** offers fully integrated circuit simulation.

↓ **1994.** Autorouter enhanced with Rip-Up and Retry algorithm.
- ↓ **1995** Gridless, shape based power plane support

↓ **1996.** True, mixed mode SPICE simulation introduced.

↓ **1997.** Interactive simulation - ideal for educational users.

↓ **1998.** PIC microcontroller simulation technology developed.

↓ **1999.** 8051 microcontroller simulation technology developed.
- ↓ **2000** World First Interactive MCU co-simulation (VSM)

↓ **2001.** High level language support added for MCU simulation.

↓ **2002.** ELECTRA adaptive shape based router interface added.

↓ **2003. World First** 32 bit MCU simulation support with ARM7.

↓ **2004.** Integration between Proteus VSM and MPLAB™.
- ↓ **2005** Redesigned GUI across the Proteus Design Suite

↓ **2006.** 3D visualisation engine integrated with ARES PCB Design.

↓ **2007. World First** USB schematic based USB Simulation.
- ↓ **2008** Coming Soon: Introduction of HDL support in simulation, ODB++ manufacturing output, improved core SPICE simulation algorithms, enhanced live DRC error checking and much more.

LABCENTER ELECTRONICS LTD

A technology pioneer in the EDA Industry since 1988
 Technical Support direct from the program authors
 Flexible packages and pricing tailored to customer requirements.



Labcenter Electronics Ltd, 53-55 Main Street, Grassington,
 North Yorks. BD23 5AA. Registered in England 4692454
 Tel: +44 (0)1756 753440, Email: info@labcenter.com